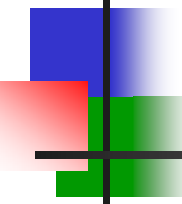




# 1. Transmission Line

---

( \* 2 )








---

1-1. Introduction .....	3
1-2. Transmission Lines .....	4
1-3. Equivalent Circuit .....	6
1-4. General Transmission Line Equation .....	8
1-5. Lossless transmission line .....	11
1-6. Microstrip Transmission Lines .....	14
1-7. Terminated Lossless line .....	20
1-8. Standing Waves .....	23
1-9. Special Termination Conditions .....	28
1-10. Sourced and loaded line .....	35
1-11. Power considerations for a line .....	38

# ■ 전송선의 용도

- 장비/모듈/부품의 연결
- 에너지 전송
- 등가회로 모델링

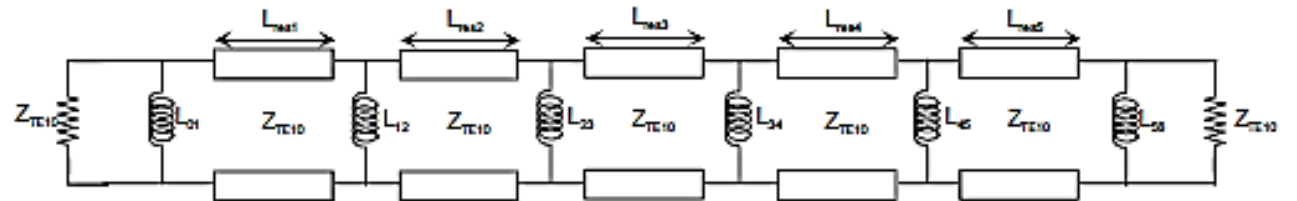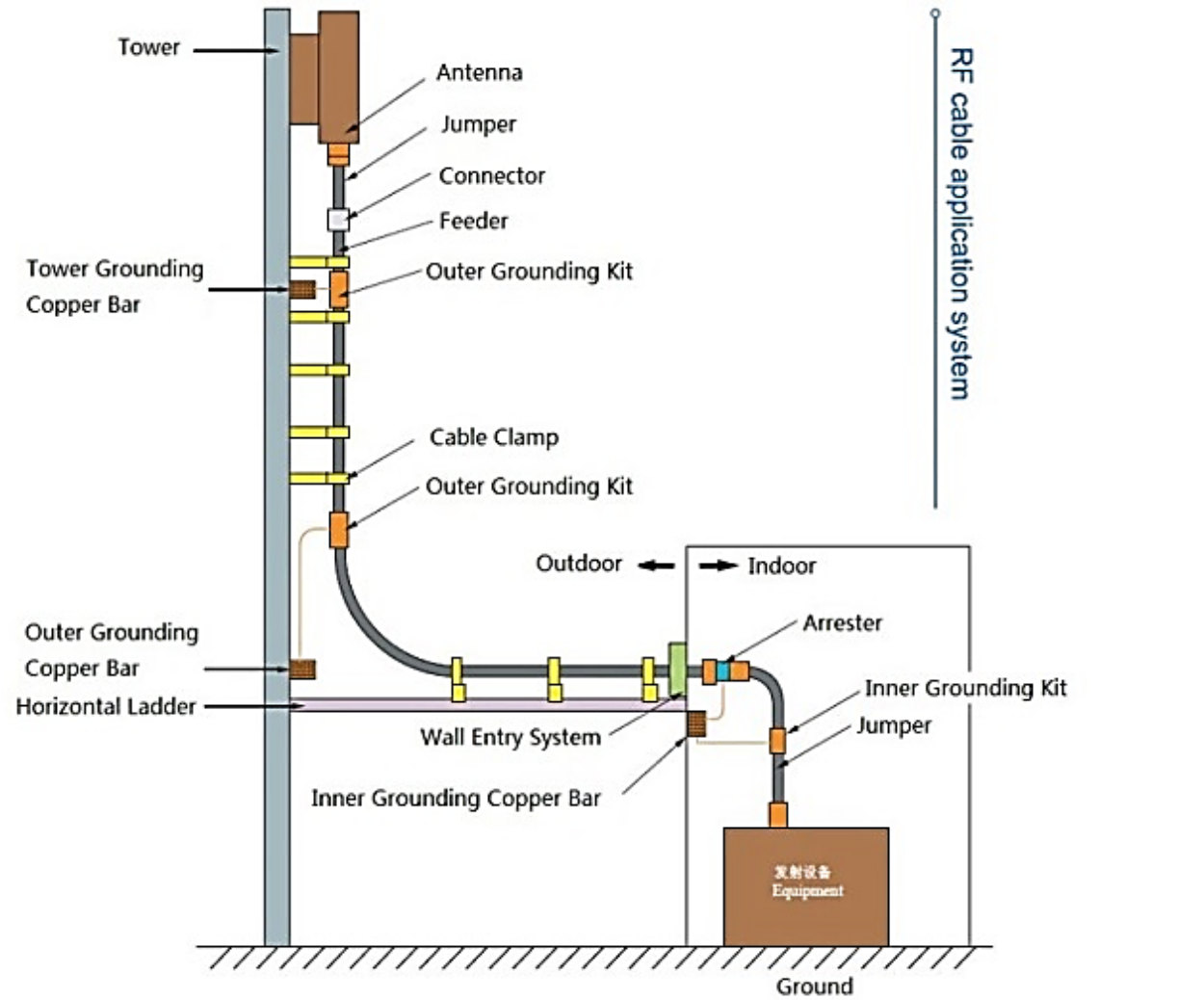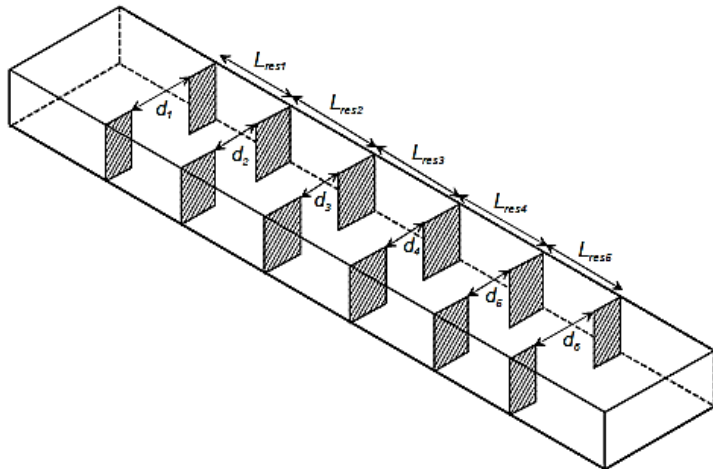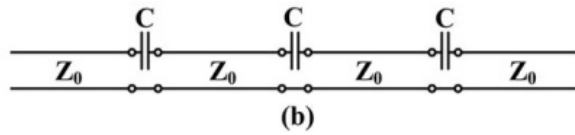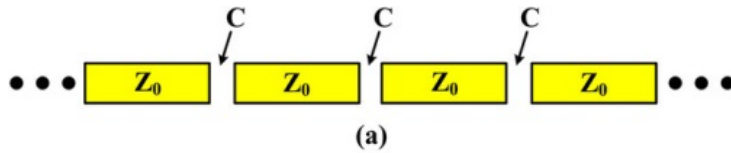

# 1-1. Introduction

At RF and microwave frequencies

- Physical size of circuit approaches to the wavelength - the phase of ac signal must be considered
  - ◆ At higher frequency range
  - ◆ For larger size of the circuits
- Voltage and Current must be treated as waves
  - ◆ Phasor notation is very convenient
  - ◆ On the circuit board one dimensional analysis is possible
- Distributed circuit approach must be used
  - ◆ Lumped element equivalent circuit approach enable us to use Basic Circuit Theory
  - ◆ Impedance is very important as in the Circuit Theory

# 1-2. Transmission Lines

- Two wire lines

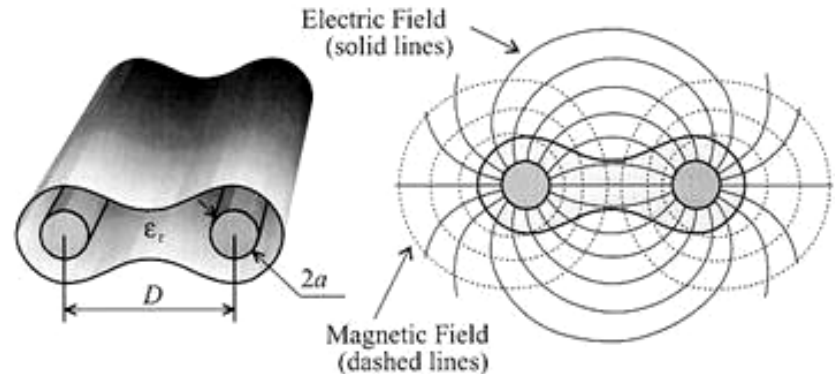


Figure 2-4 Geometry and field distribution in two-wire parallel conductor transmission line.

- Coaxial line

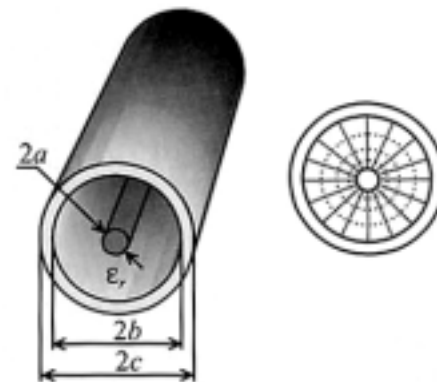


Figure 2-5 Coaxial cable transmission line.

# Transmission lines(2)

- Microstrip lines and Striplines

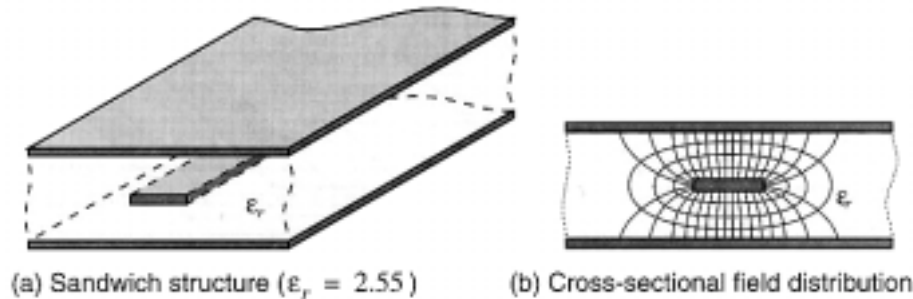


Figure 2-8 Triple-layer transmission line configuration.

- Parallel-plate transmission line

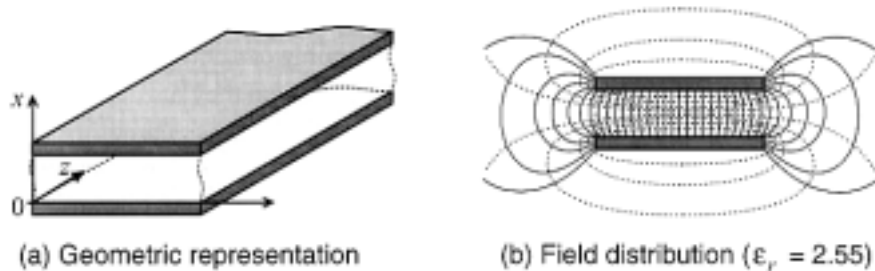


Figure 2-9 Parallel-plate transmission line.

# 1-3. Equivalent Circuit(1)

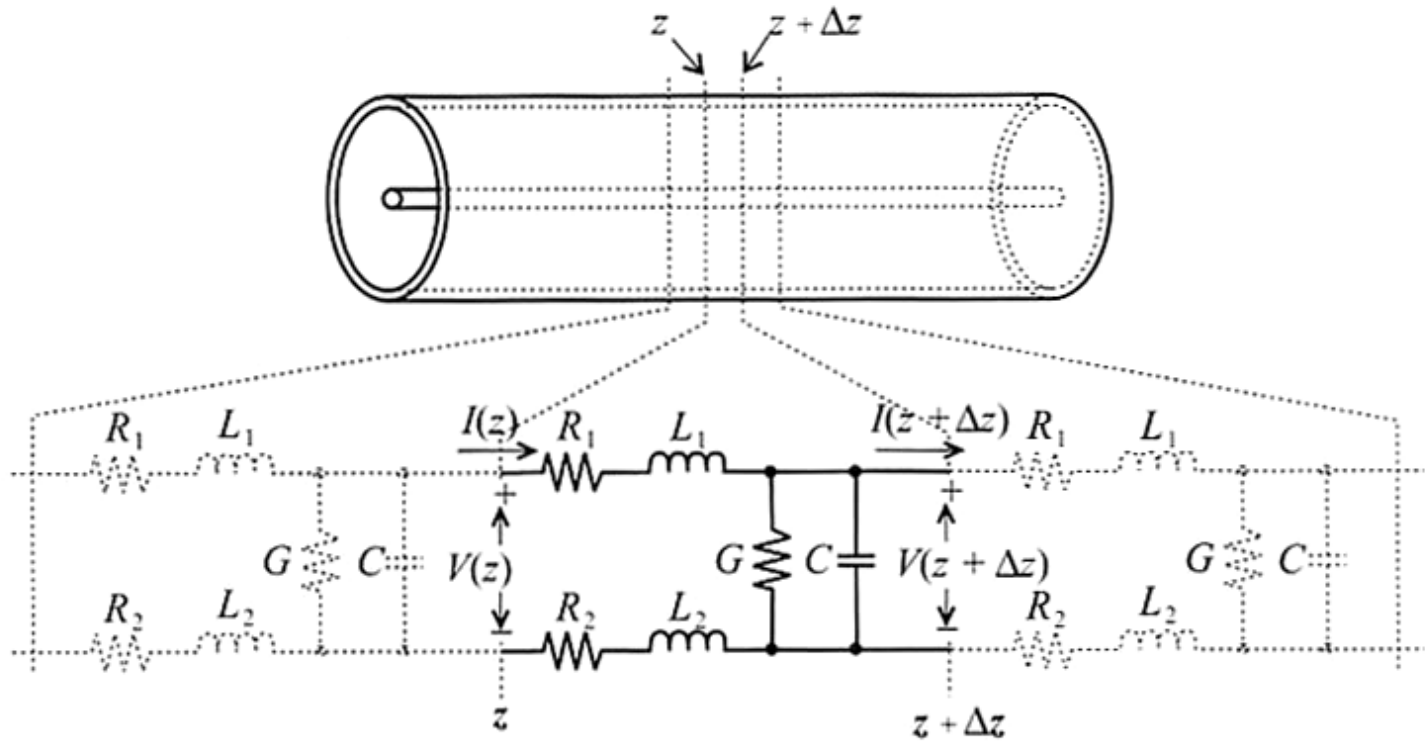


Figure 2-11 Segmentation of a coaxial cable into  $\Delta z$  length elements suitable for lumped parameter analysis.


# Equivalent circuit (2)

**Table 2-1** Transmission line parameters for three line types

Parameter	Two-Wire Line	Coaxial Line	Parallel-Plate Line	Unit
$R$	$\frac{1}{\pi a \sigma_{\text{cond}} \delta}$	$\frac{1}{2\pi \sigma_{\text{cond}} \delta} \left( \frac{1}{a} + \frac{1}{b} \right)$	$\frac{2}{w \sigma_{\text{cond}} \delta}$	$\Omega/\text{m}$
$L$	$\frac{\mu}{\pi} \text{acosh} \left( \frac{D}{2a} \right)$	$\frac{\mu}{2\pi} \ln \left( \frac{b}{a} \right)$	$\mu \frac{d}{w}$	$\text{H}/\text{m}$
$G$	$\frac{\pi \sigma_{\text{diel}}}{\text{acosh} (D/(2a))}$	$\frac{2\pi \sigma_{\text{diel}}}{\ln (b/a)}$	$\sigma_{\text{diel}} \frac{w}{d}$	$\text{S}/\text{m}$
$C$	$\frac{\pi \epsilon}{\text{acosh} (D/(2a))}$	$\frac{2\pi \epsilon}{\ln (b/a)}$	$\epsilon \frac{w}{d}$	$\text{F}/\text{m}$
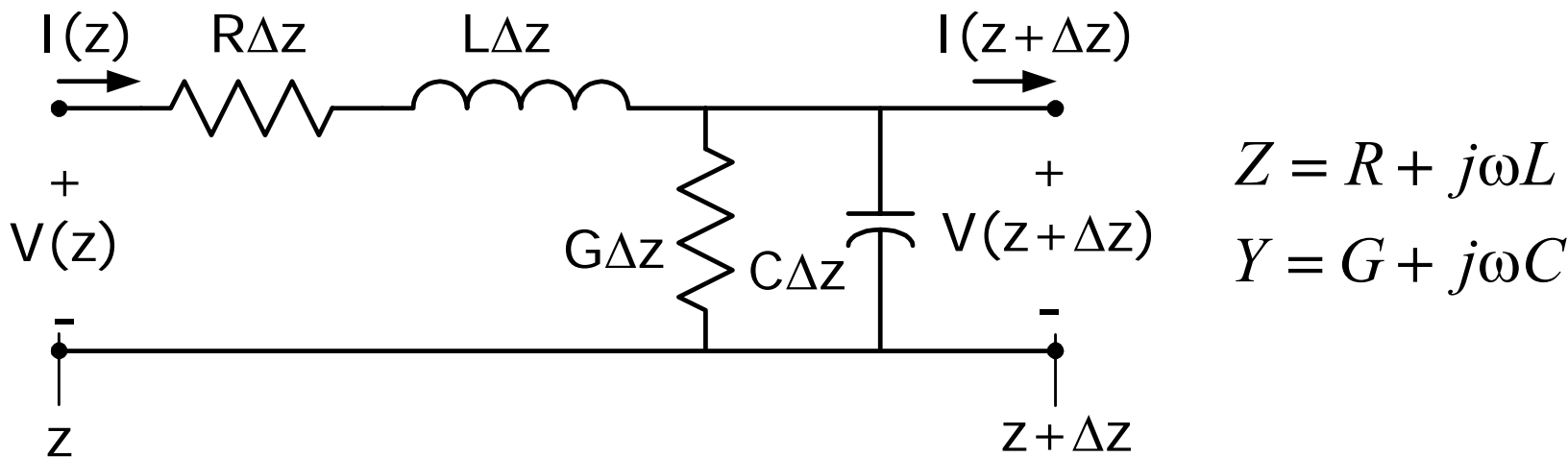
# 1-4. General Transmission Line Equation

- For a small segment of a transmission line
  - ◆ Lumped element equivalent circuit



- Apply KVL and KCL

$$V(z + \Delta z) = V(z) + \Delta V(z) \approx V(z) - Z\Delta z I(z)$$

$$I(z + \Delta z) = I(z) + \Delta I(z) \approx I(z) - Y\Delta z V(z)$$

## General Transmission Line Equation (2)

leads to the differential form as

$$\frac{dV}{dz} = -ZI, \quad \frac{dI}{dz} = -YV$$

or

$$\frac{d^2V}{dz^2} - ZYV = \frac{d^2V}{dz^2} - k^2V = 0, \quad \frac{d^2I}{dz^2} - k^2I = 0$$

where propagation constant  $k$  given as

$$k = \sqrt{ZY} = \sqrt{(R + j\omega L)(G + j\omega C)} = \alpha + j\beta$$

# General Transmission Line Equation (3)

- Voltage and current waves

$$V(z) = V^+ e^{-kz} + V^- e^{kz}, \quad I(z) = I^+ e^{-kz} + I^- e^{kz}$$

$$I(z) = -\frac{1}{Z} \frac{dV}{dz} = \frac{k}{Z} (V^+ e^{-kz} - V^- e^{kz}) = \frac{1}{Z_0} (V^+ e^{-kz} - V^- e^{kz})$$

where the characteristic impedance given as

$$Z_0 = \frac{V^+}{I^+} = \frac{V^-}{I^-} = \sqrt{\frac{Z}{Y}} = \sqrt{\frac{(R + j\omega L)}{(G + j\omega C)}}$$

# 1-5. Lossless transmission line

$$R = 0 \text{ and } G = 0$$

Propagation constant becomes

$$k = \sqrt{ZY} = j\omega\sqrt{LC} = j\beta$$

Characteristic impedance becomes

$$Z_0 = \sqrt{\frac{Z}{Y}} = \sqrt{\frac{L}{C}}$$

Voltage and current waves become

$$V(z) = V^+ e^{-j\beta z} + V^- e^{j\beta z}, \quad I(z) = I^+ e^{-j\beta z} + I^- e^{j\beta z}$$

## Low loss transmission line (2)

$$R \ll \omega L, \quad G \ll \omega C$$

Characteristic impedance ;

$$Z_0 = \sqrt{\frac{Z}{Y}} = \sqrt{\frac{R + j\omega L}{G + j\omega C}} = \sqrt{\frac{L}{C}} \left[ \left( 1 + \frac{R}{j\omega L} \right)^{\frac{1}{2}} \left( 1 + \frac{G}{j\omega C} \right)^{-\frac{1}{2}} \right]$$
$$\approx \sqrt{\frac{L}{C}} \left[ \left( 1 + \frac{R}{j2\omega L} \right) \left( 1 - \frac{G}{j2\omega C} \right) \right] \approx \sqrt{\frac{L}{C}} + j \sqrt{\frac{L}{C}} \left( \frac{R}{2\omega L} - \frac{G}{2\omega C} \right)$$

The real part of  $Z_0$  is the same as that of lossless transmission line.

# Low loss transmission line (3)


Propagation constant ;

$$\begin{aligned}k &= \sqrt{(R + j\omega L)(G + j\omega C)} = j\omega\sqrt{LC} \left[ \left(1 + \frac{R}{j\omega L}\right) \left(1 + \frac{G}{j\omega C}\right) \right]^{\frac{1}{2}} \\&\approx j\omega\sqrt{LC} \left(1 + \frac{R}{j2\omega L}\right) \left(1 + \frac{G}{j2\omega C}\right) \approx j\omega\sqrt{LC} \left(1 + \frac{R}{j2\omega L} + \frac{G}{j2\omega C}\right) \\&= \left(\frac{R}{2Z_0} + \frac{G}{2Y_0}\right) + j\omega\sqrt{LC} = \alpha + j\beta\end{aligned}$$

The phase constant is the same as that of lossless transmission line.

# 1-6. Microstrip Transmission Lines

- Microstrip Line geometry

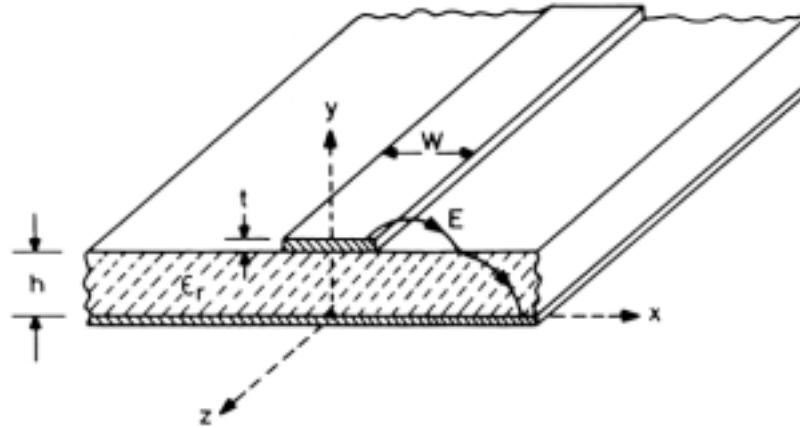

Assume that

't' is negligible compared to 'h' ;  $t/h < 0.005$   
depend only on 'w', 'h' and  $\epsilon_r$ .

# Microstrip Transmission Lines (2)

- For a narrow lines ;  $w/h < 1$

$$Z_0 = \frac{Z_f}{2\pi\sqrt{\epsilon_{eff}}} \ln\left(8\frac{h}{w} + \frac{w}{4h}\right) \quad : \text{characteristic line impedance}$$

$$Z_f = \sqrt{\mu_0/\epsilon_0} = 376.8 \Omega \quad : \text{wave impedance in free space}$$

$$\epsilon_{eff} = \frac{\epsilon_r + 1}{2} + \frac{\epsilon_r - 1}{2} \left[ \left(1 - 12\frac{h}{w}\right)^{-1/2} + 0.04\left(1 - \frac{w}{h}\right)^2 \right]$$

: effective dielectric constant

# Microstrip Transmission Lines (3)

- For a wide lines ;  $w/h > 1$

$$Z_0 = \frac{Z_f}{\sqrt{\epsilon_{eff} \left( 1.393 + \frac{w}{h} + \frac{2}{3} \ln \left( \frac{w}{h} + 1.444 \right) \right)}} \quad : \text{characteristic impedance}$$

$$\epsilon_{eff} = \frac{\epsilon_r + 1}{2} + \frac{\epsilon_r - 1}{2} \left( 1 + 12 \frac{h}{w} \right)^{-1/2} \quad : \text{effective dielectric constant}$$

- Wavelength

$$\lambda = \frac{v_p}{f} = \frac{1}{f} \frac{c}{\sqrt{\epsilon_{eff}}} = \frac{\lambda_0}{\sqrt{\epsilon_{eff}}}$$

# Microstrip Transmission Lines (4)

- $Z_0$  and  $\epsilon_{\text{eff}}$  are plotted as  $w/h$  and  $\epsilon_r$

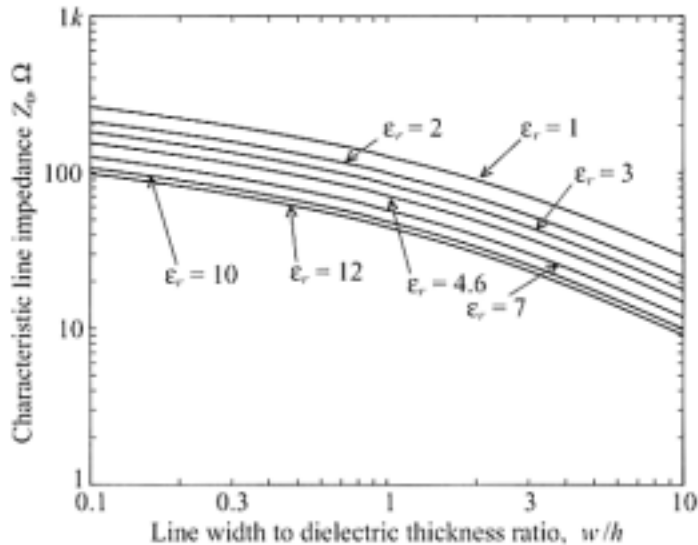


Figure 2-20 Characteristic line impedance as a function of  $w/h$ .

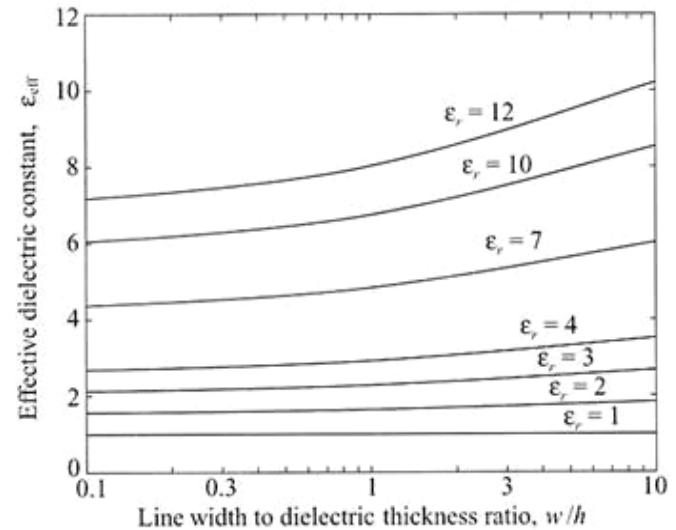


Figure 2-21 Effective dielectric constant as a function of  $w/h$  for different dielectric constants.

# Microstrip Transmission Lines (5)

- Assuming an infinitely thin line conductor,

$w/h < 2$  ;

$$\frac{w}{h} = \frac{8e^A}{e^{2A} - 2}$$

$$A = 2\pi \frac{Z_0}{Z_f} \sqrt{\frac{\epsilon_r + 1}{2}} + \frac{\epsilon_r - 1}{\epsilon_r + 1} \left( 0.23 + \frac{0.11}{\epsilon_r} \right)$$

$w/h > 2$  ;

$$\frac{w}{h} = \frac{2}{\pi} \left\{ B - 1 - \ln(2B - 1) + \frac{\epsilon_r - 1}{2\epsilon_r} \left[ \ln(B - 1) + 0.39 - \frac{0.61}{\epsilon_r} \right] \right\}$$

$$B = \frac{Z_f \pi}{2Z_0 \sqrt{\epsilon_r}}$$

# Microstrip Transmission Lines (6)

- Corrections for nonzero strip thickness  $t$  ;

$$w_{eff} = w + \frac{t}{\pi} \left( 1 + \frac{2x}{t} \right) \begin{cases} x = h & \text{if } w > h/(2\pi) > 2t \\ x = 2\pi w & \text{if } h/(2\pi) > w > 2t \end{cases}$$


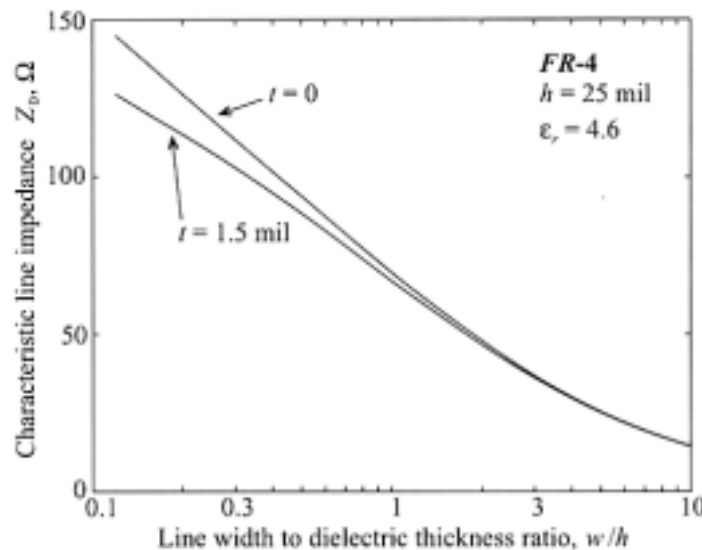


Figure 2-22 Effect of conductor thickness on the characteristic impedance of a microstrip line placed on a 25 mil thick FR-4 printed circuit board.
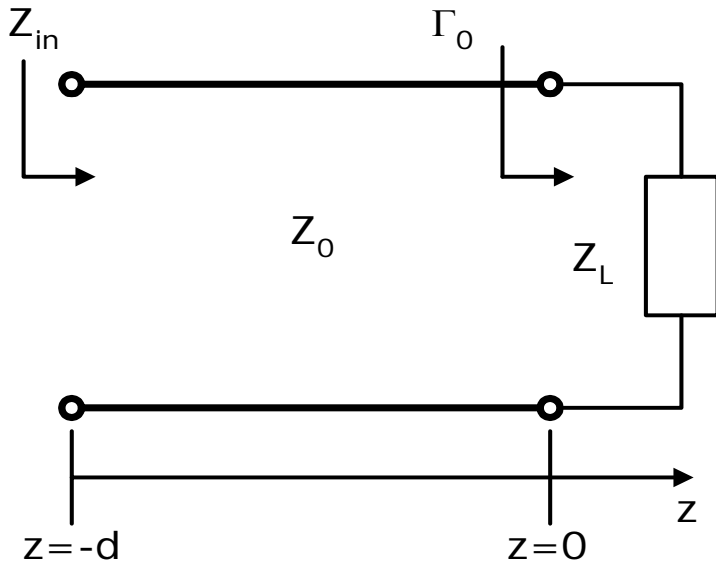
# 1-7. Terminated Lossless line

- Voltage Reflection Coefficient  $\Gamma_0$ ;



$$V(z) = V^+(0)e^{-j\beta z} + V^-(0)e^{j\beta z}$$
$$I(z) = \frac{1}{Z_0} (V^+(0)e^{-j\beta z} - V^-(0)e^{j\beta z})$$

$$= I^+(0)e^{-j\beta z} + I^-(0)e^{j\beta z}$$

$$\Gamma_0 = \frac{V^-(z=0)}{V^+(z=0)}$$

- Use standing wave concept

$$V(-d) = V^+ (1 + \Gamma_0 e^{-j2\beta d}), \quad I(-d) = \frac{V^+}{Z_0} (1 - \Gamma_0 e^{-j2\beta d})$$

# Terminated Transmission line (2)

- Input impedance  $z = -d$  ;

$$Z_{in} = \frac{V(-d)}{I(-d)} = Z_0 \frac{1 + \Gamma_0 e^{-j2\beta d}}{1 - \Gamma_0 e^{-j2\beta d}}$$

- Input impedance at  $z = 0$  ;

$$Z_{in}(0) = Z_L = \frac{V(0)}{I(0)} = Z_0 \frac{1 + \Gamma_0}{1 - \Gamma_0}$$


$$\Gamma_0 = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{\bar{Z}_L - 1}{\bar{Z}_L + 1} \quad : \text{ Reflection coefficient at load}$$

# Terminated Transmission line (3)

- Reflection coeff. for various terminations ;
  - ◆ Open line ( $Z_L \rightarrow \infty$ ):  $\Gamma_0 = 1$
  - ◆ Short circuit ( $Z_L = 0$ ):  $\Gamma_0 = -1$
  - ◆ Impedance matched ( $Z_L = Z_0$ ):  $\Gamma_0 = 0$
- For a infinite transmission line ;
  - ◆ Phase constant :  $\beta = \omega\sqrt{LC}$   
Since  $\lambda = \frac{v_p}{f} \rightarrow \beta = \frac{\omega}{v_p}$
  - ◆ Dispersion-free transmission line

# 1-8. Standing Waves

- Shorted transmission line ;

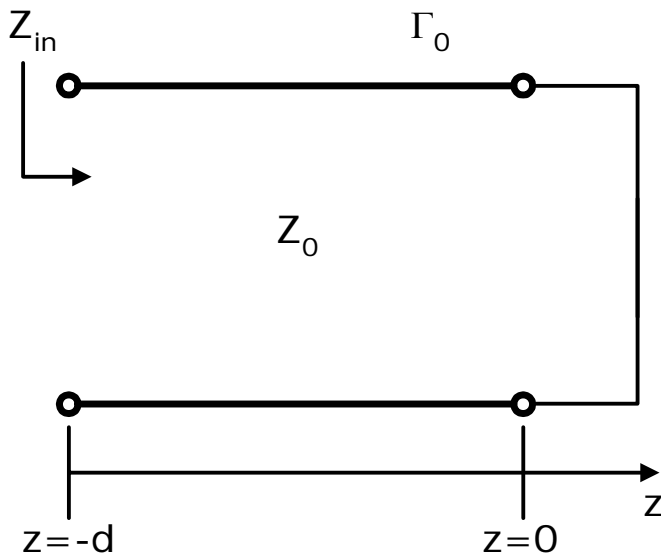

$$V(-d) = V^+ (e^{j\beta d} - e^{-j\beta d})$$
$$= j2V^+ \sin \beta d$$

$$I(-d) = \frac{V^+}{Z_0} (e^{j\beta d} + e^{-j\beta d})$$
$$= \frac{2V^+}{Z_0} \cos \beta d$$

- in the time domain ;

$$V(d, t) = \text{Re} \{ V e^{j\omega t} \} = \text{Re} \{ j2V^+ \sin \beta d e^{j\omega t} \}$$
$$= 2V^+ \sin \beta d \cos(\omega t + \pi/2)$$

# Standing Waves(2)


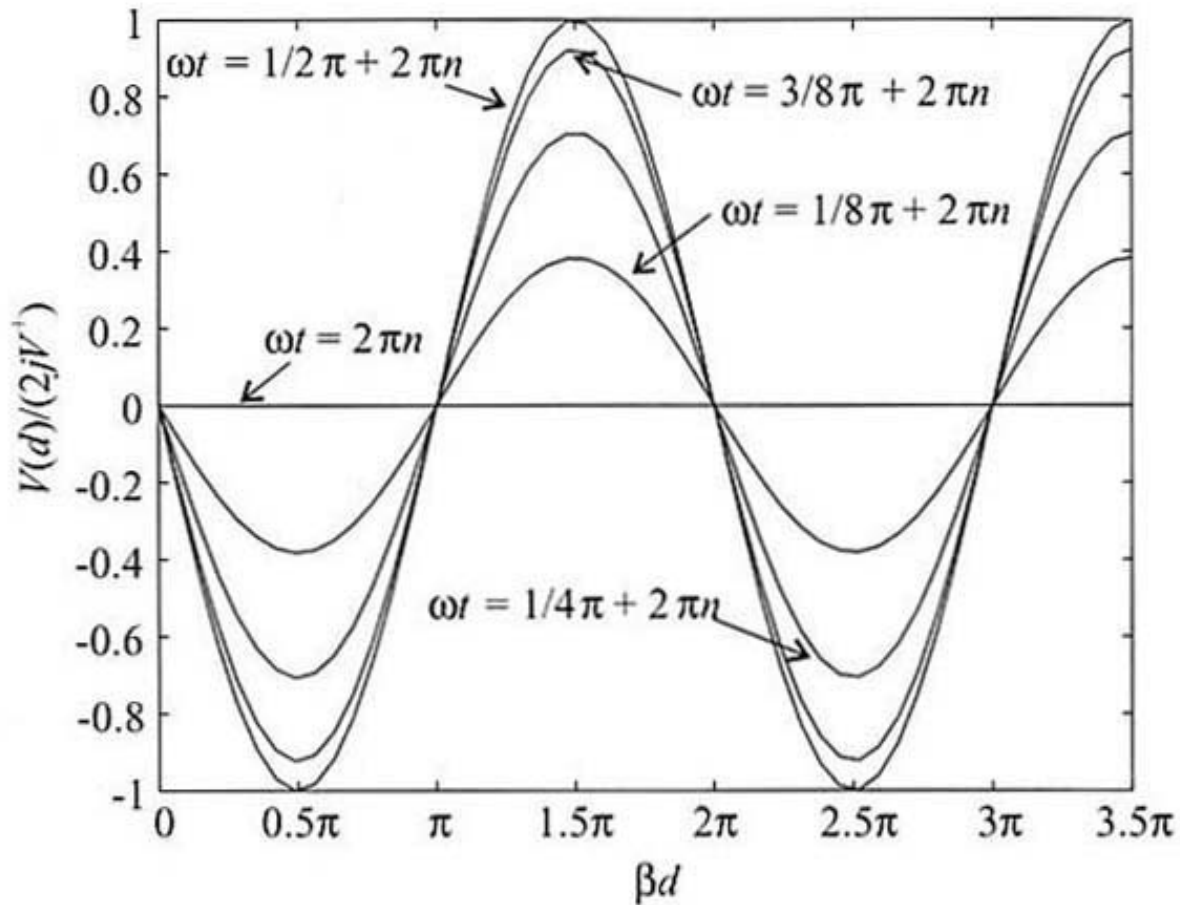


Figure 2-25 Standing wave pattern for various instances of time.

# Standing Waves(3)

- Standing wave expressions ;

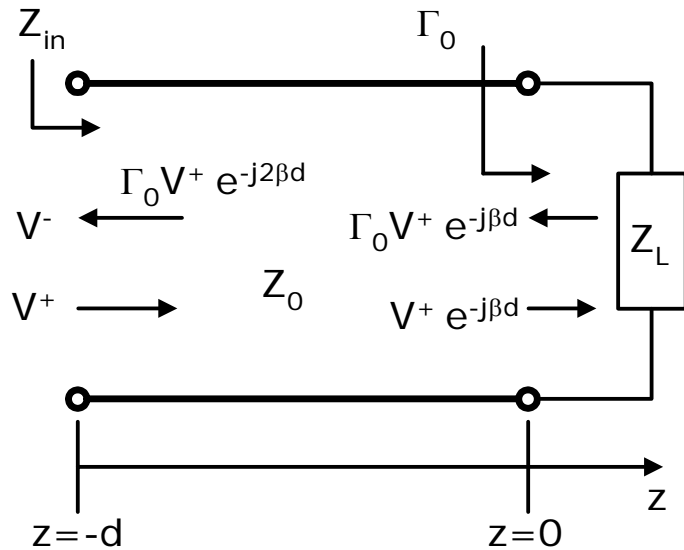

$$V(-d) = V^+ + V^-$$

$$= V^+ (1 + \Gamma_0 e^{-j2\beta d})$$

$$\Gamma(d) = \Gamma_0 e^{-j2\beta d}$$

$$V(-d) = A(d) [1 + \Gamma(d)]$$

$$I(-d) = \frac{A(d)}{Z_0} [1 - \Gamma(d)]$$

$$A(d) = V^+ e^{+j\beta d}$$

- Standing wave ratio(SWR) ;

$$SWR = \left| \frac{V_{\max}}{V_{\min}} \right| = \left| \frac{I_{\max}}{I_{\min}} \right| = \frac{1 + |\Gamma_0|}{1 - |\Gamma_0|} > 1$$

# Standing Waves(4)


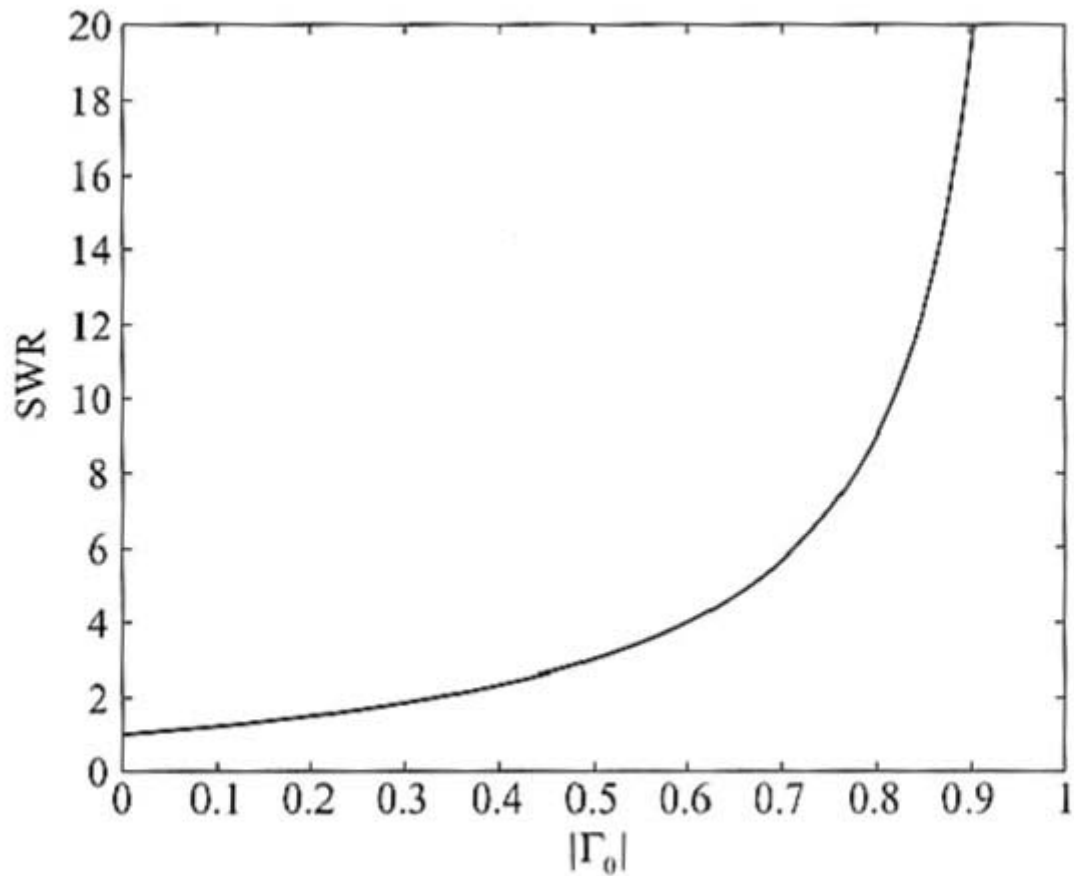


Figure 2-26 SWR as a function of load reflection coefficient  $|\Gamma_0|$ .

# Standing Waves(5)


- Graphical interpretation

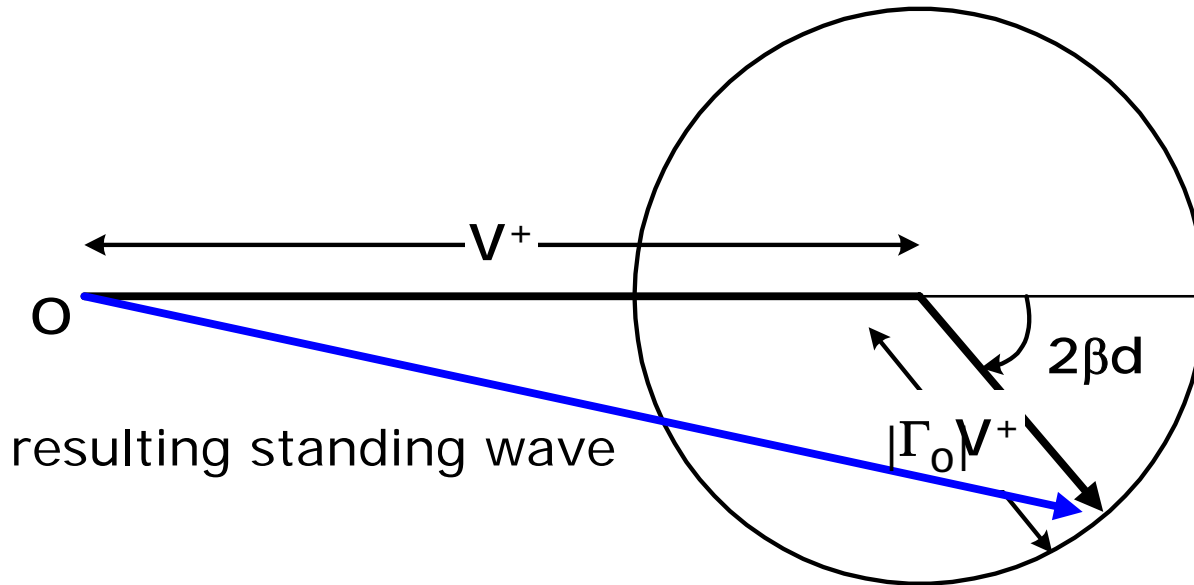

- Voltage standing wave ratio(VSWR)  
or return loss used:  $RL = -20\log|\Gamma(d)| = -20\log|\Gamma_0|$

# 1-9. Special Termination Conditions

- Input impedance of terminated line ;

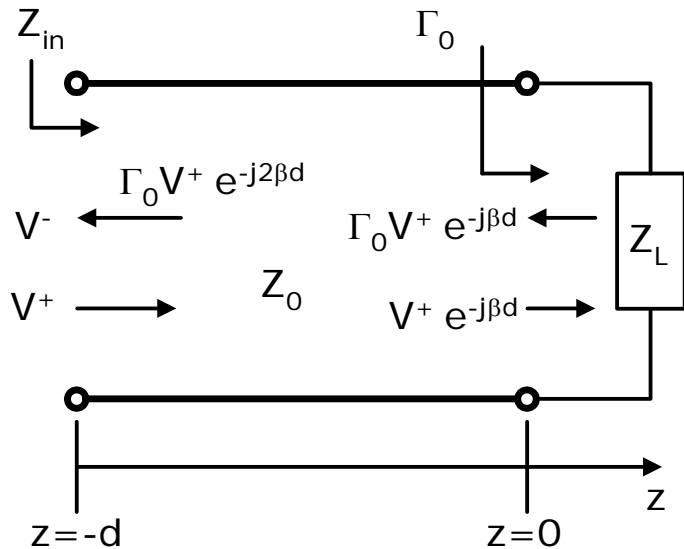

$$Z_{in}(-d) = \frac{V(-d)}{I(-d)} = Z_0 \frac{V^+ (1 + \Gamma_0 e^{-j2\beta d})}{V^+ (1 - \Gamma_0 e^{-j2\beta d})}$$


or

$$Z_{in}(-d) = Z_0 \frac{1 + \Gamma(-d)}{1 - \Gamma(-d)}$$

$$Z_{in}(-d) = Z_0 \frac{1 + \frac{Z_L - Z_0}{Z_L + Z_0} e^{-j2\beta d}}{1 - \frac{Z_L - Z_0}{Z_L + Z_0} e^{-j2\beta d}} = Z_0 \frac{Z_L + jZ_0 \tan \beta d}{Z_0 + jZ_L \tan \beta d}$$

# Special Termination Conditions(2)

## ■ Short Circuit Transmission Line

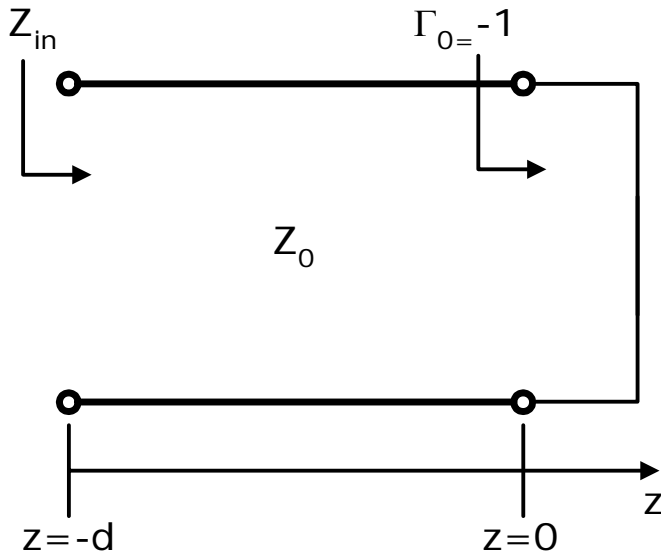

$$Z_{in}(-d) = jZ_0 \tan \beta d$$

$$\begin{aligned} V(-d) &= V^+ (e^{j\beta d} - e^{-j\beta d}) \\ &= j2V^+ \sin \beta d \end{aligned}$$

$$I(-d) = \frac{V^+}{Z_0} (e^{j\beta d} + e^{-j\beta d})$$

$$Z_{in}(-d) = Z_0 \left. \frac{Z_L + jZ_0 \tan \beta d}{Z_0 + jZ_L \tan \beta d} \right|_{Z_L=0}$$

$$= \frac{2V^+}{Z_0} \cos \beta d$$

# Special Termination Conditions(3)


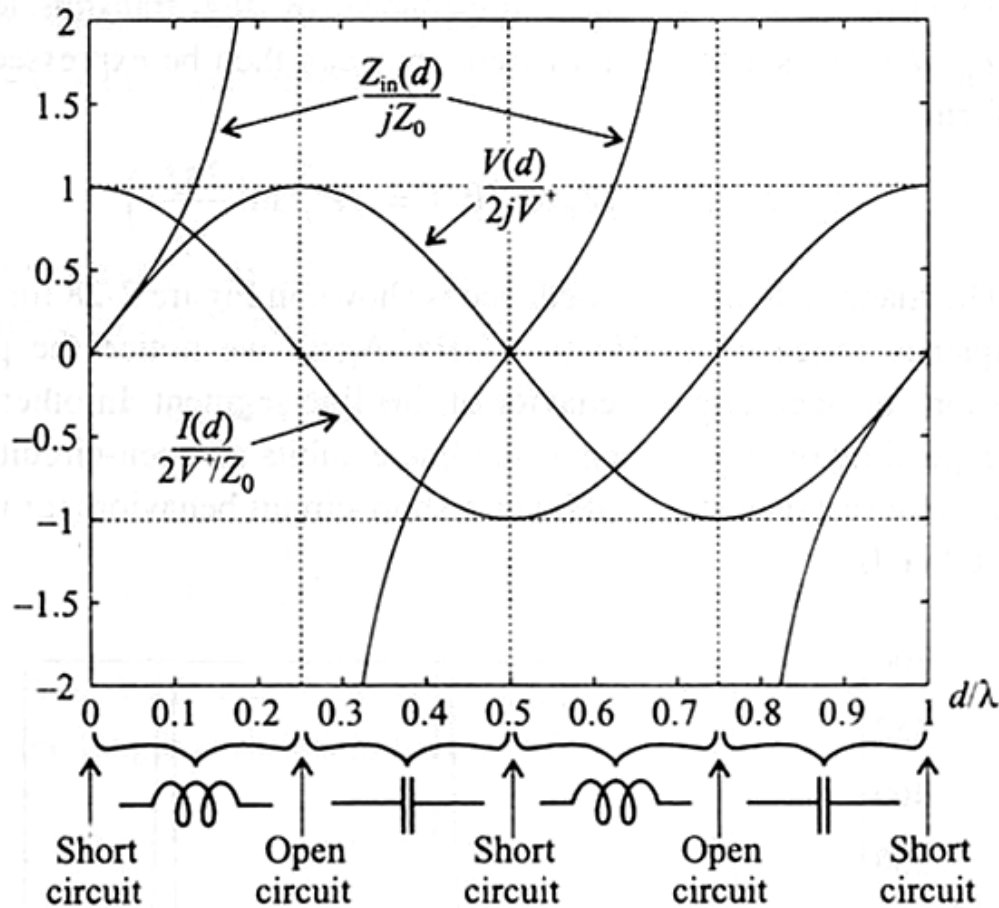


Figure 2-27 Voltage, current, and impedance as a function of line length for a short circuit termination.

# Special Termination Conditions(4)

## ■ Open-circuit transmission line

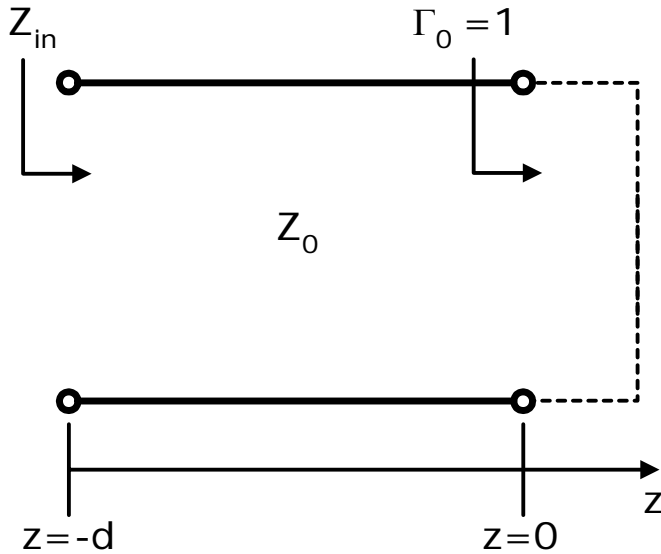

$$Z_{in}(-d) = -jZ_0 \cot \beta d$$

$$\begin{aligned} V(-d) &= V^+ (e^{j\beta d} + e^{-j\beta d}) \\ &= 2V^+ \cos \beta d \end{aligned}$$

$$I(-d) = \frac{V^+}{Z_0} (e^{j\beta d} - e^{-j\beta d})$$

$$= \frac{j2V^+}{Z_0} \sin \beta d$$

$$Z_{in}(-d) = Z_0 \left. \frac{Z_L + jZ_0 \tan \beta d}{Z_0 + jZ_L \tan \beta d} \right|_{Z_L \rightarrow \infty}$$

# Special Termination Conditions(5)


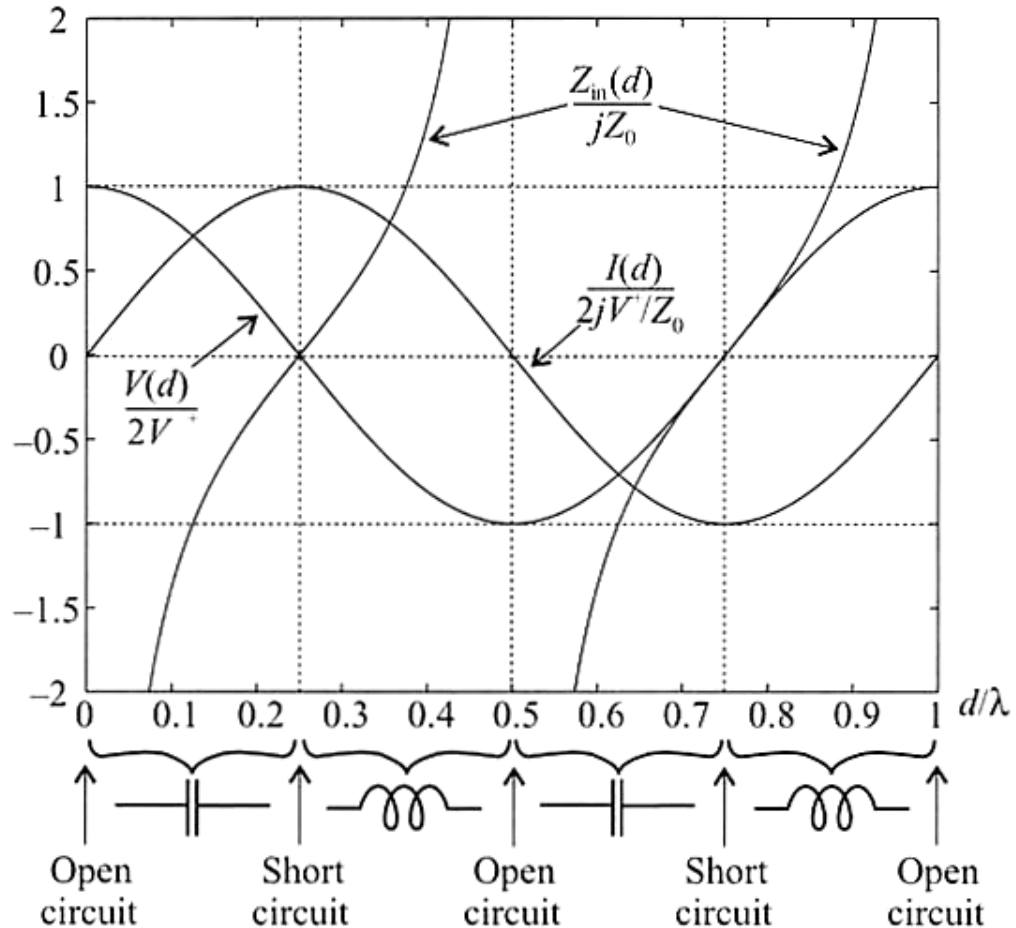


Figure 2-29 Voltage, current, and impedance as a function of line length for an open-circuit termination.

# Special Termination Conditions(6)

## ■ Quarter-wave transmission line

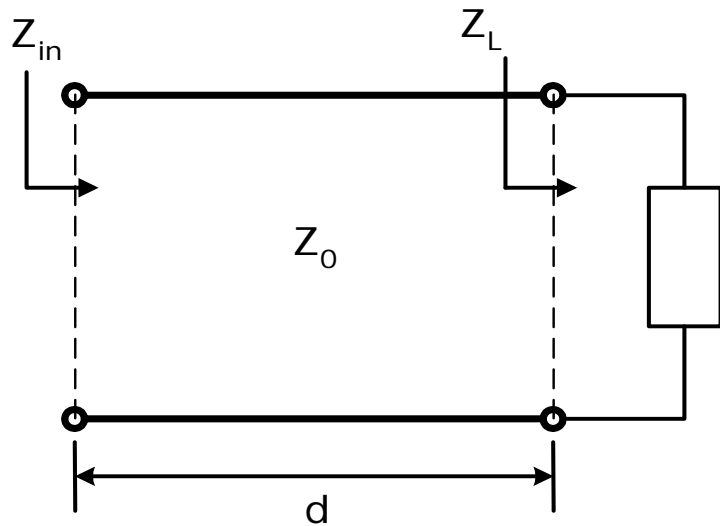

in case

$$d = \lambda/2(\lambda/2 + m\lambda/2, m = 1, 2, \dots)$$


$$\begin{aligned} Z_{in}(d = \frac{\lambda}{2}) &= Z_0 \frac{Z_L + jZ_0 \tan \beta d}{Z_0 + jZ_L \tan \beta d} \\ &= Z_0 \frac{Z_L + jZ_0 \tan \pi}{Z_0 + jZ_L \tan \pi} = Z_L \end{aligned}$$

## ◆ In case $d = \lambda/4(\lambda/4 + m\lambda/2, m = 1, 2, \dots)$

$$Z_{in}(d = \frac{\lambda}{4}) = Z_0 \frac{Z_L + jZ_0 \tan \beta d}{Z_0 + jZ_L \tan \beta d} = Z_0 \frac{Z_L + jZ_0 \tan \pi/2}{Z_0 + jZ_L \tan \pi/2} = \frac{Z_0^2}{Z_L}$$

# Special Termination Conditions(7)

- Quarter-wave transformer

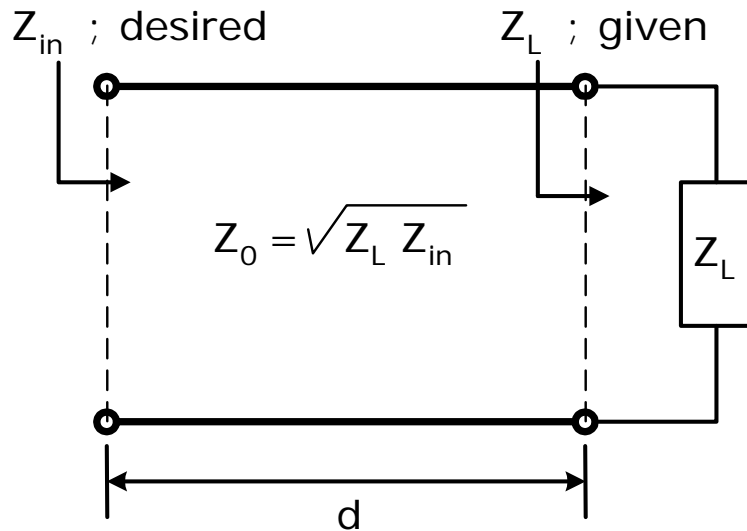


$$Z_{in}(d = \lambda / 4) = \frac{Z_0^2}{Z_L}$$

- ◆ impedance matching condition ;

$$Z_0 = \sqrt{Z_{in} Z_L}$$

# 1-10. Sourced and loaded line

- Phasor representation of source

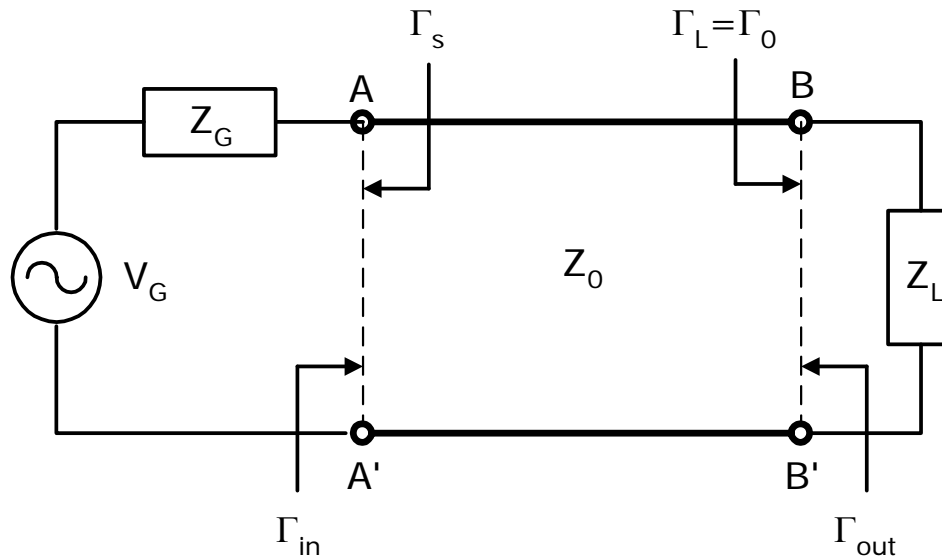

- ◆ Input voltage at plane AA' ;

$$V_{in} = V_{in}^+ + V_{in}^- = V_{in}^+ (1 + \Gamma_{in}) = V_G \left( \frac{Z_{in}}{Z_{in} + Z_G} \right)$$

## Sourced and loaded line(2)

- ◆ The input reflection coeff. at plane AA' ;  $d = \ell$

$$\Gamma_{in} = \Gamma(d = \ell) = \frac{Z_{in} - Z_0}{Z_{in} + Z_0} = \Gamma_0 \left( \frac{Z_{in}}{Z_{in} + Z_0} \right)$$

- ◆ The source reflection coeff. at plane AA' ;

$$\Gamma_s = \frac{Z_G - Z_0}{Z_G + Z_0}$$

- ◆ The source reflection coeff. at plane BB' ;

$$\Gamma_{out} = \Gamma_s e^{-j2\beta\ell}$$

# Sourced and loaded line(3)


- ◆ Transmission coefficient at plane AA' ;

$$T_{in} = 1 + \Gamma_{in} = \frac{2Z_{in}}{Z_{in} + Z_0}$$

- ◆ At the load end (at plane BB') ;

$$T_0 = 1 + \Gamma_0 = \frac{2Z_L}{Z_L + Z_0}$$

# 1-11. Power considerations for a line

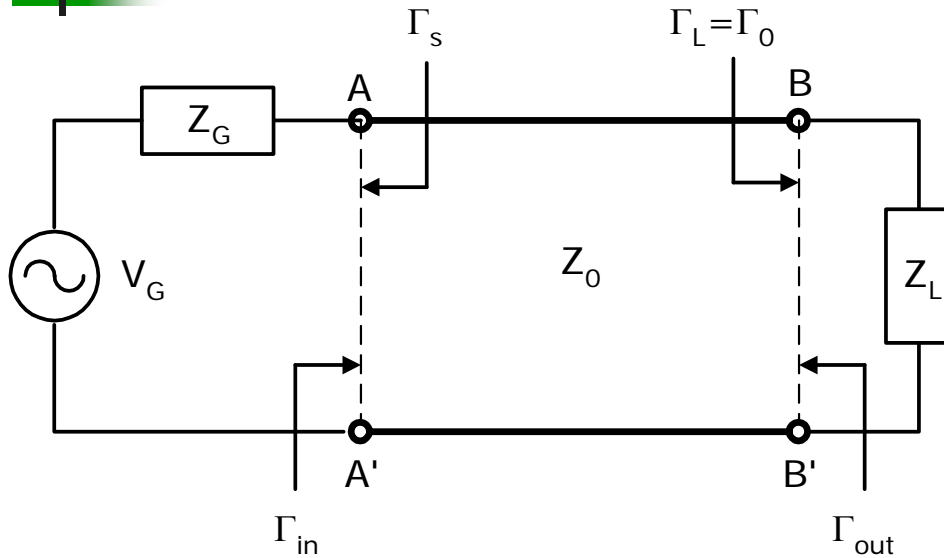

Time averaged power

$$P_{av} = \frac{1}{2} \text{Re}\{V I^*\}$$

- ◆ The total power at plane AA' ;

the complex input voltage :  $V_{in} = V_{in}^+(1 + \Gamma_{in})$

input current :  $I_{in} = (V_{in}^+ / Z_0)(1 - \Gamma_{in})$

$$P_{in} = P_{in}^+ + P_{in}^- = \frac{1}{2} \frac{|V_{in}^+|^2}{Z_0} (1 - |\Gamma_{in}|^2)$$

# Power considerations for a line(2)

- ◆ In terms of generator voltage ;

$$V_{in}^+ = \frac{V_{in}}{1 + \Gamma_{in}} = \frac{V_G}{1 + \Gamma_{in}} \left( \frac{Z_{in}}{Z_{in} + Z_G} \right)$$

- ◆ The input and the generator impedances ;

$$Z_{in} = Z_0 \frac{1 + \Gamma_{in}}{1 - \Gamma_{in}}, \quad Z_G = Z_0 \frac{1 + \Gamma_s}{1 - \Gamma_s}$$

- ◆ The generator voltage in terms of  $\Gamma_{in}$  and  $\Gamma_s$

$$P_{in} = \frac{1}{8} \frac{|V_G|^2}{Z_0} \frac{|1 - \Gamma_s|^2}{|1 - \Gamma_s \Gamma_{in}|^2} \left( 1 - |\Gamma_{in}|^2 \right)$$

# Power considerations for a line(3)

or

$$P_{in} = \frac{1}{8} \frac{|V_G|^2}{Z_0} \frac{|1 - \Gamma_s|^2}{|1 - \Gamma_s \Gamma_0 e^{-j2\beta\ell}|^2} \left( 1 - |\Gamma_0 e^{-j2\beta\ell}|^2 \right)$$

- ◆ When the impedances are matched ;

$$P_{in} = \frac{1}{8} \frac{|V_G|^2}{Z_0} = \frac{1}{8} \frac{|V_G|^2}{Z_G} \quad : \text{available power}$$

- ◆ When the source is not matched ;

$$P_{in} = \frac{1}{8} \frac{|V_G|^2}{Z_0} \left( 1 - |\Gamma_s|^2 \right) \quad : \text{available power at AA'}$$


# Transmission Line Theory

---


Microwave Engineering

EE 172


Dr. Ray Kwok

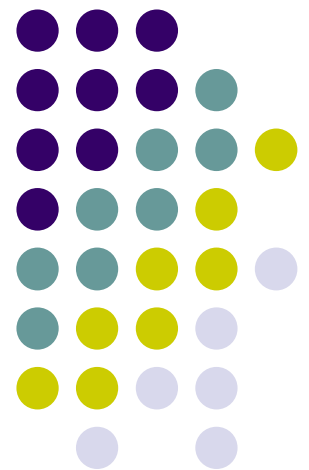


# RF Spectrum

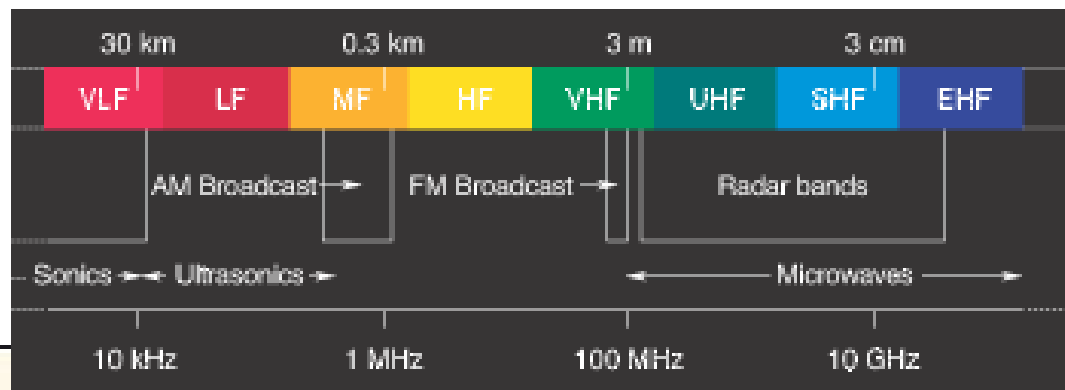


## THE ELECTROMAGNETIC SPECTRUM

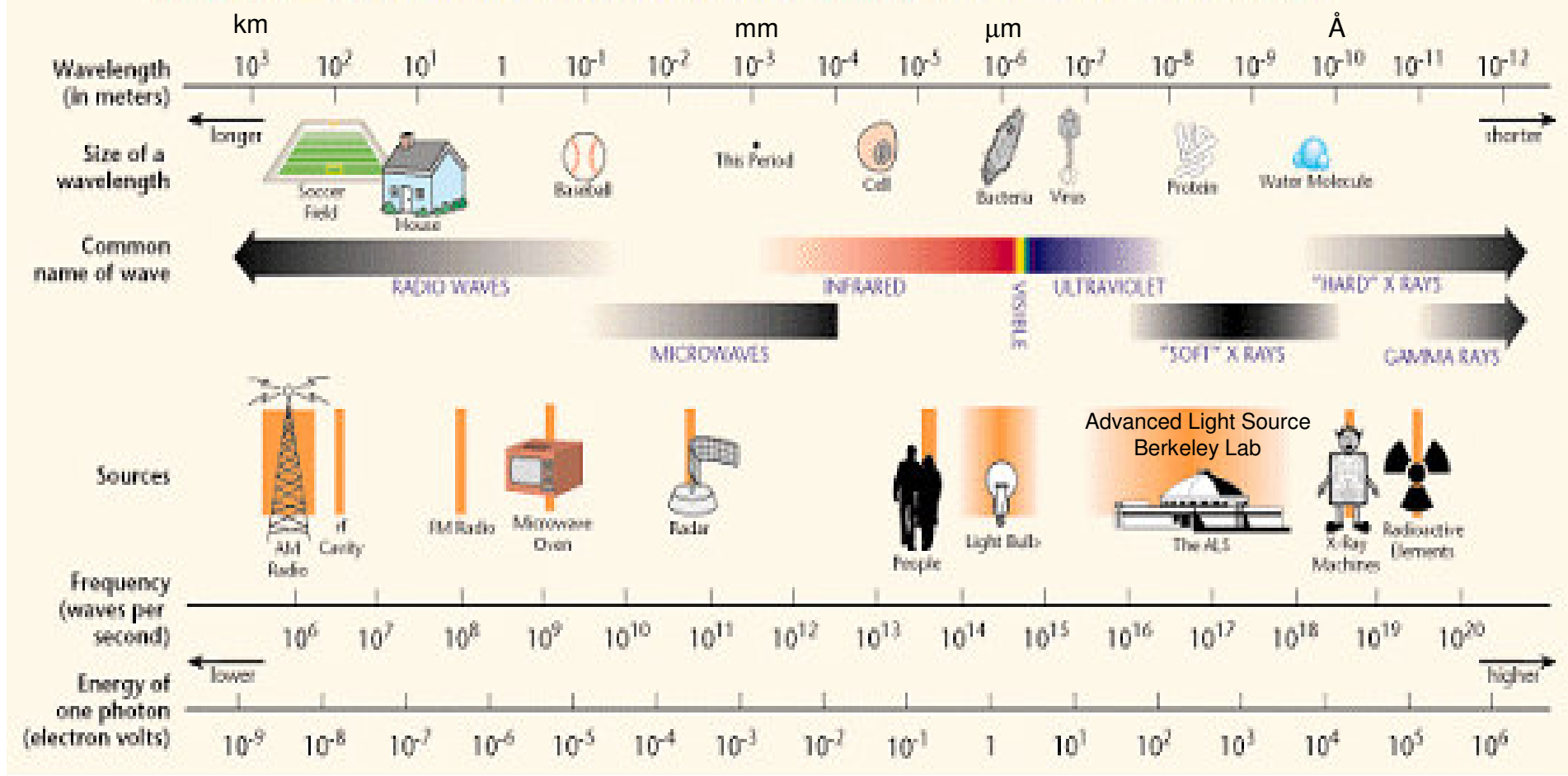

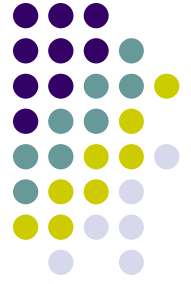


# RF / Microwave Circuit

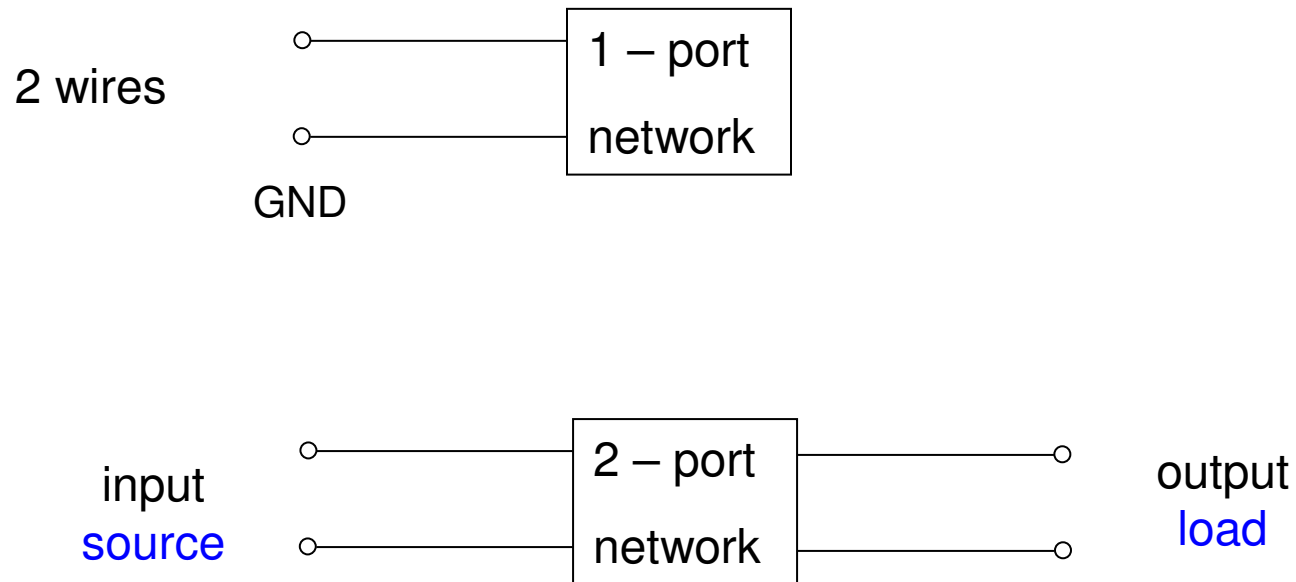





# Series connection

low f

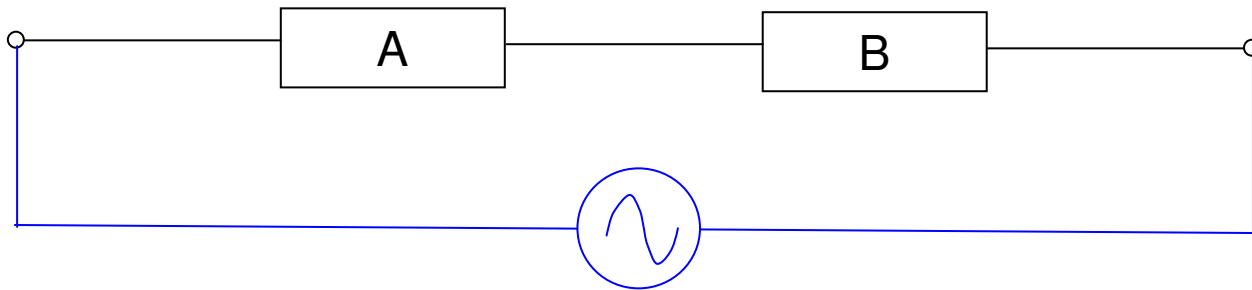


RF

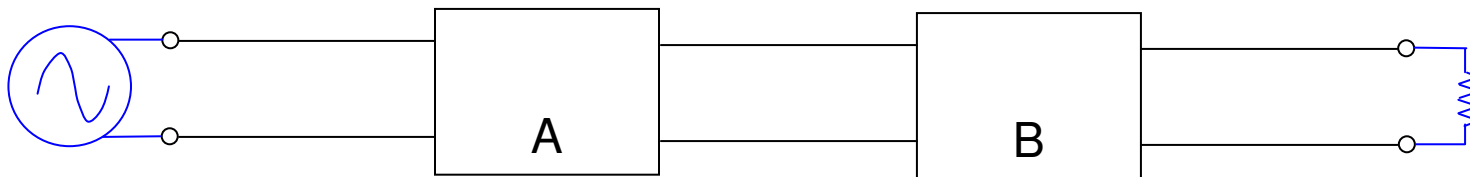

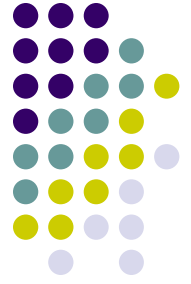


# Parallel connection

low f

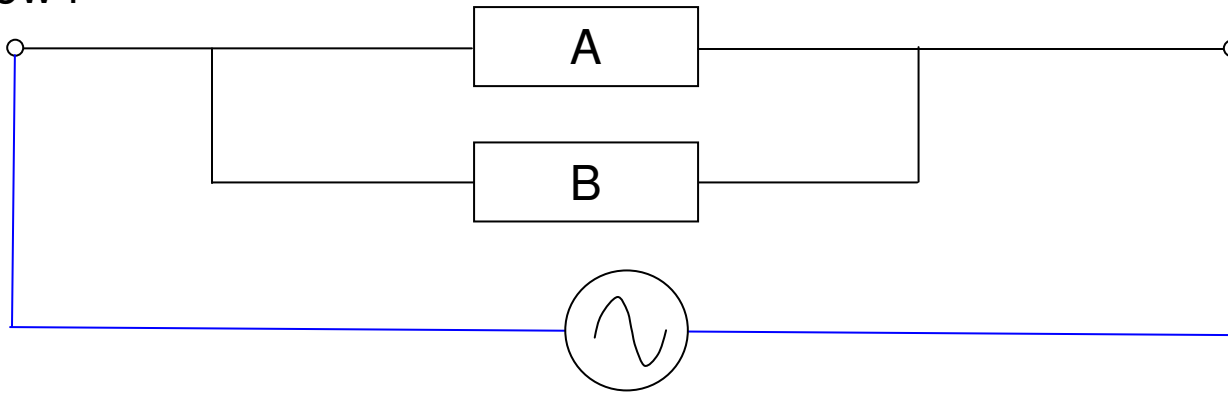


RF

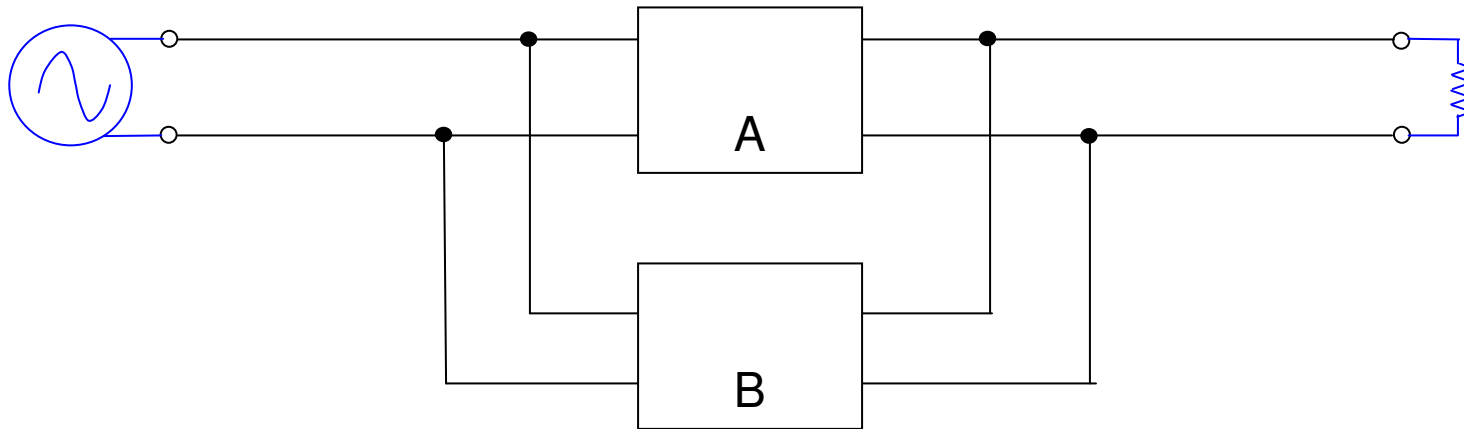




# Common transmission lines


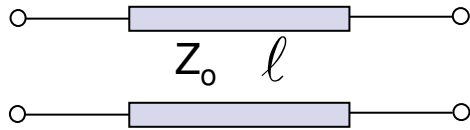


most correct schematic

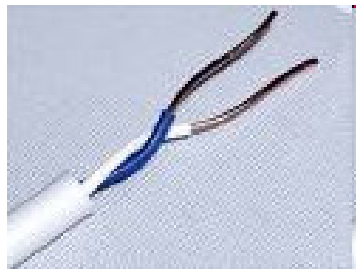



**twisted pair**  
VLF  
lossy & noisy

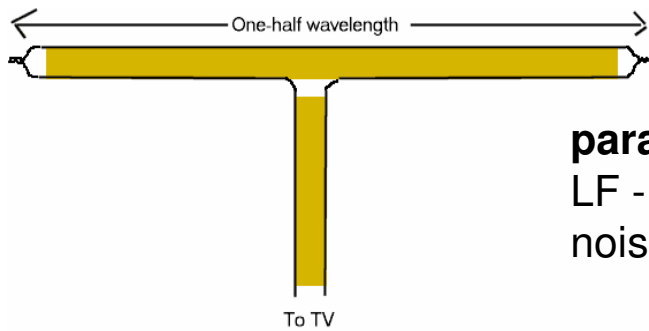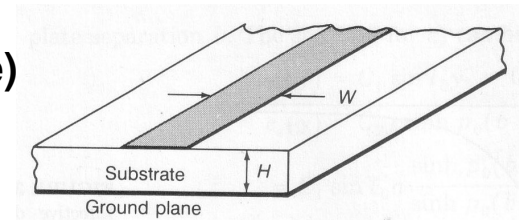**microstrip (line)**  
no distortion  
wide freq range  
lowest cost




**parallel wire**  
LF - HF  
noisy & lossy

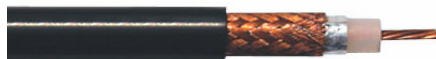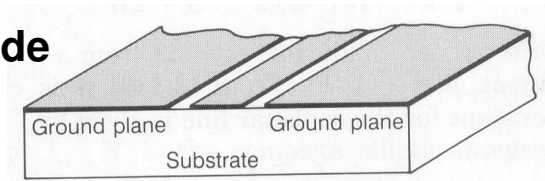
**co-planar waveguide**  
low cost  
flip chip access  
complex design




**coaxial cable**  
no distortion  
wide freq range

**waveguide**  
lowest loss  
freq bands

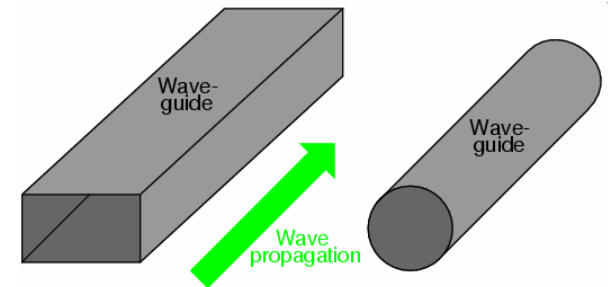

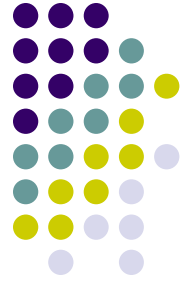

# Equivalent circuit

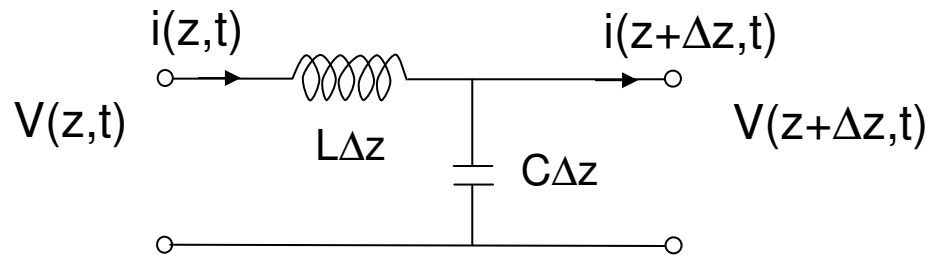

**Ideal** transmission line

Kirchhoff's law:  $V(z, t) - (L\Delta z) \frac{\partial i(z, t)}{\partial t} = V(z + \Delta z, t) \approx V(z, t) + \frac{\partial V(z, t)}{\partial z} \Delta z$  Taylor

$$\boxed{-L \frac{\partial i(z, t)}{\partial t} = \frac{\partial V(z, t)}{\partial z}}$$

Junction rule:  $i(z + \Delta z, t) - i(z, t) = -(C\Delta z) \frac{\partial V(z, t)}{\partial t} \approx \frac{\partial i(z, t)}{\partial z} \Delta z$

$Q = CV$   
 $dQ/dt = i = C dV/dt$

$$\boxed{-C \frac{\partial V(z, t)}{\partial t} = \frac{\partial i(z, t)}{\partial z}}$$



# Coupled equations (V – i)

$$-L \frac{\partial i(z, t)}{\partial t} = \frac{\partial V(z, t)}{\partial z}$$

$$-C \frac{\partial V(z, t)}{\partial t} = \frac{\partial i(z, t)}{\partial z}$$

$$-L \frac{\partial^2 i}{\partial t^2} = \frac{\partial^2 V}{\partial t \partial z} = \frac{\partial}{\partial z} \left( -\frac{1}{C} \frac{\partial i}{\partial z} \right) = -\frac{1}{C} \frac{\partial^2 i}{\partial z^2}$$

$$\frac{\partial^2 i}{\partial z^2} = LC \frac{\partial^2 i}{\partial t^2}$$

current wave

similarly

$$-C \frac{\partial^2 V}{\partial t^2} = \frac{\partial^2 i}{\partial t \partial z} = \frac{\partial}{\partial z} \left( -\frac{1}{L} \frac{\partial V}{\partial z} \right) = -\frac{1}{L} \frac{\partial^2 V}{\partial z^2}$$

$$\frac{\partial^2 V}{\partial z^2} = LC \frac{\partial^2 V}{\partial t^2}$$

voltage wave



# Wave equation

$$f(x \pm vt) \equiv f(u)$$

reverse / forward traveling wave

$$\frac{\partial f}{\partial x} = f'(u) \frac{\partial u}{\partial x} = f'(u)$$

$$\frac{\partial^2 f}{\partial x^2} = f''(u) \frac{\partial u}{\partial x} = f''(u)$$

$$\frac{\partial f}{\partial t} = f'(u) \frac{\partial u}{\partial t} = \pm v f'(u)$$

$$\frac{\partial^2 f}{\partial t^2} = \pm v f''(u) \frac{\partial u}{\partial t} = v^2 f''(u)$$

$$\frac{\partial^2 f}{\partial x^2} = \frac{1}{v^2} \frac{\partial^2 f}{\partial t^2}$$

wave equation

note:

$$x \pm vt = \frac{1}{k} \left( \frac{2\pi}{\lambda} x \pm \frac{2\pi}{\lambda} vt \right)$$

$$= \frac{1}{k} (kx \pm 2\pi ft)$$

$$= \pm \frac{1}{k} (\omega t \pm kx)$$

$$f(x \pm vt) = f(\omega t \pm kx)$$

$$f(\omega t - \vec{k} \cdot \vec{r}) \quad (3D)$$



# Voltage & Current Waves

$$V(z, t) = V_o^+ e^{j(\omega t - \beta z)} + V_o^- e^{j(\omega t + \beta z)}$$

$$i(z, t) = I_o^+ e^{j(\omega t - \beta z)} - I_o^- e^{j(\omega t + \beta z)}$$

where  $\beta = \frac{2\pi}{\lambda}$

$$v = f\lambda = (2\pi f) \left( \frac{\lambda}{2\pi} \right) = \frac{\omega}{\beta} = \frac{1}{\sqrt{LC}}$$

why "-" ?

$$\frac{\partial i}{\partial z} = -j\beta I_o^+ e^{j(\omega t - \beta z)} - j\beta I_o^- e^{j(\omega t + \beta z)}$$

$$\frac{\partial i}{\partial z} = -C \frac{\partial V}{\partial t} = -C [j\omega V_o^+ e^{j(\omega t - \beta z)} + j\omega V_o^- e^{j(\omega t + \beta z)}]$$


$$\beta I_o^+ = C\omega V_o^+$$

$$\beta I_o^- = C\omega V_o^-$$

$$V_o^\pm = \frac{\beta}{C\omega} I_o^\pm = \frac{\sqrt{LC}}{C} I_o^\pm = \sqrt{\frac{L}{C}} I_o^\pm \equiv Z_o I_o^\pm$$

$$v = \frac{1}{\sqrt{LC}}$$

$$Z_o = \sqrt{\frac{L}{C}}$$

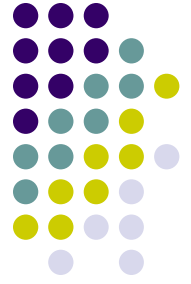

# Fields and circuits

$$\nabla^2 \begin{pmatrix} \vec{E} \\ \vec{H} \end{pmatrix} = \mu\epsilon \frac{\partial^2}{\partial t^2} \begin{pmatrix} \vec{E} \\ \vec{H} \end{pmatrix}$$

$$\vec{E}(z, t) = \vec{E}_{oi} e^{j(\omega t - \vec{k}_i \cdot \vec{r})} + \vec{E}_{or} e^{j(\omega t - \vec{k}_r \cdot \vec{r})}$$

$$\vec{H}(z, t) = \vec{H}_{oi} e^{j(\omega t - \vec{k}_i \cdot \vec{r})} - \vec{H}_{or} e^{j(\omega t - \vec{k}_r \cdot \vec{r})}$$

$$v = \frac{1}{\sqrt{\mu\epsilon}}$$

$$\eta = \sqrt{\frac{\mu}{\epsilon}}$$

$$\frac{\partial^2}{\partial z^2} \begin{pmatrix} V \\ i \end{pmatrix} = LC \frac{\partial^2}{\partial t^2} \begin{pmatrix} V \\ i \end{pmatrix}$$

$$V(z, t) = V_o^+ e^{j(\omega t - \beta z)} + V_o^- e^{j(\omega t + \beta z)}$$

$$i(z, t) = I_o^+ e^{j(\omega t - \beta z)} - I_o^- e^{j(\omega t + \beta z)}$$

$$v = \frac{1}{\sqrt{LC}}$$

$$Z_o = \sqrt{\frac{L}{C}}$$




# What is $Z_0$ ?

- Characteristic Impedance.
- 50 ohms for most communications system,
- 75 ohms for TV cable.
- Measure 75 ohms with a ohmmeter?
- Two  $75\Omega$  cables together (in series) makes a  $150\Omega$  cable?
- $75 + 75 = 75$  !!!!
- What does  $Z_0$  represent?



# Reflection at Load

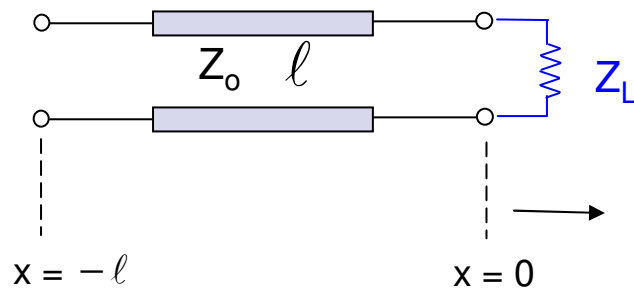

$$V(x) = V_o^+ e^{-j\beta x} + V_o^- e^{j\beta x}$$

$$i(x) = I_o^+ e^{-j\beta x} - I_o^- e^{j\beta x}$$

$$V(0) \equiv V_L = V_o^+ + V_o^- \quad \text{at the load}$$

$$i(0) \equiv I_L = I_o^+ - I_o^- = \frac{1}{Z_o} (V_o^+ - V_o^-)$$

$$\frac{V_L}{I_L} \equiv Z_L = Z_o \left( \frac{V_o^+ + V_o^-}{V_o^+ - V_o^-} \right)$$

$$Z_L (V_o^+ - V_o^-) = Z_o (V_o^+ + V_o^-)$$

$$V_o^+ (Z_L - Z_o) = V_o^- (Z_L + Z_o)$$

$$\frac{V_o^-}{V_o^+} \equiv \Gamma_L = \frac{Z_L - Z_o}{Z_L + Z_o}$$

$Z_L \neq Z_o$   
reflection

Define normalized impedance

$$\bar{Z} \equiv \frac{Z}{Z_o}$$

$$\Gamma_L = \frac{\bar{Z}_L - 1}{\bar{Z}_L + 1}$$



# Example

does it work?



$75\Omega$




$75\Omega$



$50\Omega$

# Impedance at Input

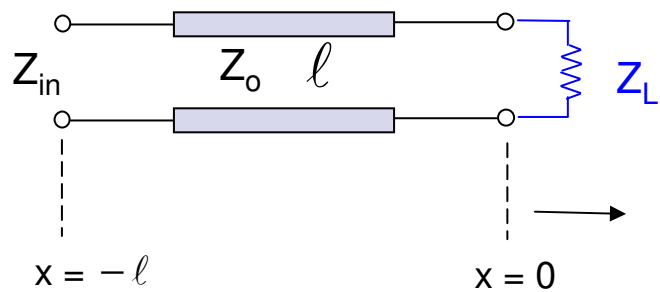

$$V(x) = V_o^+ e^{-j\beta x} + V_o^- e^{j\beta x}$$

$$i(x) = I_o^+ e^{-j\beta x} - I_o^- e^{j\beta x}$$

$$Z_{in} \equiv \frac{V_{in}}{I_{in}} = \frac{V(-l)}{i(-l)} = \frac{V_o^+ e^{j\beta l} + V_o^- e^{-j\beta l}}{\frac{1}{Z_o} (V_o^+ e^{j\beta l} - V_o^- e^{-j\beta l})}$$

$$Z_{in} = Z_o \left( \frac{e^{j\beta l} + \Gamma_L e^{-j\beta l}}{e^{j\beta l} - \Gamma_L e^{-j\beta l}} \right)$$


$$\bar{Z}_{in} = \frac{e^{-j\beta l} \left( \frac{1 + j \tan \beta l}{1 - j \tan \beta l} \right) + \left( \frac{\bar{Z}_L - 1}{\bar{Z}_L + 1} \right) e^{-j\beta l}}{e^{-j\beta l} \left( \frac{1 + j \tan \beta l}{1 - j \tan \beta l} \right) - \left( \frac{\bar{Z}_L - 1}{\bar{Z}_L + 1} \right) e^{-j\beta l}}$$


$$\bar{Z}_{in} = \frac{(\bar{Z}_L + 1)(1 + j \tan \beta l) + (\bar{Z}_L - 1)(1 - j \tan \beta l)}{(\bar{Z}_L + 1)(1 + j \tan \beta l) - (\bar{Z}_L - 1)(1 - j \tan \beta l)}$$

$$\bar{Z}_{in} = \frac{2(\bar{Z}_L + j \tan \beta l)}{2(1 + j \bar{Z}_L \tan \beta l)}$$


$$\bar{Z}_{in} = \frac{\bar{Z}_L + j \tan \beta l}{1 + j \bar{Z}_L \tan \beta l}$$
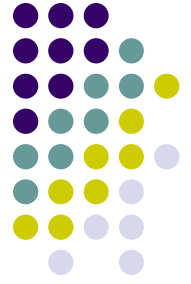
$$Z_{in} = Z_o \left( \frac{Z_L + j Z_o \tan \beta l}{Z_o + j Z_L \tan \beta l} \right)$$



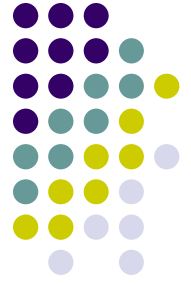

# Exercise

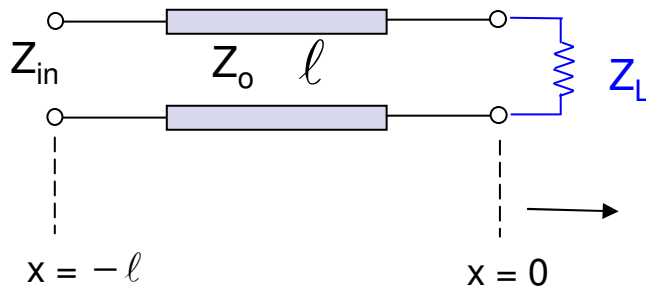

$$\begin{aligned} Z_o &= 50 \Omega \\ Z_L &= 100 \Omega \\ Z_{in} &= ? \end{aligned}$$

For length =  $\lambda/8$ ?  $\lambda/4$ ?  $\lambda/2$ ?

What if  $Z_o = Z_L = 50 \Omega$ ?

Would the length make any difference?

$$\bar{Z}_{in} = \frac{\bar{Z}_L + j \tan \beta l}{1 + j \bar{Z}_L \tan \beta l}$$


$$Z_{in} = Z_o \left( \frac{Z_L + j Z_o \tan \beta l}{Z_o + j Z_L \tan \beta l} \right)$$

$$50 \Omega \angle -37^\circ$$


$$25 \Omega$$

$$100 \Omega$$

$$Z_{in} = Z_o = Z_L$$

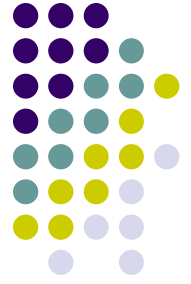

# Transmission Line Impedance

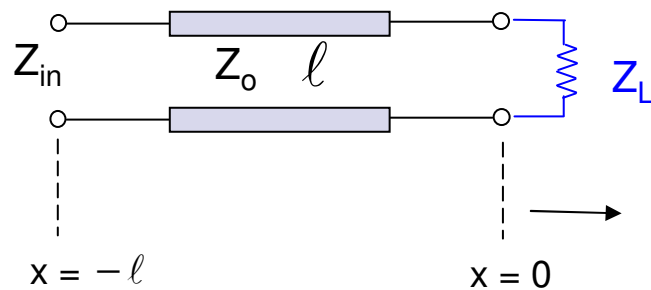

$$\bar{Z}_{in} = \frac{\bar{Z}_L + j \tan \beta l}{1 + j \bar{Z}_L \tan \beta l}$$

$$Z_{in} = Z_o \left( \frac{Z_L + j Z_o \tan \beta l}{Z_o + j Z_L \tan \beta l} \right)$$

case 1:  $\beta l = 0$ , or  $l = 0$

$$\tan \beta l = 0$$

$$Z_{in} = Z_L$$

case 2:  $\beta l = \pi$ , or  $l = \lambda/2$

$$\tan \beta l = 0$$

$$Z_{in} = Z_L$$

case 3:  $\beta l = \pi/2$ , or  $l = \lambda/4$

$$\tan \beta l \rightarrow \infty$$


$$Z_{in} = Z_o^2 / Z_L$$

Quarter-wave transformer (impedance),  
real-to-real, complex-to-complex.

note: at low freq,  $\beta \rightarrow 0$ ,  $Z_{in} = Z_L$  regardless of line length or line impedance.



# Reflection at Input

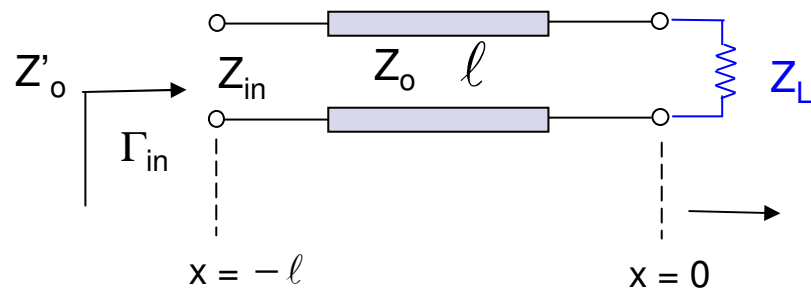

$$\bar{Z}_{in} = \frac{\bar{Z}_L + j \tan \beta l}{1 + j \bar{Z}_L \tan \beta l}$$

$$Z_{in} = Z_o \left( \frac{Z_L + j Z_o \tan \beta l}{Z_o + j Z_L \tan \beta l} \right)$$

$$\Gamma_{in} = \frac{Z_{in} - Z_o}{Z_{in} + Z_o} = \frac{\bar{Z}'_{in} - 1}{\bar{Z}'_{in} + 1}$$


In general

$$\Gamma_{in} = \frac{Z_{in} - Z_o}{Z_{in} + Z_o} = \frac{\bar{Z}'_{in} - 1}{\bar{Z}'_{in} + 1}$$

just have to know what Z to use



# Exercise

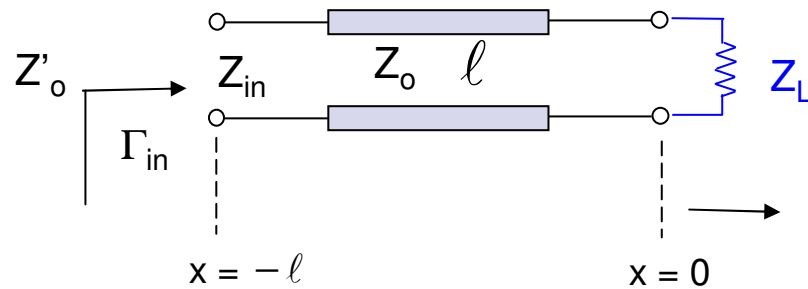

$$Z_o = 50 \Omega$$

$$Z'_o = 50 \Omega$$

$$Z_L = 100 \Omega$$

$$\text{Length} = \lambda/8$$

$$\Gamma_L = ? \quad \Gamma_{in} = ?$$

What if  $Z'_o$  is  $75 \Omega$ ?

$$\bar{Z}_{in} = \frac{\bar{Z}_L + j \tan \beta l}{1 + j \bar{Z}_L \tan \beta l}$$

$$Z_{in} = Z_o \left( \frac{Z_L + j Z_o \tan \beta l}{Z_o + j Z_L \tan \beta l} \right)$$

$$\Gamma_{in} = \frac{Z_{in} - Z'_o}{Z_{in} + Z'_o} = \frac{\bar{Z}'_{in} - 1}{\bar{Z}'_{in} + 1}$$


$$1/3$$

$$1/3 (-90^\circ) \quad \text{only change phase !?!}$$

$$0.388 (235^\circ)$$



# Voltage wave in transmission line

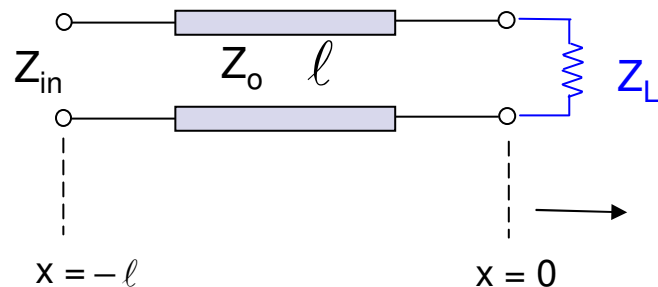

$$V(x) = V_o^+ e^{-j\beta x} + V_o^- e^{j\beta x}$$

$$V(x) = V_o^+ e^{-j\beta x} (1 + \Gamma_L e^{2j\beta x})$$

$$|V| = |V_o^+| |1 + \Gamma_L e^{2j\beta x}|$$

$$\Gamma_L \equiv \rho e^{j\theta}$$

$$|V| = V_o^+ |1 + \rho e^{j(\theta + 2\beta x)}|$$

$$|V| = V_o^+ \sqrt{(1 + \rho \cos(\theta + 2\beta x))^2 + \rho^2 \sin^2(\theta + 2\beta x)}$$

$$|V| = V_o^+ \sqrt{1 + 2\rho \cos(\theta + 2\beta x) + \rho^2}$$

$$|V| = V_o^+ \sqrt{(1 + \rho)^2 - 2\rho(1 - \cos(\theta + 2\beta x))}$$

$$|V| = V_o^+ \sqrt{(1 + \rho)^2 - 4\rho \sin^2\left(\frac{\theta + 2\beta x}{2}\right)}$$

min when sine = 1


$$V_{\min} = V_o^+ \sqrt{(1 + \rho)^2 - 4\rho} = V_o^+ (1 - \rho)$$

max when sine = 0

$$V_{\max} = V_o^+ \sqrt{(1 + \rho)^2} = V_o^+ (1 + \rho)$$



# Voltage Standing Wave

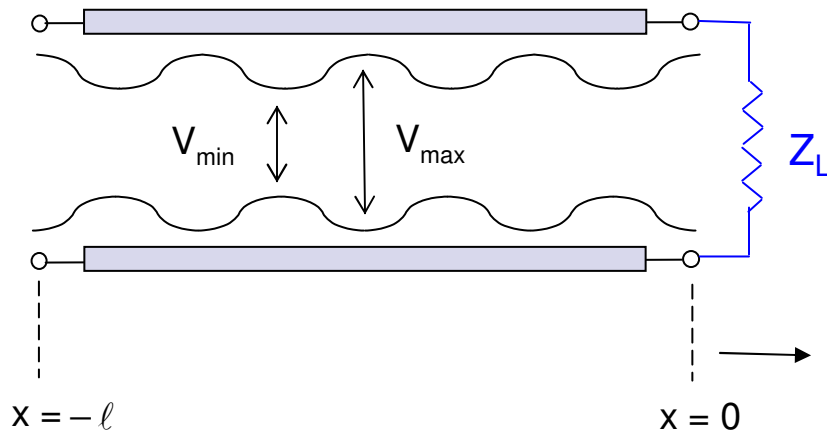

$$V(x) = V_o^+ e^{-j\beta x} + V_o^- e^{j\beta x}$$

standing wave

If  $|V_o^+| = |V_o^-|$ ,  $|\Gamma_L| \equiv \rho = \pm 1$   
perfect standing wave with nodes

$$|V| = V_o^+ \sqrt{(1 + \rho)^2 - 4\rho \sin^2\left(\frac{\theta + 2\beta x}{2}\right)}$$

$$\text{min when } \frac{\theta + 2\beta x}{2} = \pm \frac{(2n + 1)\pi}{2}$$


$$(x < 0) \quad x = -\left[\theta \mp (2n + 1)\pi\right] \frac{\lambda}{4\pi}$$

$$\text{max when } \frac{\theta + 2\beta x}{2} = \pm n\pi$$

$$x = -\left[\theta \mp 2n\pi\right] \frac{\lambda}{4\pi}$$



# VSWR (Voltage Standing Wave Ratio)

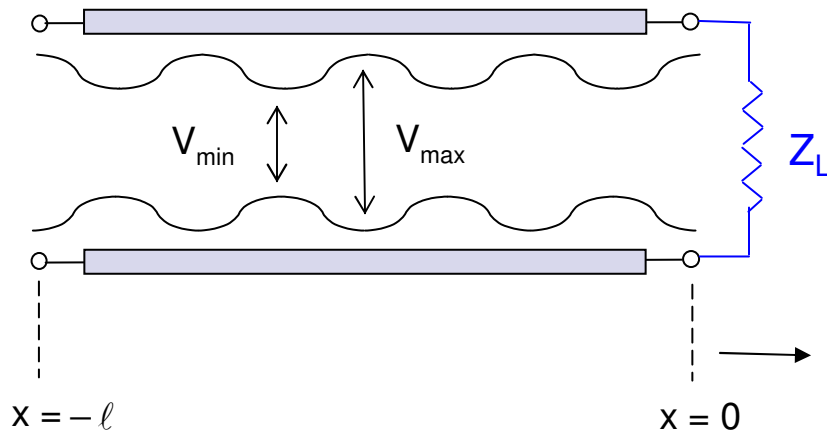

$$|V| = V_o^+ \sqrt{(1+\rho)^2 - 4\rho \sin^2\left(\frac{\theta + 2\beta x}{2}\right)}$$

$$V_{\min} = V_o^+ \sqrt{(1+\rho)^2 - 4\rho} = V_o^+ (1-\rho)$$

$$V_{\max} = V_o^+ \sqrt{(1+\rho)^2} = V_o^+ (1+\rho)$$

$$\text{VSWR} \equiv \frac{V_{\max}}{V_{\min}} = \frac{1+\rho}{1-\rho} = \frac{1+|\Gamma|}{1-|\Gamma|}$$

perfect match:  $\rho = 0$ ,  $\text{VSWR} = 1.0$


open / short:  $\rho = 1$ ,  $\text{VSWR} \rightarrow \infty$

It is an indicator on how well the load matches the line.

VSWR is the standing wave pattern INSIDE the line.

Only  $\Gamma$  at the reflected junction that counts


# Exercise

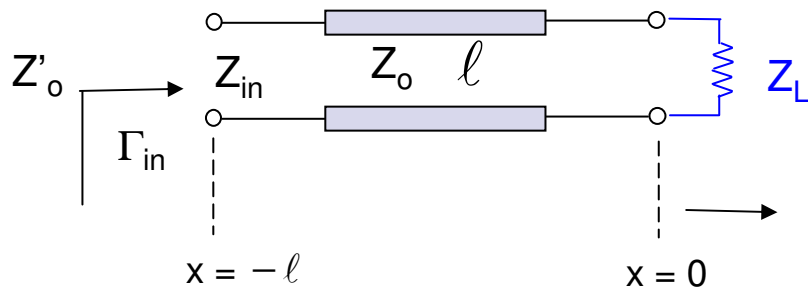

$Z_o = 50 \Omega$   
 $Z'_{in} = 75 \Omega$   
 $Z_L = 100 \Omega$   
Length =  $\lambda/8$   
VSWR = ?

$\Gamma_L = 1/3$   
VSWR = 2



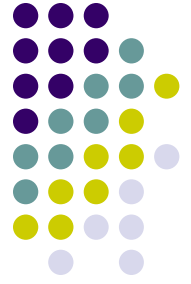

# Return Loss


$$\text{RL} \equiv -20 \log \rho \quad (\text{dB})$$

perfect match:  $\rho \rightarrow 0$ ,  $\text{VSWR} \rightarrow 1.0$ ,  $\text{RL} \rightarrow -\infty$

open / short:  $\rho = 1$ ,  $\text{VSWR} \rightarrow \infty$ ,  $\text{RL} \rightarrow 0 \text{ dB}$

$$\text{VSWR} \equiv \frac{1+\rho}{1-\rho} = \frac{1+|\Gamma|}{1-|\Gamma|} \longrightarrow \rho = |\Gamma| = \frac{\text{VSWR} - 1}{\text{VSWR} + 1}$$

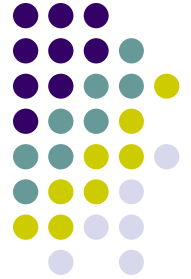Typical  $\text{VSWR} = 1.1$  to  $2$   
 $\rho = 0.048$  to  $0.33$   
 $\text{RL} = -26 \text{ dB}$  to  $-9.5 \text{ dB}$



# dB scale

power intensity ratio in log scale, not a unit !!

$$(\text{dB}) = 10 \log \left( \frac{I}{I_o} \right) = 10 \log \left( \frac{P}{P_o} \right) = 20 \log \left( \frac{V}{V_o} \right)$$

↑
↑
↑  
 sound intensity      power      voltage

> 0 gain  
< 0 loss

- 10 log(2) ≈ 3,      3 dB = double
- 10 log(1/2) ≈ -3,      -3 dB = half
- 10 log(10) = 10,      10 dB = 10x
- 10 log(100) = 20,      20 dB = 100x
- 10 log(0.1) = -10,      -10 dB = 1/10

What is 6 dB?   -9 dB?   7 dB?   -44 dB?

4x      1/8      5x      4 x 10<sup>-5</sup>



# dBm & dBW

$$\text{dBW} \equiv 10 \log \left( \frac{P}{1\text{W}} \right)$$

$$\text{dBm} \equiv 10 \log \left( \frac{P}{1\text{mW}} \right)$$


become real units

0 dBm = 1 mW  
30 dBW = 1 kW  
-30 dBm = 1  $\mu$ W

What is 40 dBW? -7 dBm? -26 dBm? 21 dBm?  
10 kW      0.2 mW      4  $\mu$ W      1/8 W



# Example

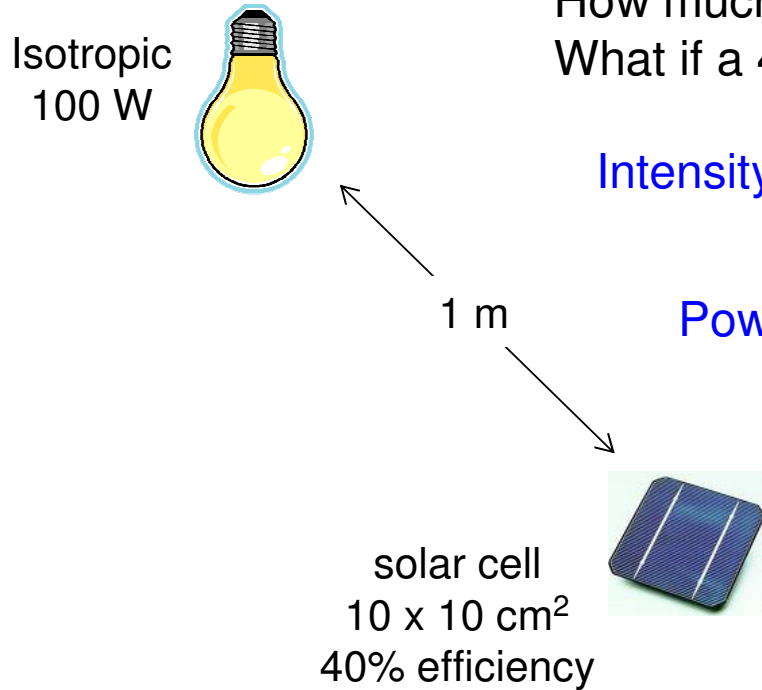

How much electricity generated by the solar cell?  
What if a 40 W bulb is used? 200 W bulb?

$$\text{Intensity} = \text{power/area} = \frac{100}{4\pi R^2} = \frac{100}{4\pi(1)^2} = 7.96 \frac{\text{W}}{\text{m}^2}$$

Power generated in solar cell

$$= \left(7.96 \frac{\text{W}}{\text{m}^2}\right) (100\text{cm}^2) (40\%) = 31.8\text{mW}$$

$$\text{In terms of dB} = 10\log\left(\frac{0.0318\text{W}}{100\text{W}}\right) = \boxed{-35\text{dB}}$$

system gain

$$40 \text{ W bulb? } -35 = 10\log\left(\frac{P}{40}\right)$$

Power of electricity generated = 12.6 mW

$$200 \text{ W bulb? } -35 = 10\log\left(\frac{P}{200}\right)$$


Power of electricity generated = 63.2 mW




# Stub

Transmission line connecting nowhere(?)


- Open stub

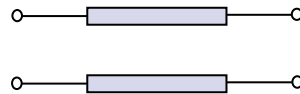


- Short stub

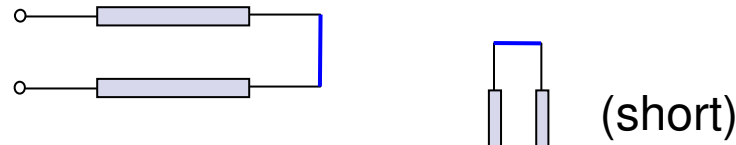


- Series stub


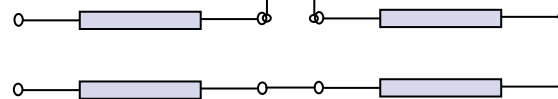


- Shunt stub

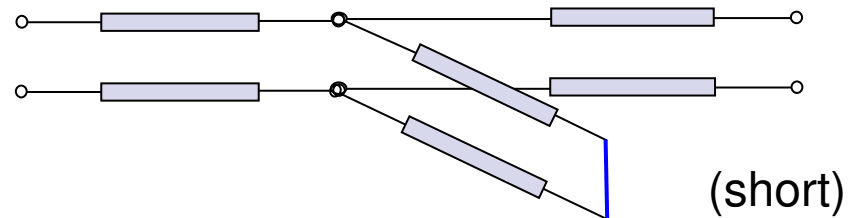

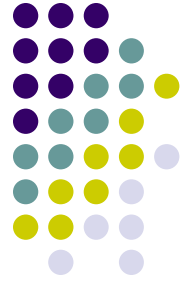


# Open Shunt Stub

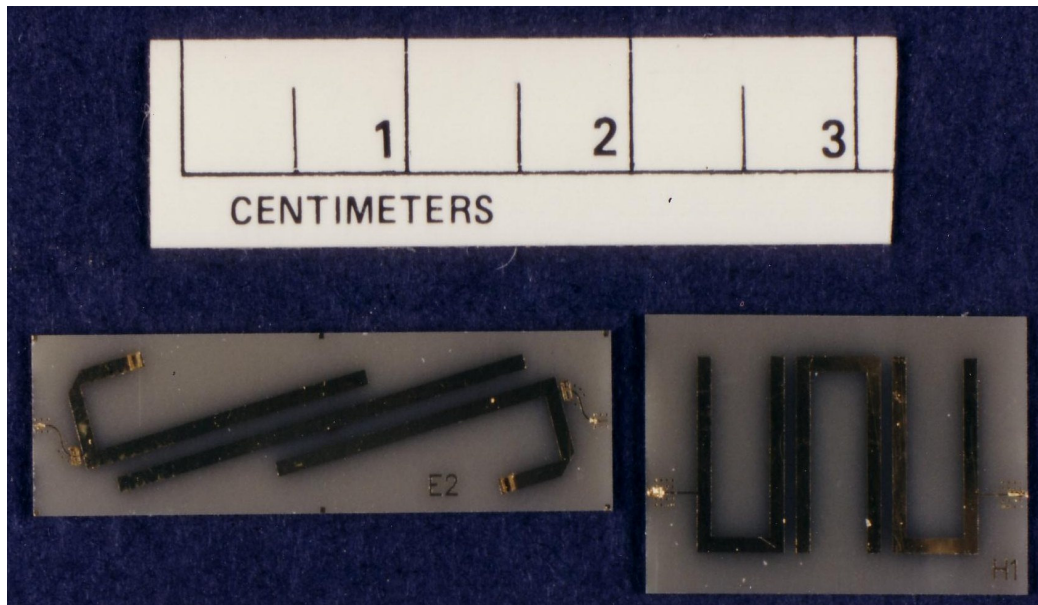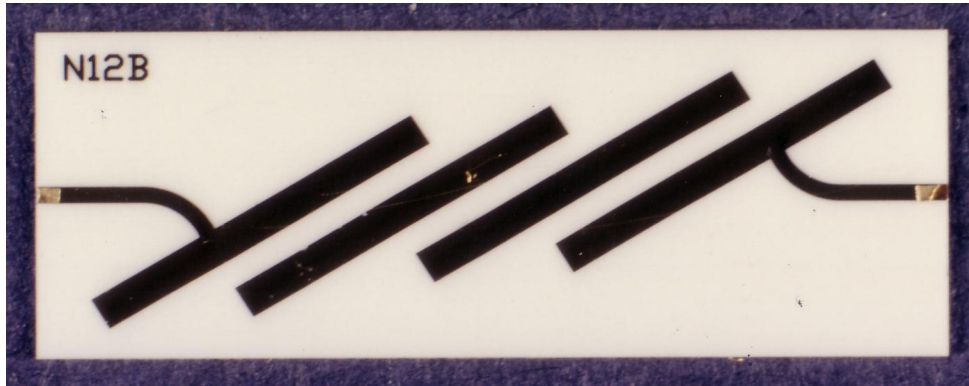

L-Band





# Short Shunt Stub

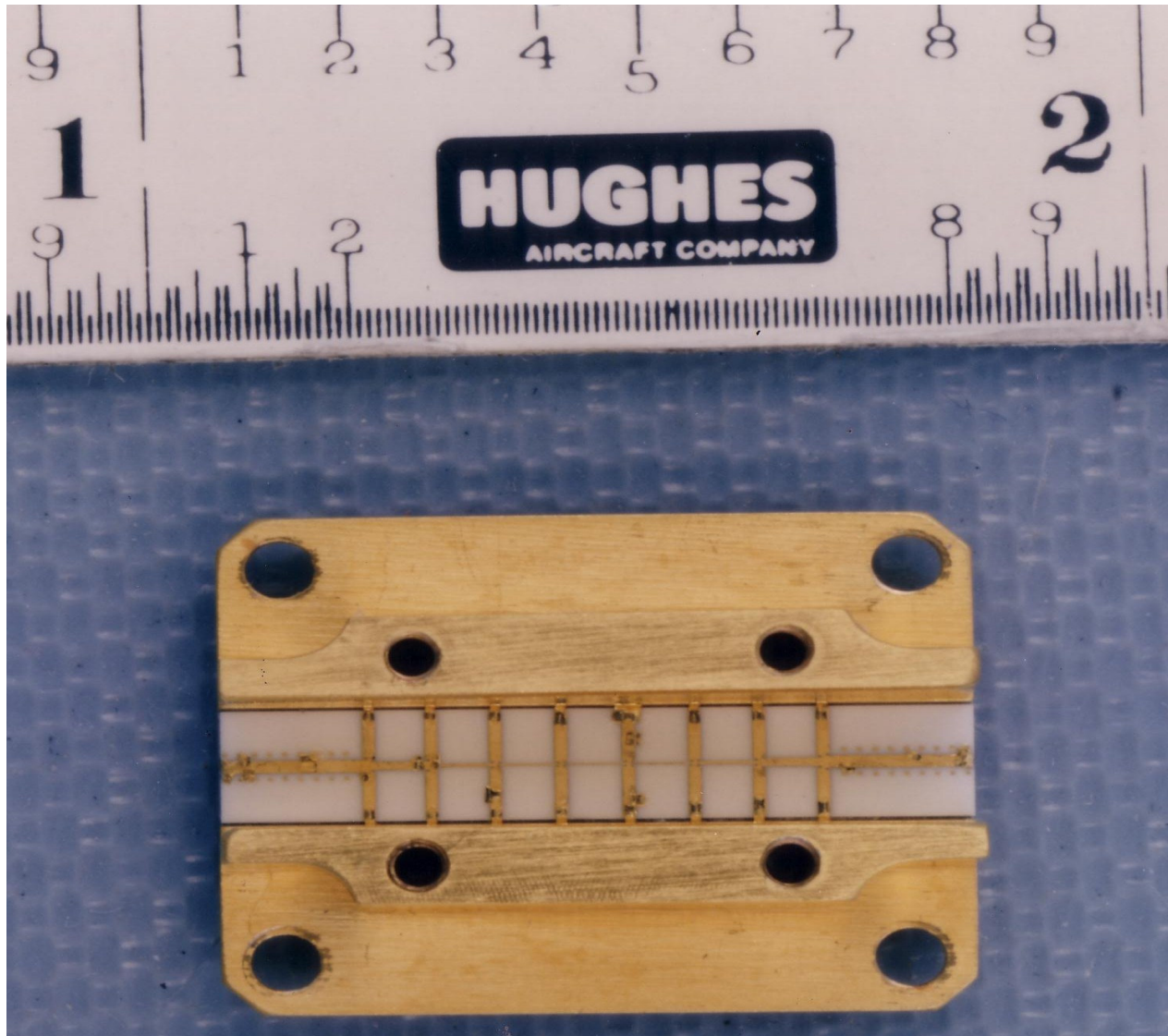

20 GHz  
Interdigital  
Filter



# Radial Stub

18 GHz  
Rat Race


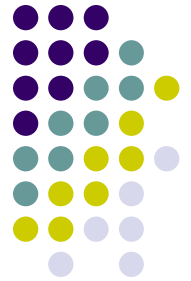
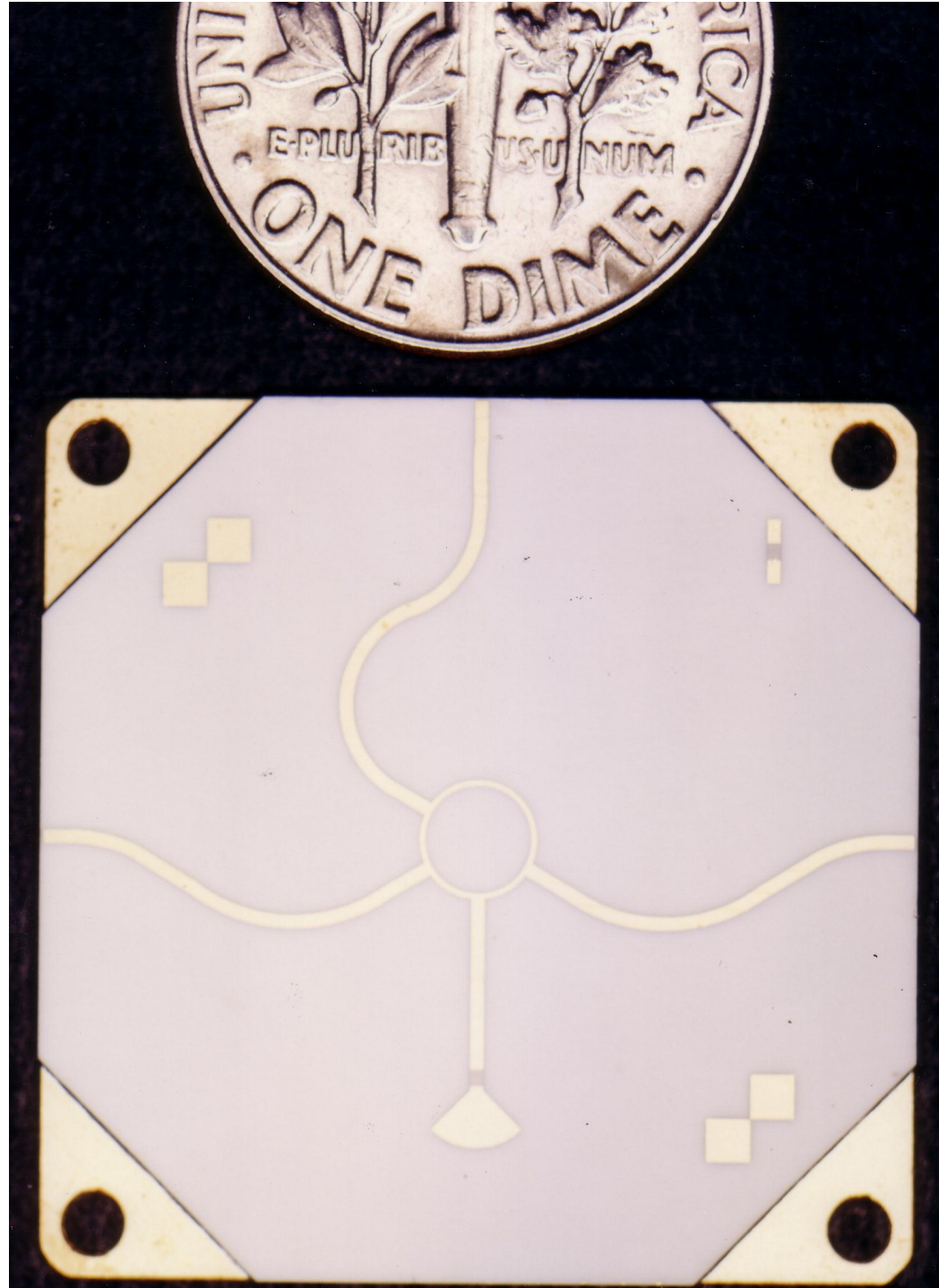


# ■ 180° 하이브리드 커플러

- 평면회로: Rat-race coupler

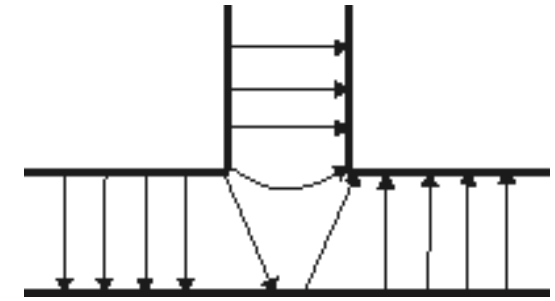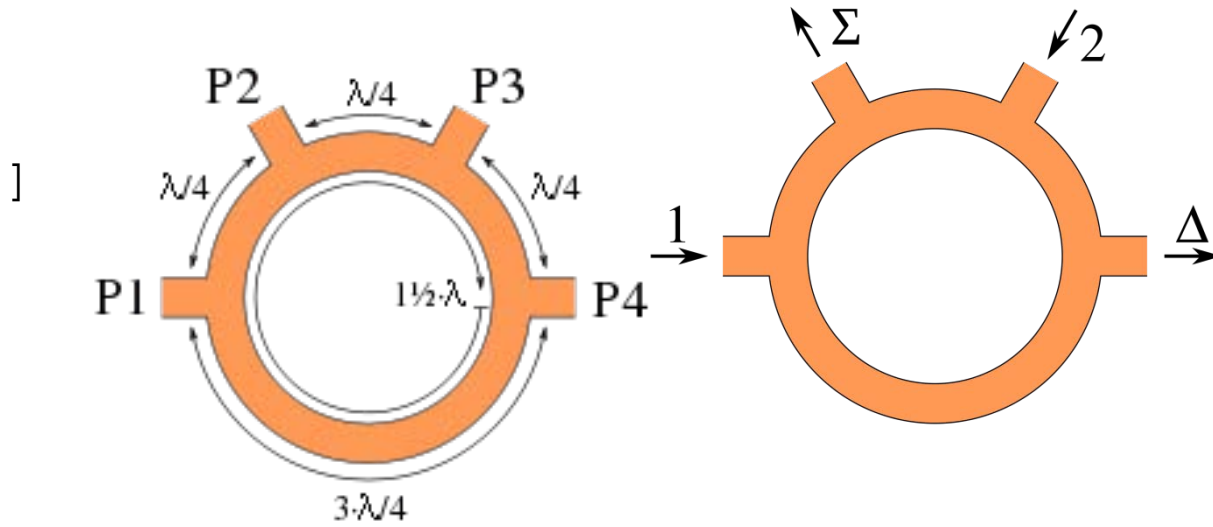


- 사각 도파관: Ring Hybrid Coupler,

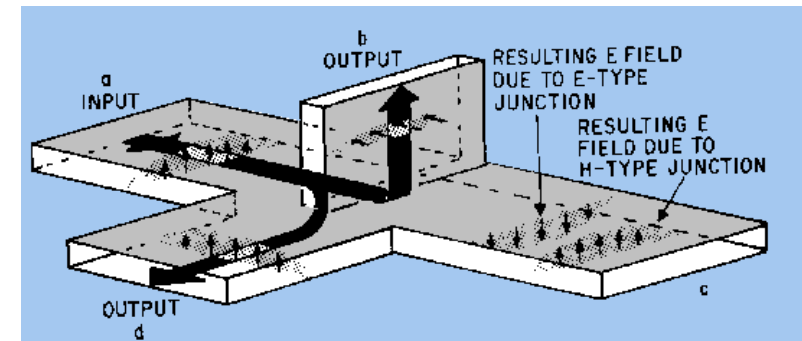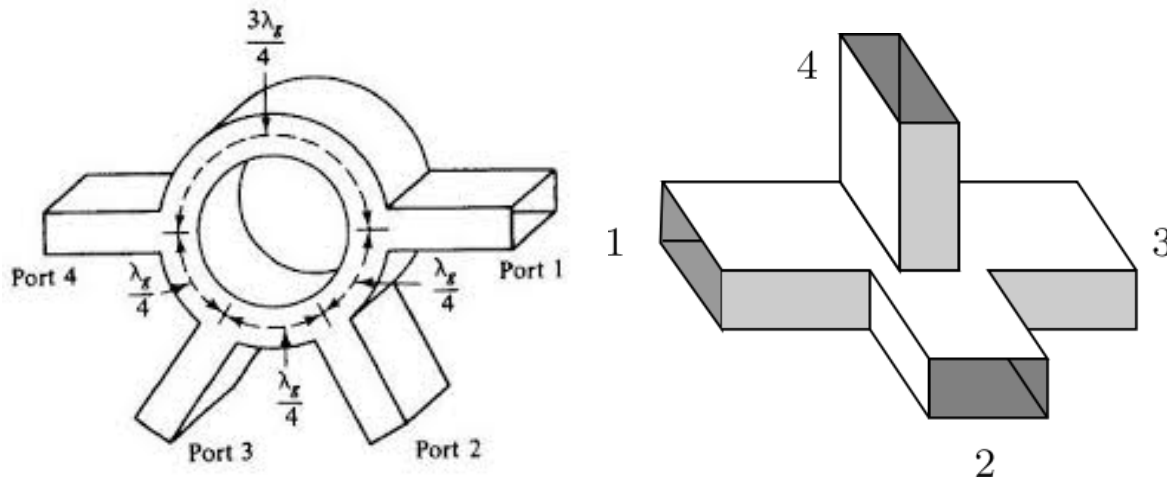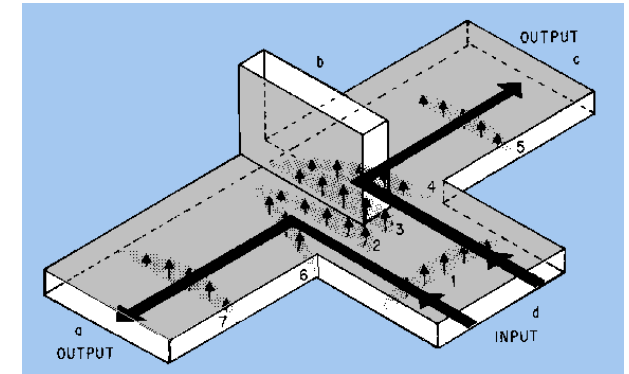





# Tuning stub (open)

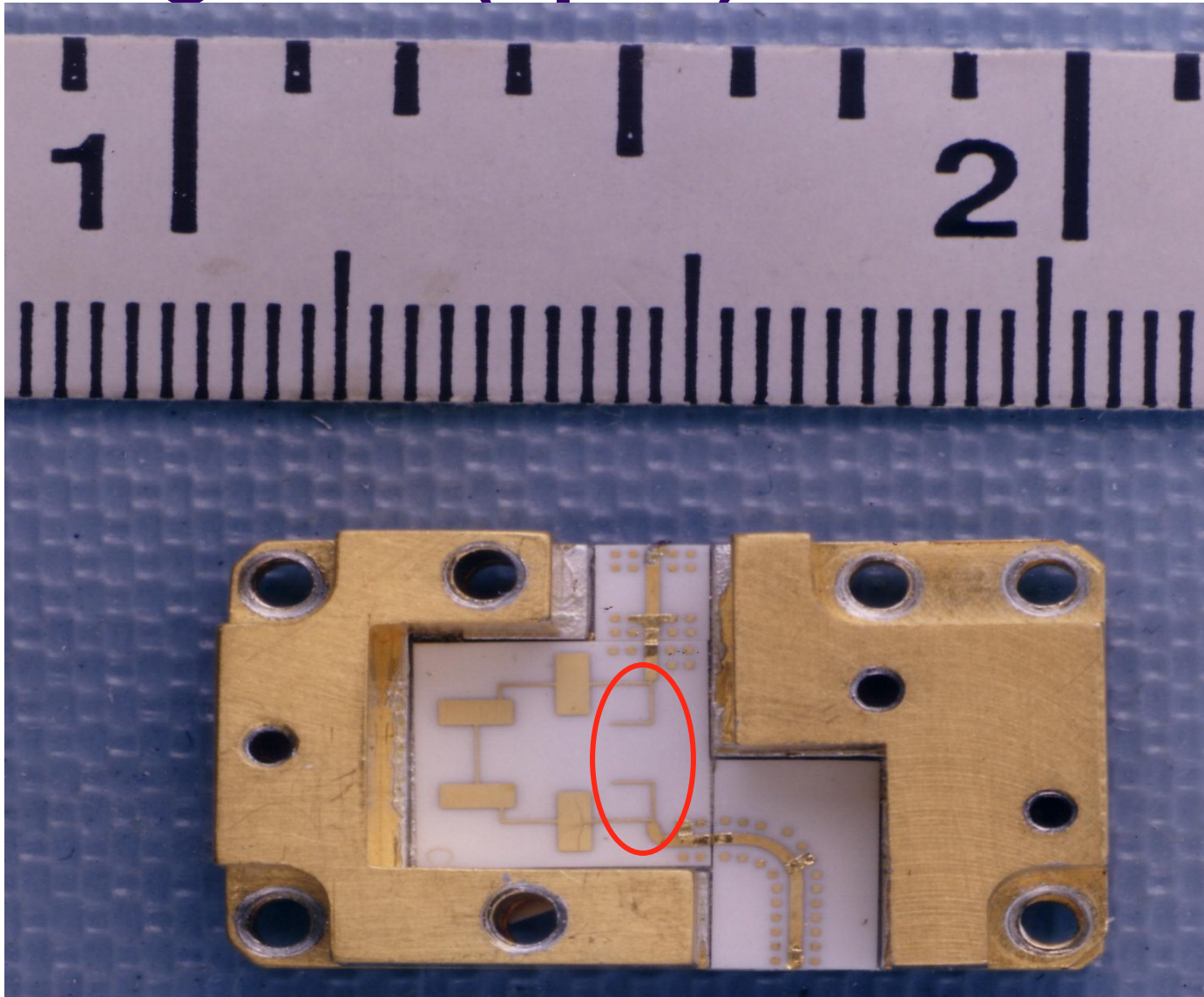




# Short Stub

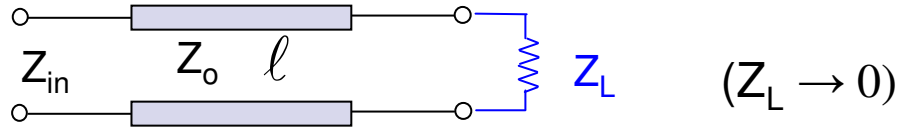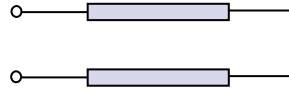

$$\bar{Z}_{in} = \frac{\bar{Z}_L + j \tan \beta l}{1 + j \bar{Z}_L \tan \beta l}$$

$$\bar{Z}_{sh} = j \tan \beta l$$
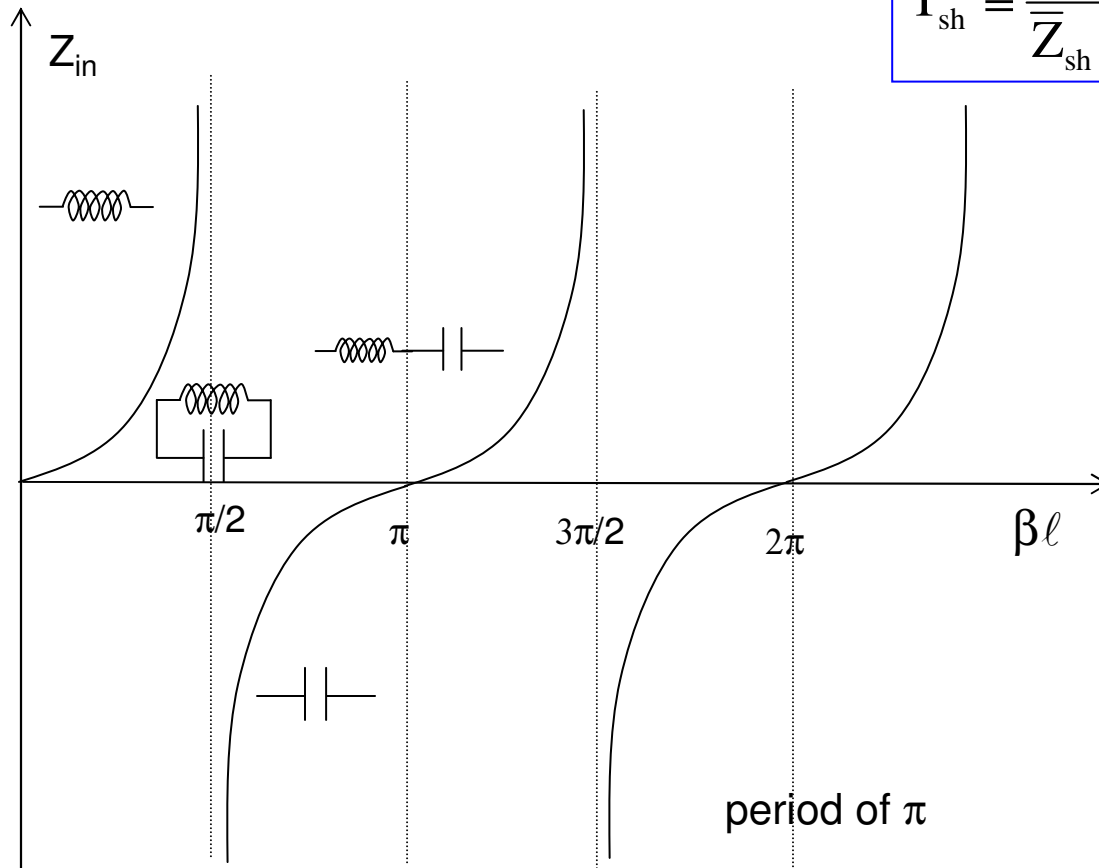
$$\bar{Y}_{sh} \equiv \frac{1}{\bar{Z}_{sh}} = -j \cot \beta l$$



$$Z_{coil} = j\omega L$$



$$Z_{cap} = -j/\omega C$$

$$Z_{sres} = j\omega L \left( 1 - \frac{1}{\omega^2 LC} \right)$$

$$Z_{pres} = \frac{1}{j\omega C \left( 1 - \frac{1}{\omega^2 LC} \right)}$$



# Open Stub

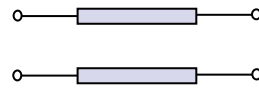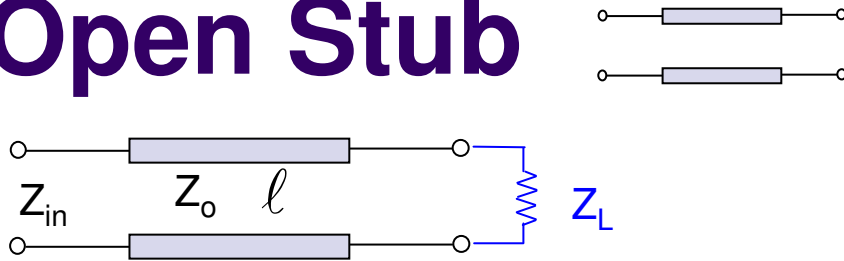


$$\bar{Z}_{in} = \frac{\bar{Z}_L + j \tan \beta l}{1 + j \bar{Z}_L \tan \beta l}$$

$(Z_L \rightarrow \infty)$

$$\bar{Z}_{op} = -j \cot \beta l$$

$$\bar{Y}_{op} = j \tan \beta l$$

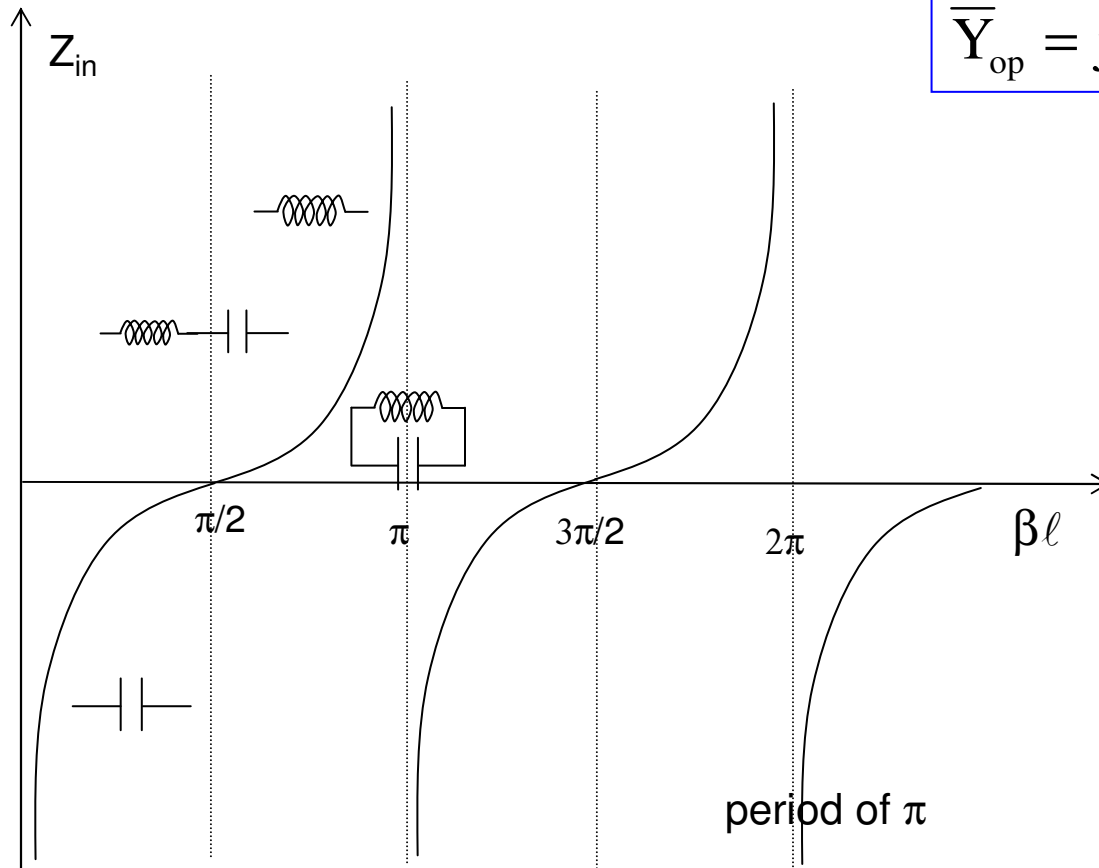

$$Z_{cap} = -j/\omega C$$


$$Z_{coil} = j\omega L$$

$$Z_{sres} = j\omega L \left( 1 - \frac{1}{\omega^2 LC} \right)$$

$$Z_{pres} = \frac{1}{j\omega C \left( 1 - \frac{1}{\omega^2 LC} \right)}$$




# Exercise

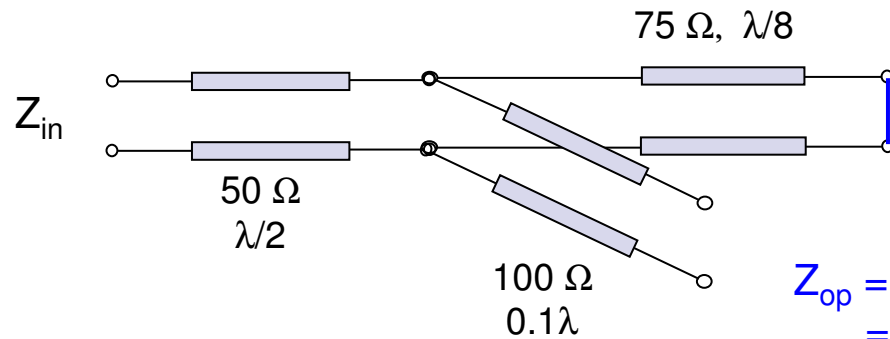

Find  $Z_{in}$  &  $\Gamma_{in}$ .


$$Z_{sh} = j Z_o \tan(\beta l) \\ = j 75 \tan(45^\circ) = j 75 \Omega$$
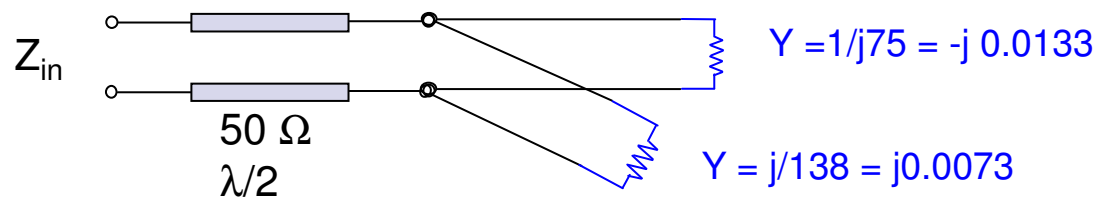
$$Z_{op} = -j Z_o \cot(\beta l) \\ = -j 100 \cot(36^\circ) = -j 138 \Omega$$



$$Y = 1/j75 = -j 0.0133$$

$$Y = j/138 = j0.0073$$

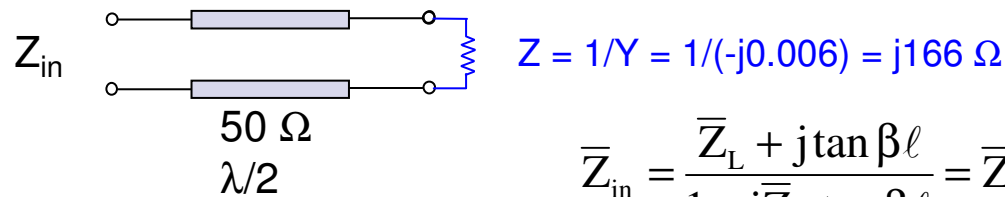

$$Z = 1/Y = 1/(-j0.006) = j166 \Omega$$


$$\bar{Z}_{in} = \frac{\bar{Z}_L + j \tan \beta \ell}{1 + j \bar{Z}_L \tan \beta \ell} = \bar{Z}_L$$

$$Z_{in} = j 166 \Omega$$

$$\Gamma_{in} = \frac{Z_{in} - Z_o}{Z_{in} + Z_o} = \frac{j166 - 50}{j166 + 50} = 1 \angle (107^\circ - 73^\circ) = 1 \angle 34^\circ$$



# Transmission line with loss

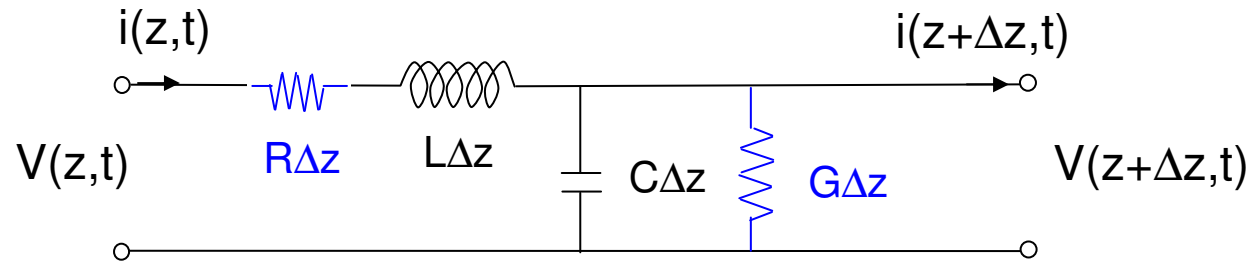

Kirchhoff's law:

$$V(z,t) - (L\Delta z) \frac{\partial i(z,t)}{\partial t} - (R\Delta z)i(z,t) = V(z+\Delta z,t)$$

$$-L \frac{\partial i(z,t)}{\partial t} - Ri(z,t) = \frac{\partial V(z,t)}{\partial z}$$


$$-(R + j\omega L)i(z,t) = \frac{\partial V(z,t)}{\partial z}$$

Junction rule:

$$i(z+\Delta z,t) - i(z,t) = -(C\Delta z) \frac{\partial V(z,t)}{\partial t} - (G\Delta z)V(z,t)$$

$$-C \frac{\partial V(z,t)}{\partial t} - GV(z,t) = \frac{\partial i(z,t)}{\partial z}$$
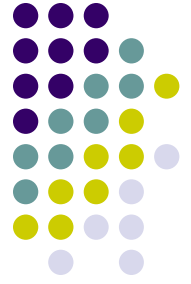
$$-(G + j\omega C)V(z,t) = \frac{\partial i(z,t)}{\partial z}$$



# Propagation Constants

$$-(G + j\omega C)V = \frac{\partial I}{\partial z}$$

$$-(R + j\omega L)I = \frac{\partial V}{\partial z}$$

$$\frac{\partial^2 V}{\partial z^2} = -(R + j\omega L) \frac{\partial I}{\partial z}$$

$$\frac{\partial^2 V}{\partial z^2} = (R + j\omega L)(G + j\omega C)V$$

$$V(z) = V_o^+ e^{-\gamma z} + V_o^- e^{\gamma z}$$

$$\gamma^2 = (R + j\omega L)(G + j\omega C)$$

$$V(z) = V_o^+ e^{-\gamma z} + V_o^- e^{\gamma z}$$

$$I(z) = I_o^+ e^{-\gamma z} - I_o^- e^{\gamma z}$$

$$\frac{\partial V}{\partial z} = -(R + j\omega L)I$$

$$-\gamma V_o^+ e^{-\gamma z} + \gamma V_o^- e^{\gamma z} = -(R + j\omega L)(I_o^+ e^{-\gamma z} - I_o^- e^{\gamma z})$$

$$\gamma V_o^\pm = (R + j\omega L)I_o^\pm$$

$$V_o^\pm = \frac{(R + j\omega L)}{\gamma} I_o^\pm \equiv I_o^\pm Z_o$$

$$Z_o = \frac{(R + j\omega L)}{\gamma} = \frac{(R + j\omega L)}{\sqrt{(R + j\omega L)(G + j\omega C)}}$$

$$Z_o = \sqrt{\frac{(R + j\omega L)}{(G + j\omega C)}}$$



# Lossless limit

$$R \rightarrow 0, \quad G \rightarrow 0$$

$$Z_o = \sqrt{\frac{(R + j\omega L)}{(G + j\omega C)}} \rightarrow \sqrt{\frac{L}{C}}$$

$$\gamma^2 = (R + j\omega L)(G + j\omega C) \rightarrow -\omega^2 LC$$


$$\gamma = \pm j\omega\sqrt{LC}$$

$$v = f\lambda = \frac{\omega}{\beta} = \frac{1}{\sqrt{LC}}$$


$$\gamma = \pm j\beta$$

$$\begin{pmatrix} V(z) \\ I(z) \end{pmatrix} = \begin{pmatrix} V_o^+ \\ I_o^+ \end{pmatrix} e^{-\gamma z} + \begin{pmatrix} V_o^- \\ -I_o^- \end{pmatrix} e^{\gamma z}$$
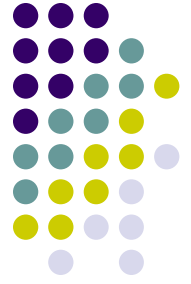
$$\begin{pmatrix} V(z) \\ I(z) \end{pmatrix} = \begin{pmatrix} V_o^+ \\ I_o^+ \end{pmatrix} e^{-j\beta z} + \begin{pmatrix} V_o^- \\ -I_o^- \end{pmatrix} e^{j\beta z}$$



# Transmission Line Equation

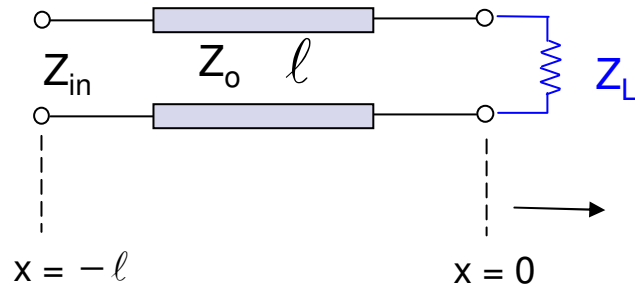

$$Z_{in} = Z_o \left( \frac{Z_L + Z_o \tanh \gamma l}{Z_o + Z_L \tanh \gamma l} \right)$$

$$\bar{Z}_{in} = \frac{\bar{Z}_L + \tanh \gamma l}{1 + \bar{Z}_L \tanh \gamma l}$$

which reduce to ideal transmission line equation when  $\gamma = j\beta$ .

$$\tanh(jx) = j \tan(x)$$



# Low Loss Line

$$\gamma^2 = (R + j\omega L)(G + j\omega C)$$

$$\gamma^2 = (j\omega)^2 LC \left( 1 + \frac{R}{j\omega L} \right) \left( 1 + \frac{G}{j\omega C} \right)$$

$$\gamma^2 \approx (j\omega)^2 LC \left( 1 + \frac{R}{j\omega L} + \frac{G}{j\omega C} \right)$$

$$\gamma \approx j\omega\sqrt{LC} \left( 1 + \frac{1}{2} \left[ \frac{R}{j\omega L} + \frac{G}{j\omega C} \right] \right)$$

$$\gamma \approx \frac{1}{2} \left( R\sqrt{\frac{C}{L}} + G\sqrt{\frac{L}{C}} \right) + j\omega\sqrt{LC}$$

$$\gamma = \alpha + j\beta$$

phase constant


attenuation constant

propagation constant

$$Z_o = \sqrt{\frac{(R + j\omega L)}{(G + j\omega C)}} \approx \sqrt{\frac{L}{C}}$$

$$\alpha \approx \frac{1}{2} \left( R\sqrt{\frac{C}{L}} + G\sqrt{\frac{L}{C}} \right) = \frac{1}{2} \left( \frac{R}{Z_o} + GZ_o \right)$$
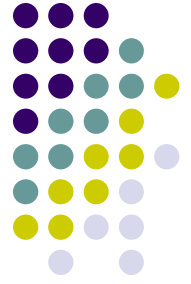
$$\beta \approx \omega\sqrt{LC} \rightarrow v \approx \frac{1}{\sqrt{LC}} \quad \text{distortionless}$$



# Distortionless Line

$$\frac{R}{L} = \frac{G}{C}$$

$$\gamma^2 = (R + j\omega L)(G + j\omega C)$$

$$\gamma^2 = (j\omega)^2 LC \left(1 + \frac{R}{j\omega L}\right) \left(1 + \frac{G}{j\omega C}\right)$$

$$\gamma^2 = (j\omega)^2 LC \left(1 + \frac{R}{j\omega L}\right)^2$$

$$\gamma = j\omega\sqrt{LC} \left(1 + \frac{R}{j\omega L}\right)$$

$$\gamma = R\sqrt{\frac{C}{L}} + j\omega\sqrt{LC}$$

$$\alpha = R\sqrt{\frac{L}{C}}$$

$$\beta = \omega\sqrt{LC} \rightarrow v \approx \frac{1}{\sqrt{LC}}$$

frequency independence



# Attenuation

$$V(z) = V_o^+ e^{-\gamma z} \quad \text{forward voltage wave}$$

$$V(z) = V_o^+ e^{-\alpha z} e^{-j\beta z} \quad \text{attenuation \& propagation}$$


$$\left| \frac{V(z)}{V(0)} \right| = e^{-\alpha z}$$

$$20 \log \left| \frac{V(z)}{V(0)} \right| = 20 \log(e^{-\alpha z}) \equiv -A(z) \equiv -\alpha_{\text{dB}} z$$


$$e^{-\alpha z} = 10^{-(\alpha_{\text{dB}} / 20) z}$$

$$e^{-\alpha} = 10^{-\alpha_{\text{dB}} / 20}$$

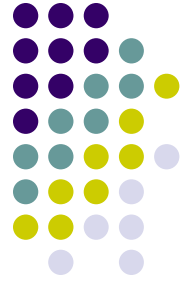A = attenuation in dB  
 $\alpha_{\text{dB}}$  = atten. dB/m  
 $\alpha$  in 1/m or nepers/m



# Example

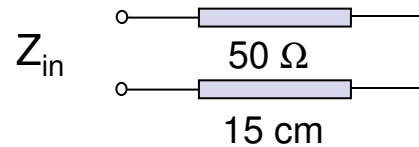

$$\alpha = 0.04 \text{ dB/m}$$

$$Z_{in} = ? \text{ at 3 GHz}$$

$$A = (0.04 \text{ dB/m})(0.15\text{m}) = 0.006 \text{ dB} \quad (\text{very low loss})$$

$$e^{-\alpha} = 10^{-\alpha_{\text{dB}}/20}$$

$$\alpha = \ln(10^{-0.04/20})$$

$$\beta = \frac{\omega}{v} = \frac{2\pi(3 \cdot 10^9)}{3 \cdot 10^8} = 20\pi$$

$$0.04 \text{ dB} = 8.868 \alpha$$

$$\alpha = 0.0046 \text{ /m (or Np / m)}$$

$$\beta = 62.8 \text{ /m (or rad / m), } 15 \text{ cm} = 3\lambda/2 !!$$

$$Z_{in} = Z_o \left( \frac{Z_L + Z_o \tanh \gamma l}{Z_o + Z_L \tanh \gamma l} \right)$$

$$Z_{sh} = Z_o \tanh \gamma l = Z_o \tanh(\alpha l + j\beta l)$$

$$Z_{sh} = Z_o \left( \frac{\tanh(\alpha l) + j \tan(\beta l)}{1 + j \tanh(\alpha l) \tan(\beta l)} \right)$$

$$Z_{sh} = 50 \left( \frac{\tanh(0.00069) + j \tan(3\pi)}{1 + j \tanh(0.00069) \tan(3\pi)} \right)$$


$$Z_{sh} = 50 \left( \frac{0.00069 + 0}{1 + 0} \right)$$

$$Z_{sh} = 0.0345 \text{ ohms}$$

$$\tanh(x) \approx x \quad \text{for small } x$$



# Example

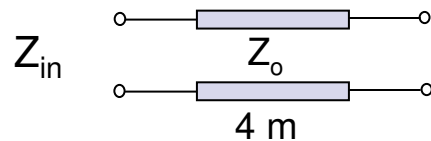

$$Z_{\text{open}} = 250 \angle -50^\circ \Omega$$

$$Z_{\text{short}} = 360 \angle 20^\circ \Omega$$

What is  $Z_o$ ,  $\alpha$ ,  $\beta$ ? Also  $R$ ,  $L$ ,  $G$ ,  $C$  =?

complex  $Z$  short / open  $\rightarrow$  lossy !!

$$Z_{\text{sh}} = Z_o \tanh \gamma \ell$$


$$Z_{\text{op}} = \frac{Z_o}{\tanh \gamma \ell}$$

$$Z_o = \sqrt{Z_{\text{op}} Z_{\text{sh}}} = \sqrt{250 \cdot 360 \angle -30^\circ} = 300 \angle -15^\circ = (290 - j78) \Omega$$


$$\tanh \gamma \ell = \sqrt{\frac{Z_{\text{sh}}}{Z_{\text{op}}}} = \sqrt{\frac{360}{250} \angle 70^\circ} = 1.2 \angle 35^\circ = 0.983 + j0.688$$

$$\tanh \gamma \ell = \tanh(\alpha \ell + j\beta \ell) = \frac{\tanh \alpha \ell + j \tan \beta \ell}{1 + j \tanh \alpha \ell \tan \beta \ell} = 0.983 + j0.688$$
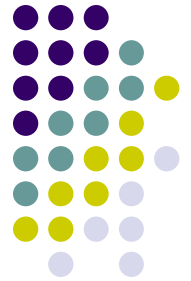
$$\ell = 4\text{m}, \quad \alpha = 0.139 \text{ Np/m}, \quad \beta = 0.235 \text{ rad/m}$$



# Example - continue

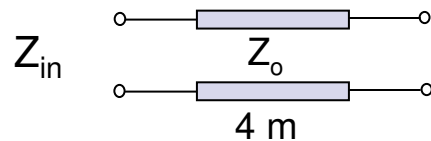

What is  $Z_0$ ,  $\alpha$ ,  $\beta$ ? Also  $R$ ,  $L$ ,  $G$ ,  $C$  =?

$$Z_0 = \sqrt{\frac{R + j\omega L}{G + j\omega C}}$$

$$\gamma = \sqrt{(R + j\omega L)(G + j\omega C)}$$

$$\gamma Z_0 = R + j\omega L$$

$$\frac{\gamma}{Z_0} = G + j\omega C$$

$$Z_0 = 290 - j78$$

$$\gamma = \alpha + j\beta = 0.139 + j0.235$$



$$\omega = \beta v = (0.235)(3 \cdot 10^8) = 0.705 \cdot 10^8$$

4 equations, 4 unknowns

$$R = 58.6 \Omega/\text{m}, \quad L = 0.812 \mu\text{H}/\text{m}$$

$$G = 0.246 \text{ 1}/\Omega\text{m}, \quad C = 12.4 \text{ pF}/\text{m}$$

# Field Equivalence

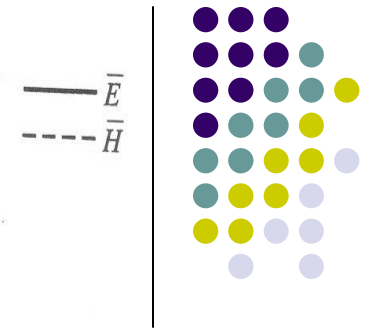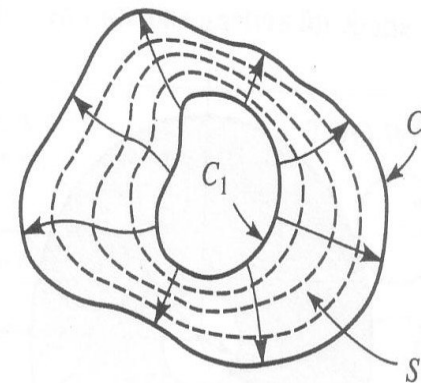

e.g. TEM - coaxial

time average

$$W_m = \frac{1}{4} L |I_o|^2$$

$$W_e = \frac{1}{4} C |V_o|^2$$

$$P_c = \frac{1}{2} R |I_o|^2$$

$$P_d = \frac{1}{2} G |V_o|^2$$

$$L = \frac{\mu}{|I_o|^2} \int_S |\vec{H}|^2 ds$$

$$C = \frac{\epsilon}{|V_o|^2} \int_S |\vec{E}|^2 ds$$


$$R = \frac{R_s}{|I_o|^2} \int_{C_1+C_2} |\vec{H}|^2 dl$$

$$G = \frac{\omega \epsilon''}{|V_o|^2} \int_S |\vec{E}|^2 ds$$

$$R_s = 1/\sigma \delta_s$$

$$\begin{aligned} \epsilon &= \epsilon' - \epsilon'' \\ &= \epsilon' (1 - j \tan \delta) \end{aligned}$$

# Coaxial Cable - L

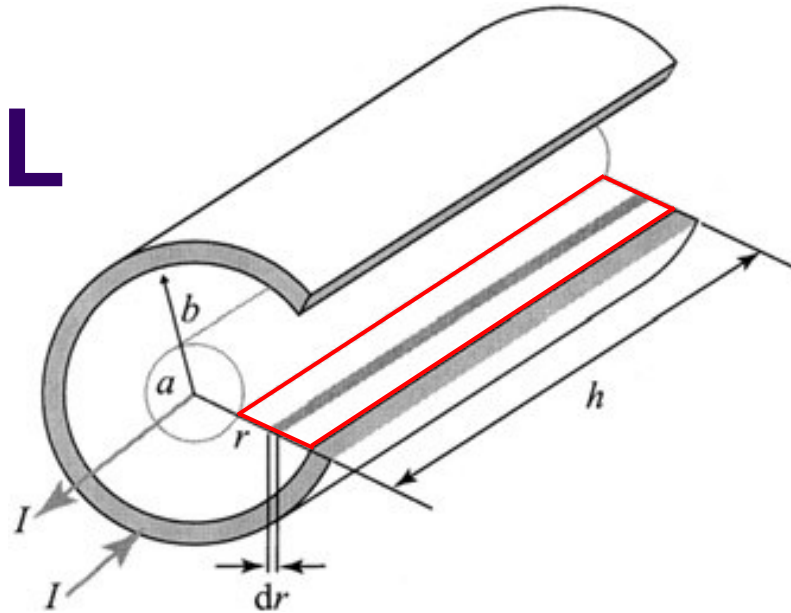

$$\oint \vec{H} \cdot d\vec{\ell} = I_f$$

$$\vec{H} = \frac{\vec{B}}{\mu} = \frac{I}{2\pi r} \hat{\phi}$$

$$\Phi = \int \vec{B} \cdot d\vec{a} = \int_a^b \frac{\mu I}{2\pi r} \hat{\phi} \cdot \hat{\phi} h dr$$

$$\Phi = \frac{\mu I h}{2\pi} \ln\left(\frac{b}{a}\right)$$


$$L' = \frac{\Phi}{I} = \frac{\mu h}{2\pi} \ln\left(\frac{b}{a}\right)$$

$$L \equiv \frac{L'}{h} = \frac{\mu}{2\pi} \ln\left(\frac{b}{a}\right)$$

$$L = \frac{\mu}{|I_o|^2} \int_s |\vec{H}|^2 ds$$

$$L = \frac{\mu}{|I_o|^2} \int_a^b \left(\frac{I_o}{2\pi r}\right)^2 2\pi r dr$$
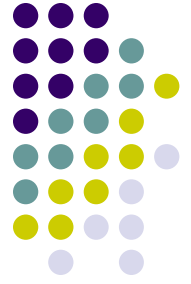
$$L = \frac{\mu}{2\pi} \int_a^b \frac{dr}{r} = \frac{\mu}{2\pi} \ln\left(\frac{b}{a}\right)$$



# Coaxial Cable - C

$$\oint \vec{D} \cdot d\vec{s} = Q_f$$


$$\epsilon E(2\pi r h) = Q$$

$$E = \frac{Q}{2\pi h \epsilon r} \hat{r}$$

$$V = -\int_b^a \vec{E} \cdot d\vec{r} = \frac{Q}{2\pi h \epsilon} \ln\left(\frac{b}{a}\right)$$

$$C' = \frac{Q}{V} = \frac{2\pi h \epsilon}{\ln(b/a)}$$
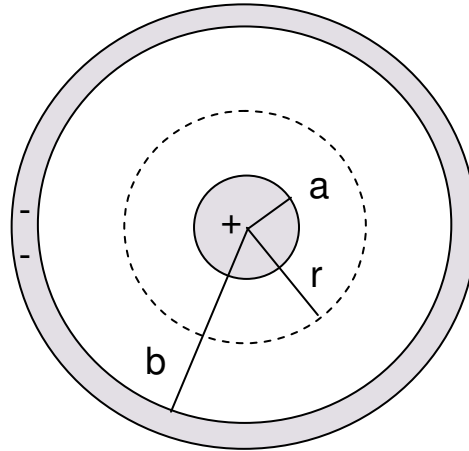
$$C \equiv \frac{C'}{h} = \frac{2\pi \epsilon}{\ln(b/a)}$$



$$C = \frac{\epsilon}{|V_o|^2} \int_S |\vec{E}|^2 ds$$

$$C = \frac{\epsilon}{|V_o|^2} \int_a^b \left( \frac{Q}{2\pi h \epsilon r} \right)^2 2\pi r dr$$

$$C = \frac{\epsilon}{|V_o|^2} \int_a^b \left( \frac{V_o / \ln(b/a)}{r} \right)^2 2\pi r dr$$

$$C = \frac{2\pi \epsilon}{[\ln(b/a)]^2} \int_a^b \frac{dr}{r}$$

$$C = \frac{2\pi \epsilon}{\ln(b/a)}$$




# Coaxial Cable – R & G

$$R = \frac{R_s}{|I_o|^2} \int_{C_1+C_2} |\vec{H}|^2 d\ell$$

$$R = \frac{R_s}{|I_o|^2} \left[ \int_{r=a} \left( \frac{I_o}{2\pi a} \right)^2 a d\phi + \int_{r=b} \left( \frac{I_o}{2\pi b} \right)^2 b d\phi \right]$$
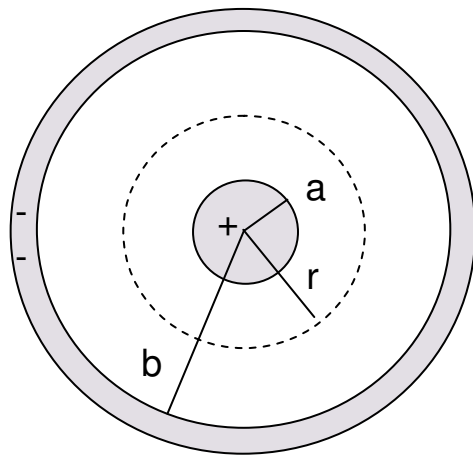
$$R = \frac{R_s}{2\pi} \left( \frac{1}{a} + \frac{1}{b} \right)$$




$$G = \frac{\omega \epsilon''}{|V_o|^2} \int_S |\vec{E}|^2 ds$$

$$G = \frac{\omega \epsilon''}{|V_o|^2} \int_a^b \left( \frac{Q}{2\pi h \epsilon r} \right)^2 2\pi r dr$$


$$G = \frac{\omega \epsilon''}{|V_o|^2} \int_a^b \left( \frac{V_o / \ln(b/a)}{r} \right)^2 2\pi r dr$$

$$G = \frac{2\pi \omega \epsilon''}{[\ln(b/a)]^2} \int_a^b \frac{dr}{r}$$
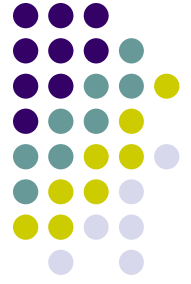
$$G = \frac{2\pi \omega \epsilon''}{\ln(b/a)}$$



# Summary - Coaxial Cable

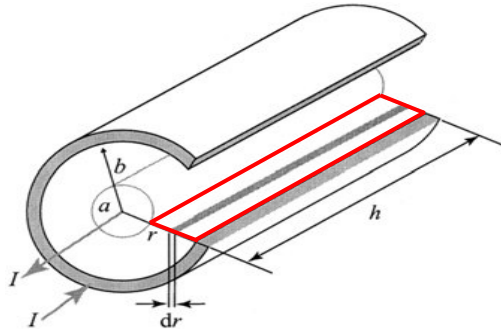

$$L = \frac{\mu}{2\pi} \ln\left(\frac{b}{a}\right)$$

$$C = \frac{2\pi\epsilon'}{\ln(b/a)}$$

$$R = \frac{R_s}{2\pi} \left( \frac{1}{a} + \frac{1}{b} \right)$$

$$G = \frac{2\pi\omega\epsilon''}{\ln(b/a)}$$


Low loss coaxial

$$Z_o \approx \sqrt{\frac{L}{C}} = \sqrt{\frac{\mu}{2\pi} \ln\left(\frac{b}{a}\right) \cdot \frac{\ln(b/a)}{2\pi\epsilon}}$$

$$Z_o = \frac{\eta_o}{2\pi\sqrt{\epsilon_r}} \ln\left(\frac{b}{a}\right) \quad (\eta_o = 377 \Omega)$$

$$v \approx \frac{1}{\sqrt{LC}} = \sqrt{\frac{2\pi}{\mu \ln(b/a)} \cdot \frac{\ln(b/a)}{2\pi\epsilon'}}$$
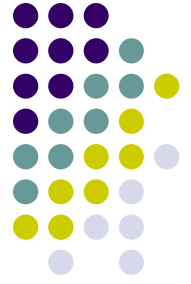
$$v = \frac{1}{\sqrt{\mu\epsilon}} \quad \text{EM wave in media}$$



# Admittance ( $Y = 1/Z$ )


$$\bar{Z}_{in} = \frac{\bar{Z}_L + j \tan \beta l}{1 + j \bar{Z}_L \tan \beta l}$$

$$\bar{Y}_{in} \equiv \frac{1}{\bar{Z}_{in}} = \frac{1 + j \bar{Z}_L \tan \beta l}{\bar{Z}_L + j \tan \beta l}$$

$$\bar{Y}_{in} = \frac{1 + j(1/\bar{Y}_L) \tan \beta l}{1/\bar{Y}_L + j \tan \beta l}$$

$$\bar{Y}_{in} = \frac{\bar{Y}_L + j \tan \beta l}{1 + j \bar{Y}_L \tan \beta l}$$
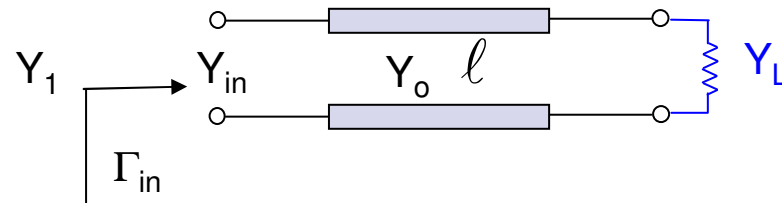
$$Y_{in} = Y_o \left( \frac{Y_L + j Y_o \tan \beta l}{Y_o + j Y_L \tan \beta l} \right)$$




$$\Gamma_{in} = \frac{Z_{in} - Z_1}{Z_{in} + Z_1}$$


$$\Gamma_{in} = \frac{1/Y_{in} - 1/Y_1}{1/Y_{in} + 1/Y_1}$$

$$\Gamma_{in} = \frac{Y_1 - Y_{in}}{Y_1 + Y_{in}} = \frac{1 - \bar{Y}_{in}}{1 + \bar{Y}_{in}}$$

useful for shunt circuits

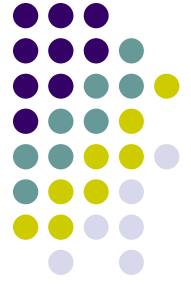

# Earlier exercise

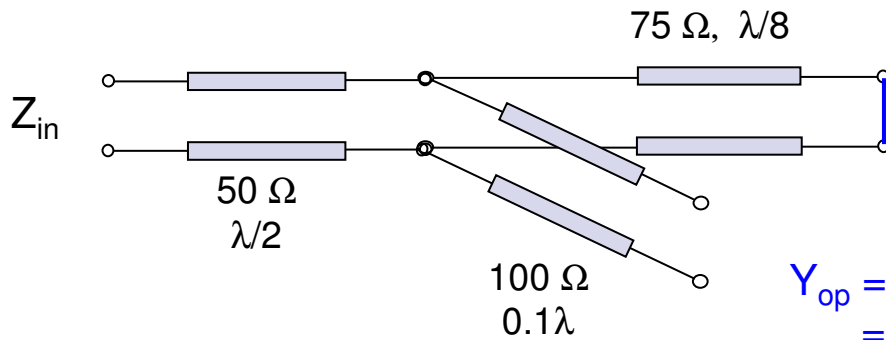



Find  $Z_{in}$  &  $\Gamma_{in}$ .

$$Y_{sh} = -j Y_o \cot(\beta l)$$

$$= -j (1/75) \cot(45^\circ) = -j 0.0133$$

$$Y_{op} = j Y_o \tan(\beta l)$$
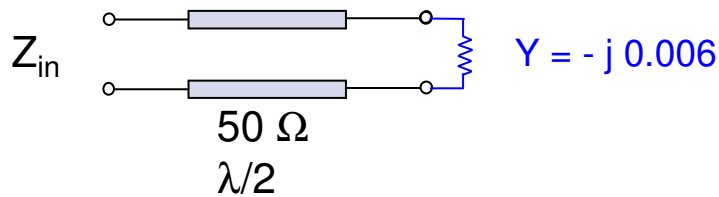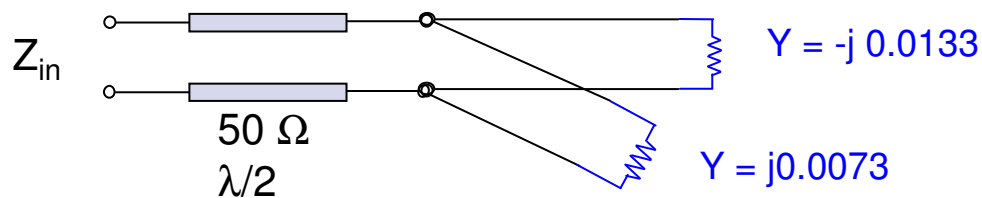
$$= j 0.01 \tan(36^\circ) = j 0.0073 \Omega$$




$$\bar{Y}_{in} = \frac{\bar{Y}_L + j \tan \beta \ell}{1 + j \bar{Y}_L \tan \beta \ell} = \bar{Y}_L$$


$$Y_L = -j 0.006$$

$$Z_{in} = j 166 \Omega$$
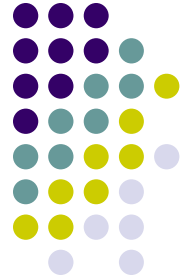
$$\Gamma_{in} = \frac{Y_o - Y_{in}}{Y_o + Y_{in}} = \frac{1/50 + j0.006}{1/50 - j0.006} = 1 \angle (17^\circ + 17^\circ) = 1 \angle 34^\circ$$



# Earlier Exercise – power consideration

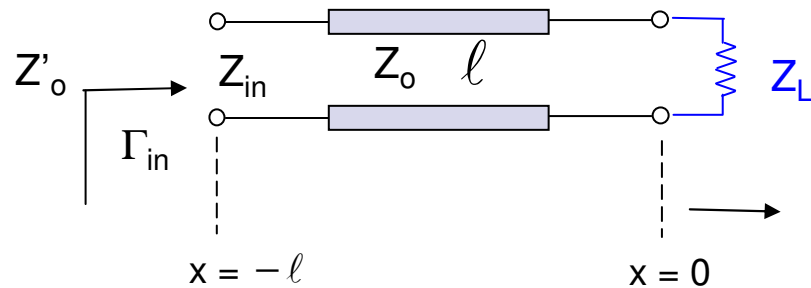

$$Z_o = 50 \Omega$$

$$Z'_o = 50 \Omega$$

$$Z_L = 100 \Omega$$

$$\text{Length} = \lambda/8$$

$$\Gamma_L = 1/3 \quad \Gamma_{in} = 1/3 (-90^\circ)$$

only change phase

$$\bar{Z}_{in} = \frac{\bar{Z}_L + j \tan \beta l}{1 + j \bar{Z}_L \tan \beta l}$$

$$Z_{in} = Z_o \left( \frac{Z_L + j Z_o \tan \beta l}{Z_o + j Z_L \tan \beta l} \right)$$

$$\Gamma_{in} = \frac{Z_{in} - Z'_o}{Z_{in} + Z'_o} = \frac{\bar{Z}'_{in} - 1}{\bar{Z}'_{in} + 1}$$

$$\text{Power reflected} = ? \quad \left| \frac{V^-}{V^+} \right|^2 = |\Gamma|^2 = \left| \frac{1}{3} \right|^2 = 11\%$$


$$\text{Power delivered} = ? \quad 1 - |\Gamma|^2 = 89\%$$

Don't double count reflection....  $\Gamma_L$  &  $\Gamma_{in}$

$$\text{Return Loss (RL)} = -20 \log |\rho| = +9.5 \text{ dB}$$



## Problem 2.26 (input voltage)

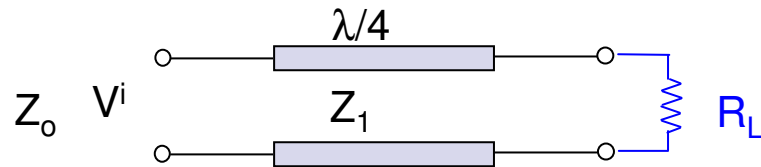

Write  $V^+$  &  $V^-$  in terms of  $V^i$

$$Z_1 = \sqrt{Z_o R_L}$$


$$V(z) = V^+ e^{-j\beta z} + V^- e^{j\beta z}$$

$$\Gamma_L = \frac{Z_L - Z_o}{Z_L + Z_o} = \frac{Z_L - \sqrt{Z_o R_L}}{Z_L + \sqrt{Z_o R_L}}$$


$$V(-\ell) \equiv V^i = V^+ e^{j\beta \ell} + V^- e^{-j\beta \ell} = V^+ (e^{j\beta \ell} + \Gamma_L e^{-j\beta \ell})$$

$$V^+ = \frac{V^i}{e^{j\beta \ell} + \Gamma_L e^{-j\beta \ell}}$$
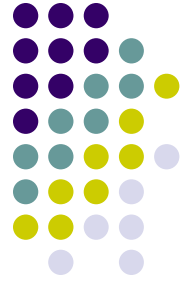
$$V^- = \Gamma_L V^+ = \frac{\Gamma_L V^i}{e^{j\beta \ell} + \Gamma_L e^{-j\beta \ell}}$$


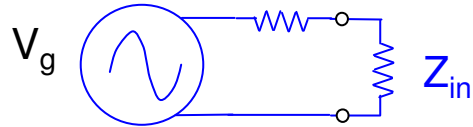
# Max Power Delivery (related to problem 2.12)



Max power deliver when  $Z_{in} = Z_g$  (assuming real)  
 & =  $\frac{1}{2}$  source power.  
 Why ??

assume Z's & V's are all real for simplicity

$$P_{in} = \frac{1}{2} I^2 Z_{in} = \frac{1}{2} \left| \frac{V_g}{Z_g + Z_{in}} \right|^2 Z_{in}$$

$$\frac{dP_{in}}{dZ_{in}} = \frac{1}{2} \left( \frac{-2|V_g|^2}{|Z_g + Z_{in}|^3} \right) Z_{in} + \frac{1}{2} \left| \frac{V_g}{Z_g + Z_{in}} \right|^2$$

$$0 = \left| \frac{V_g}{Z_g + Z_{in}} \right|^2 \left\{ \frac{-2Z_{in}}{Z_g + Z_{in}} + 1 \right\}$$

$$Z_g + Z_{in} = 2Z_{in}$$

$$Z_{in} = Z_g$$

$$\frac{d^2 P_{in}}{dZ_{in}^2} > 0 \quad \text{max}$$

$$P_{in} = \frac{1}{2} \left| \frac{V_g}{Z_g + Z_{in}} \right|^2 Z_{in}$$


$$P_{in}^{max} = \frac{1}{2} \left| \frac{V_g}{Z_g + Z_g} \right|^2 Z_g = \frac{1}{8} \frac{|V_g|^2}{Z_g}$$

$$P_{source} = \frac{1}{2} |V_g I_g| = \frac{1}{2} \left| \frac{V_g^2}{Z_g + Z_{in}} \right| = \frac{1}{4} \frac{|V_g|^2}{Z_g}$$


$$P_{in}^{max} = \frac{1}{2} P_{source}$$




# High f circuit elements

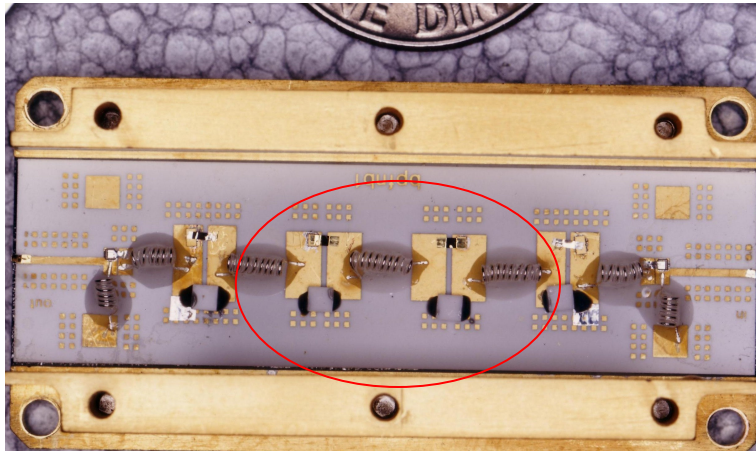


1 GHz lumped element  
Band pass filter

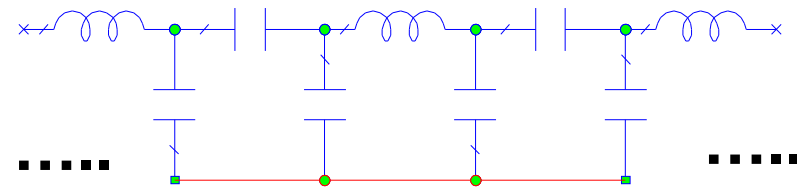

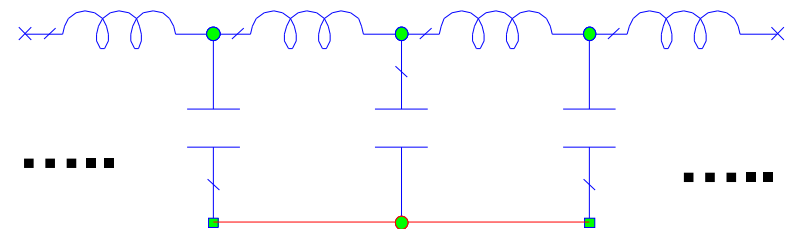
12 GHz lumped element  
Low pass filter  
much smaller



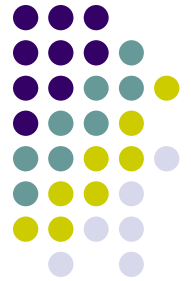A small loop of thin wire is an inductor !!



# High-Z Line as inductor

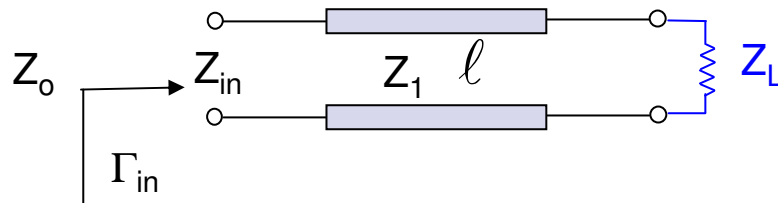


$$Z_{in} = Z_1 \left( \frac{Z_L + jZ_1 \tan \beta l}{Z_1 + jZ_L \tan \beta l} \right)$$


$Z_1 \gg Z_L$   
 line length  $\ll \lambda/4$  ( $\pi/2$ )  
 $Z_L \sim Z_o$

$$Z_{in} = Z_1 \left( \frac{a \angle + \Psi}{b \angle + \varphi} \right) = |Z_{in}| \angle + \theta$$

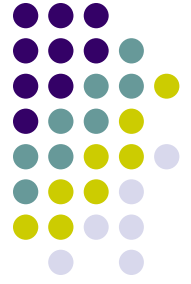$Z_{in}$  has a positive phase  
 $\rightarrow$  inductor-like !!!



# Low-Z Line as capacitor

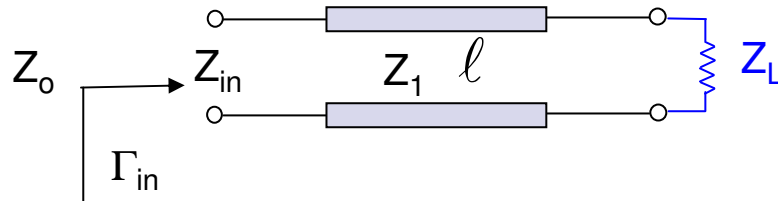

$$Z_{in} = Z_1 \left( \frac{Z_L + jZ_1 \tan \beta l}{Z_1 + jZ_L \tan \beta l} \right)$$


$$\begin{aligned} Z_1 &\ll Z_L \\ \text{line length} &\ll \lambda/4 \quad (\pi/2) \\ Z_L &\sim Z_o \end{aligned}$$

$$Z_{in} = Z_1 \left( \frac{a \angle + \varphi}{b \angle + \Psi} \right) = |Z_{in}| \angle -\theta$$



$Z_{in}$  has a negative phase  
 → capacitor-like !!!



# Low pass filter

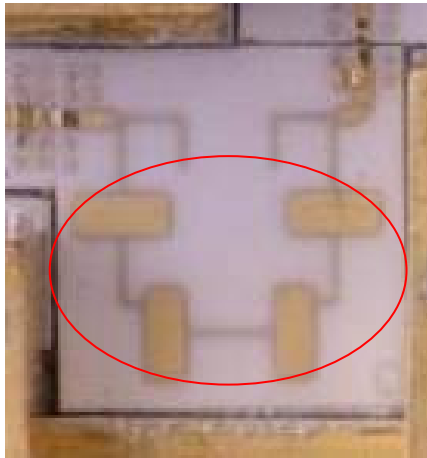


5 GHz low pass filter

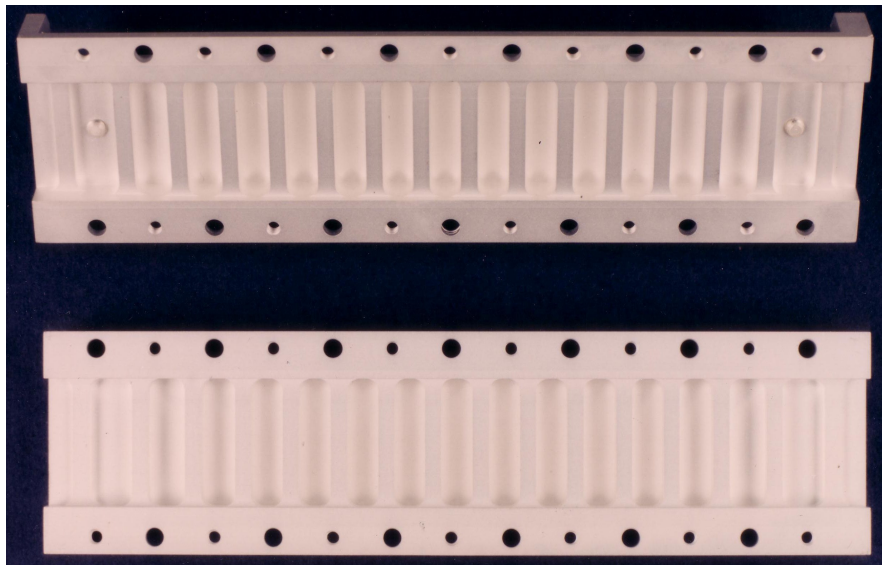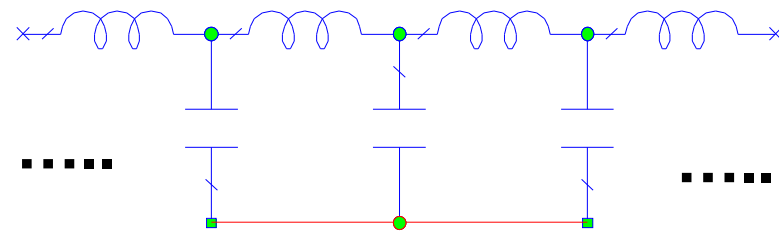



14 GHz low pass filter  
high-low impedance lines  
waveguide  
high power  
low loss



# High-Low-Z lines

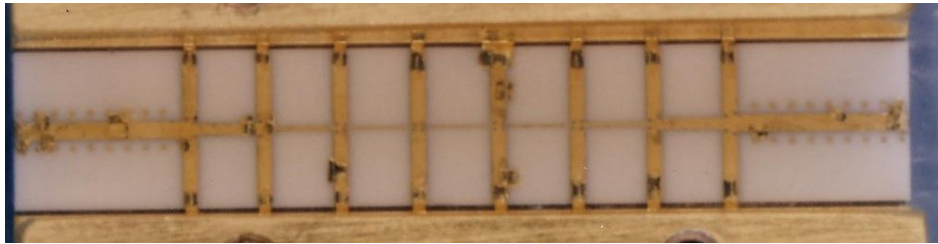

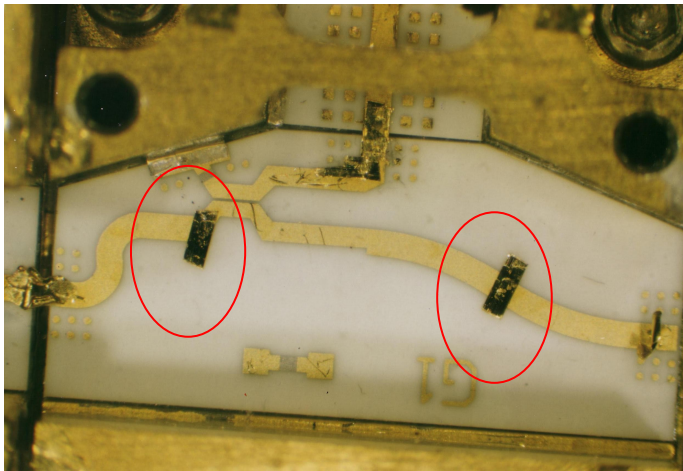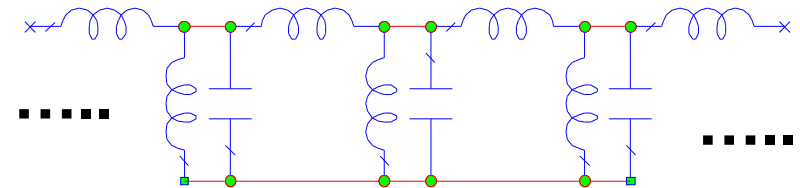20 GHz band pass filter  
high Z lines  $\rightarrow$  inductors  
Short shunt stubs  $\lambda/4$  resonators



13 GHz coupler  
Tuning with stubs (shunt open)  
Think of them as shunt capacitors  
 $\rightarrow$  low Z lines




# Homework

- Ch. 2 # 1, 3, 6, 8, 9, 10
- Ch. 2 # 11-14, 17, 18


# **Common Transmission Lines Radio**

# Coaxial Cable

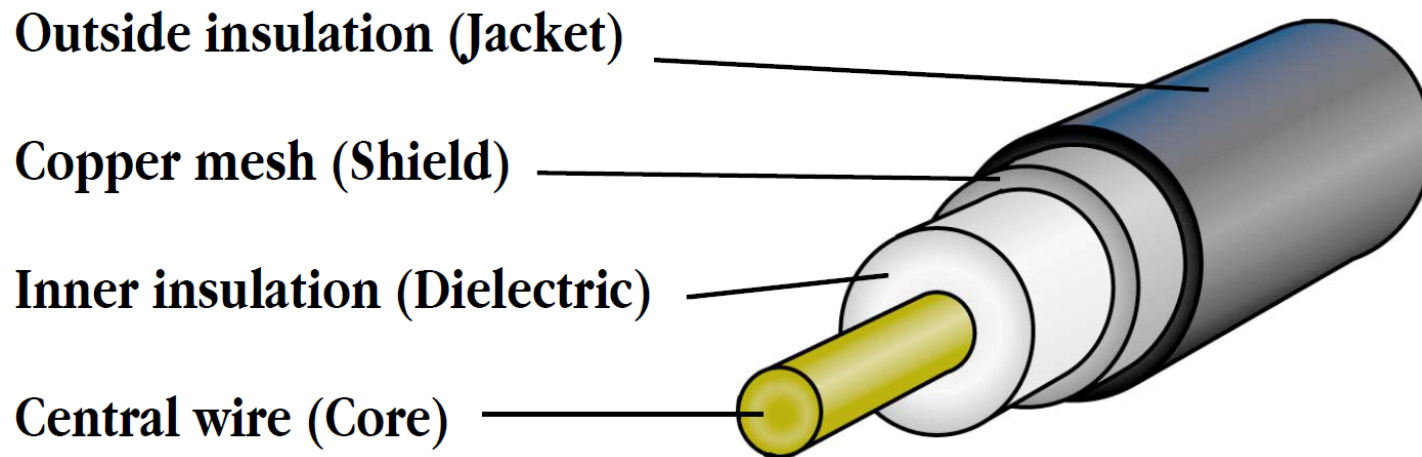

Cable Type	Core (mm)	Dielectric (mm)	Shield (mm)	Jacket (mm)
RG-58	0.9	2.95	3.8	4.95
RG-213	2.26	7.24	8.64	10.29
LMR-400	2.74	7.24	8.13	10.29
3/8" LDF	3.1	8.12	9.7	11

# Coaxial Cable

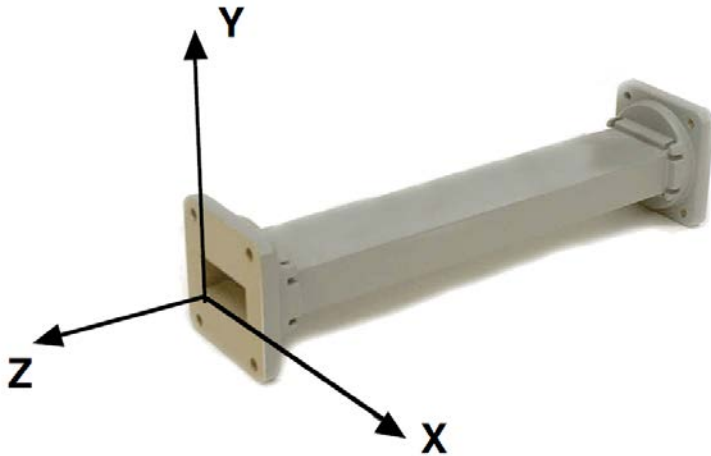

Type of Guide	Rectangular	Circular
Cutoff Wavelength	$2X$	$3.41r$
Longest Wavelength transmitted with little attenuation	$1.6X$	$3.2r$
Shortest Wavelength before next mode becomes possible	$1.1X$	$2.8r$

# Transmission Line Basics

Prof. Tzong-Lin Wu


NTUEE

# Outlines


- ◆ Transmission Lines in Planar structure.
- ◆ Key Parameters for Transmission Lines.
- ◆ Transmission Line Equations.
- ◆ Analysis Approach for  $Z_0$  and  $T_d$
- ◆ Intuitive concept to determine  $Z_0$  and  $T_d$
- ◆ Loss of Transmission Lines
- ◆ Example: Rambus and RIMM Module design

# Transmission Lines in Planar structure

## Homogeneous

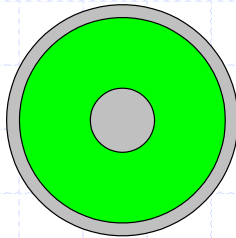


Coaxial Cable

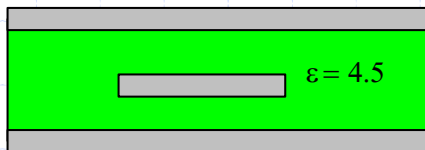


Stripline

## Inhomogeneous

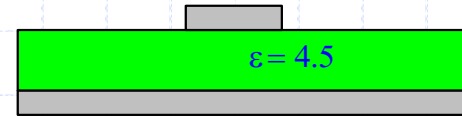

Microstrip line

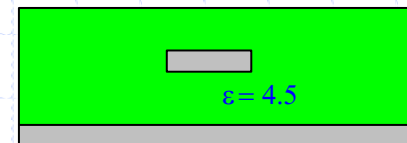

Embedded Microstrip line



# Key Parameters for Transmission Lines


1. Relation of  $V / I$  : Characteristic Impedance  $Z_0$
2. Velocity of Signal: Effective dielectric constant  $\epsilon_e$
3. Attenuation: Conductor loss  $\alpha_c$   
Dielectric loss  $\alpha_d$

Lossless case


$Z_0$	$\sqrt{\frac{L}{C}}$	$\frac{1}{V_p C}$	$\frac{T_d}{C}$
$V_p$	$\frac{1}{\sqrt{LC}}$	$\frac{c_0}{\sqrt{\epsilon_e}}$	$\frac{1}{T_d}$




# Transmission Line Equations

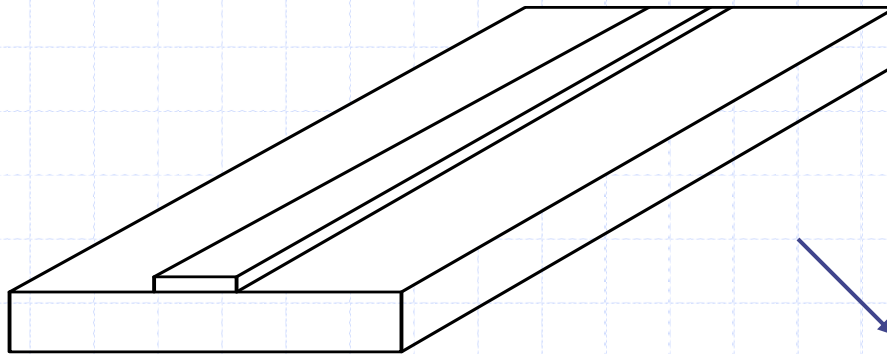

Quasi-TEM assumption

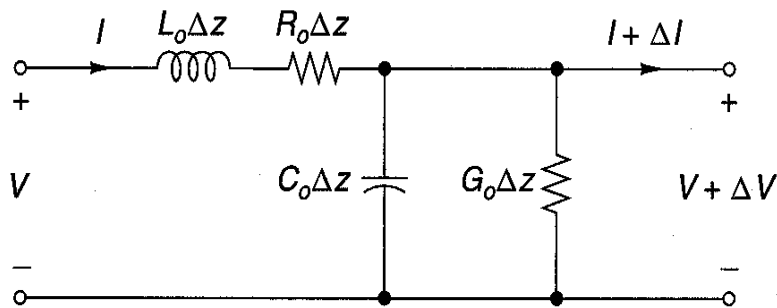

# Transmission Line Equations

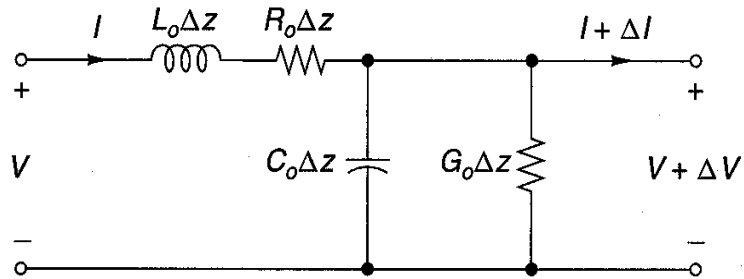

$R_0$  = resistance per unit length (Ohm / cm)

$G_0$  = conductance per unit length (mOhm / cm)

$L_0$  = inductance per unit length (H / cm)

$C_0$  = capacitance per unit length (F / cm)

KVL :  $\frac{dV}{dz} = -(R_0 + j\omega L_0)I$

KCL :  $\frac{dI}{dz} = -(G_0 + j\omega C_0)V$



Solve 2nd order D.E. for V and I

## Transmission Line Equations

Two wave components with amplitudes  $V_+$  and  $V_-$  traveling in the direction of  $+z$  and  $-z$

$$V = V_+ e^{-rz} + V_- e^{+rz}$$

$$I = \frac{1}{Z_0} (V_+ e^{-rz} - V_- e^{+rz}) = I_+ + I_-$$

Where propagation constant and characteristic impedance are

$$r = \sqrt{(R_0 + j\omega L_0)(G_0 + j\omega C_0)} = \alpha + j\beta$$

$$Z_0 = \frac{V_+}{I_+} = \frac{V_-}{I_-} = \sqrt{\frac{R_0 + j\omega L_0}{G_0 + j\omega C_0}}$$

## Transmission Line Equations

$\alpha$  and  $\beta$  can be expressed in terms of  $(R_0, L_0, G_0, C_0)$

$$\alpha^2 - \beta^2 = R_0 G_0 - \omega^2 L_0 C_0$$

$$2\alpha\beta = \omega(R_0 C_0 + G_0 L_0)$$


The actual voltage and current on transmission line:

$$V(z, t) = \text{Re}[(V_+ e^{-\alpha z} e^{-j\beta z} + V_- e^{+\alpha z} e^{j\beta z}) e^{j\omega t}]$$

$$I(z, t) = \text{Re}\left[\frac{1}{Z_0} (V_+ e^{-\alpha z} e^{-j\beta z} - V_- e^{+\alpha z} e^{j\beta z}) e^{j\omega t}\right]$$



# Analysis approach for $Z_0$ and $T_d$ (Wires in air)

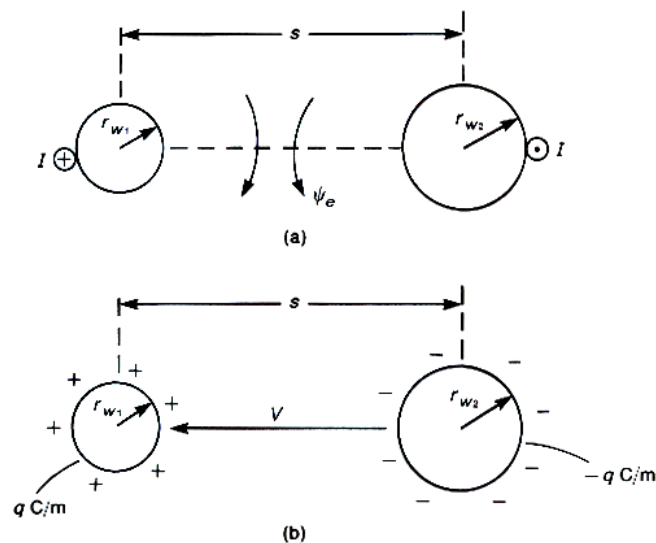


**FIGURE 4.8** Determination of the per-unit-length parameters of a two-wire line: (a) inductance; (b) capacitance.

$$C = ? \text{ (by } Q = C V \text{)}$$

$$L = ? \text{ (by } \Psi = L I \text{)}$$

# Analysis approach for $Z_0$ and $T_d$ (Wires in air):

Ampere's Law for H field

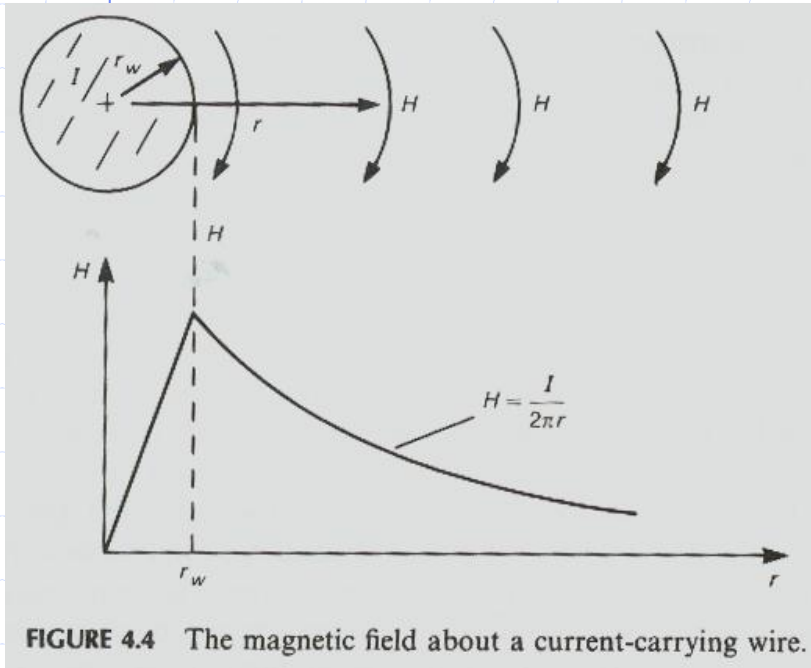

$$H(r) = \frac{I}{\oint_c dl} = \frac{I}{2\pi r}$$

$$2) \quad \psi_e = \int_S \vec{B}_T \cdot d\vec{s} = \int_{r=R_1}^{R_2} \frac{\mu_0 I}{2\pi r} dr = \frac{\mu_0 I}{2\pi} \ln\left(\frac{R_1}{R_2}\right) \quad (\text{in Wb})$$

# Analysis approach for $Z_0$ and $T_d$ (Wires in air):

## Ampere's Law for H field

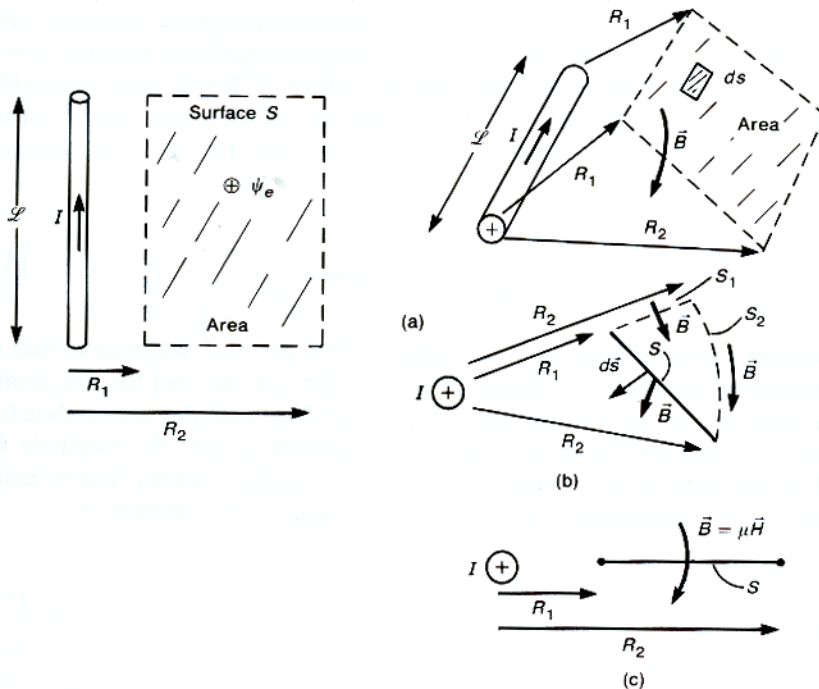


FIGURE 4.5 Illustration of a basic subproblem of determining the flux of a current through a surface: (a) dimensions of the problem; (b) use of Gauss' law; (c) an equivalent but simpler problem.

$$\psi_e = \frac{\mu_0 I}{2\pi} \ln\left(\frac{R_2}{R_1}\right)$$

$$L = \psi_e / I$$

# The per-unit-length Parameters (E):

## Gauss's Law

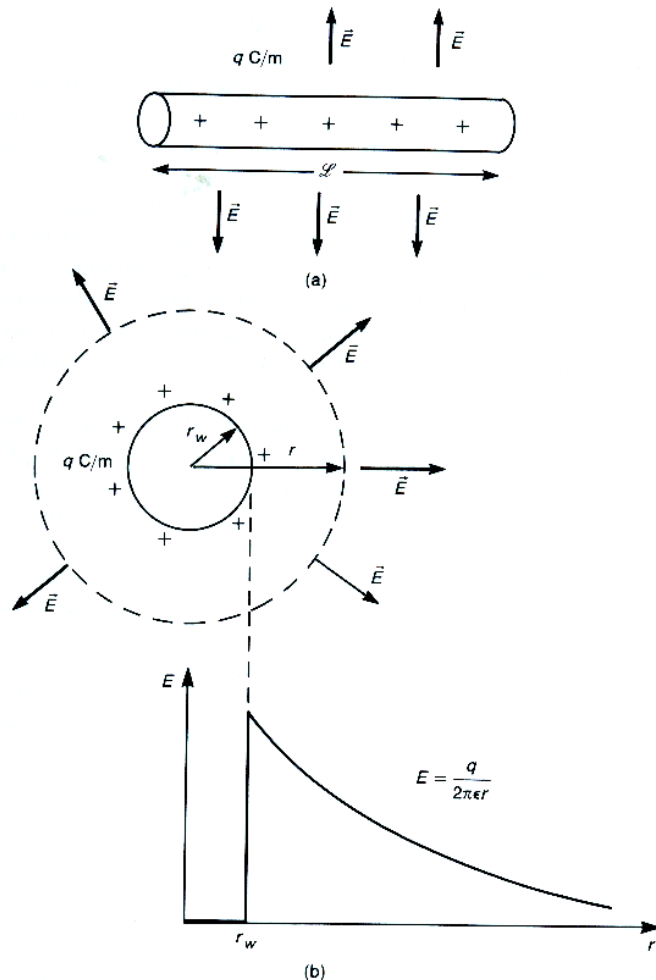


FIGURE 4.6 The electric field about a charge-carrying wire.

1) from gauss law

$$\nabla \cdot \vec{D} = \rho \Leftrightarrow \oint_S \epsilon \vec{E}_T \cdot d\vec{s} = Q_{total}$$


$$\therefore E_T = \frac{q \times 1m}{\epsilon_0 \oint_S ds}$$

$$= \frac{q}{2\pi\epsilon_0 r}$$

$$2) V = \int_C \vec{E}_T \cdot d\vec{l} = - \int_{r=R_2}^{R_1} \frac{q}{2\pi\epsilon_0 r} dr$$

$$= \frac{q}{2\pi\epsilon_0} \ln \frac{R_2}{R_1}$$

# The per-unit-length Parameters (E)

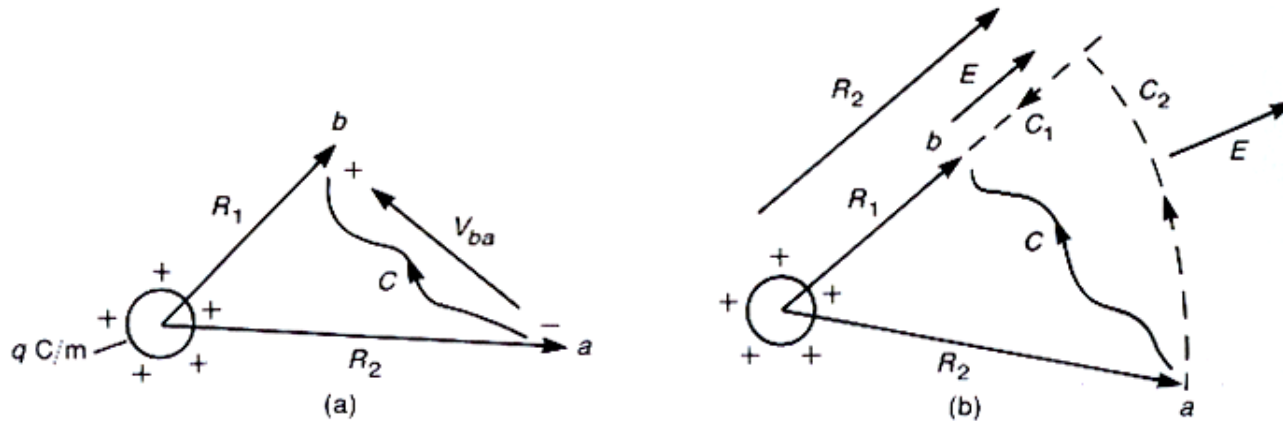

**FIGURE 4.7** Illustration of a basic subproblem of determining the voltage between two points: (a) dimensions of the problem; (b) an equivalent but simpler problem.

$$V = \frac{q}{2\pi\epsilon_0} \ln\left(\frac{R_2}{R_1}\right)$$

$$C = Q/V$$

c. For example Determine the L.C.G.R of the two-wire line.

Inductance :


$$L = \ell_e = \frac{\psi_e}{I}$$

where

$$\begin{aligned} \psi_e &= \frac{\mu_0 I}{2\pi} \ln\left(\frac{s-r_{w2}}{r_{w1}}\right) + \frac{\mu_0 I}{2\pi} \ln\left(\frac{s-r_{w1}}{r_{w2}}\right) \\ &= \frac{\mu_0 I}{2\pi} \ln\left(\frac{(s-r_{w2})(s-r_{w1})}{r_{w1}r_{w2}}\right) \end{aligned}$$

assume  $s \gg r_{w1}, r_{w2}$

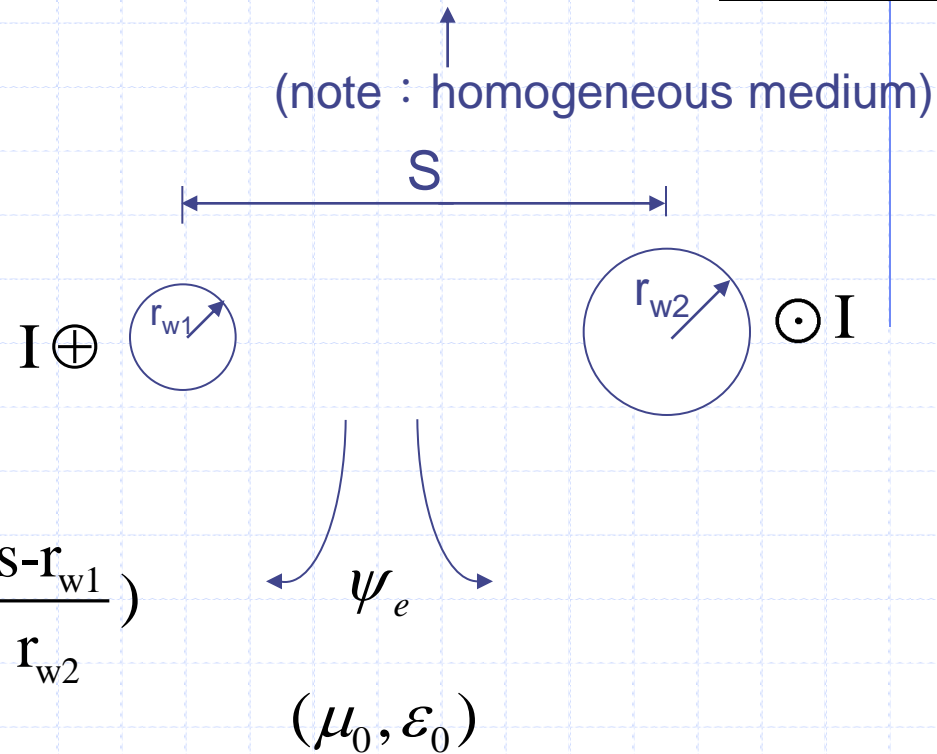
$$\Rightarrow L = \frac{\mu_0}{2\pi} \ln\left(\frac{s^2}{r_{w1}r_{w2}}\right)$$


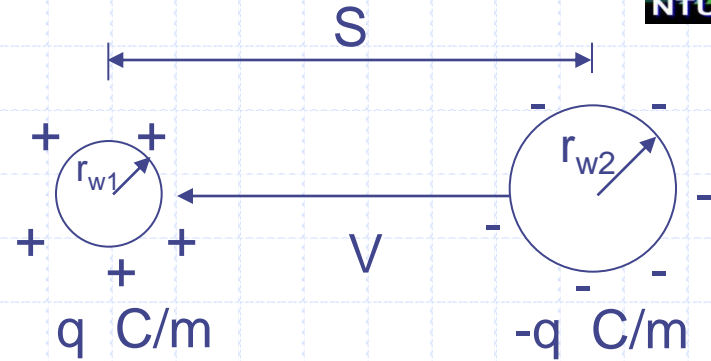
# Capacitance :

$$1) \ell_e \cdot c = \mu_0 \epsilon_0$$

$$\Rightarrow C = \frac{2\pi\epsilon_0}{\ln\left(\frac{s^2}{r_{w1}r_{w2}}\right)}$$



$$2) V = \frac{q}{2\pi\epsilon_0} \ln\left(\frac{s-r_{w2}}{r_{w1}}\right) + \frac{q}{2\pi\epsilon_0} \ln\left(\frac{s-r_{w1}}{r_{w2}}\right)$$

$$= \frac{q}{2\pi\epsilon_0} \ln\left(\frac{(s-r_{w2})(s-r_{w1})}{r_{w1}r_{w2}}\right)$$

$$\cong \frac{q}{2\pi\epsilon_0} \ln\left(\frac{s^2}{r_{w1}r_{w2}}\right) \quad \text{if } s \gg r_{w1}, r_{w2}$$

$$C = \frac{q}{V} = \frac{2\pi\epsilon_0}{\ln\left(\frac{s^2}{r_{w1}r_{w2}}\right)}$$

← the same with 1) approach

# The per-unit-length Parameters

Homogeneous structure


TEM wave structure is like the DC (static) field structure

$$LG = \mu\sigma$$

$$LC = \mu\varepsilon$$

So, if you can derive how to get the L, G and C can be obtained by the above two relations.
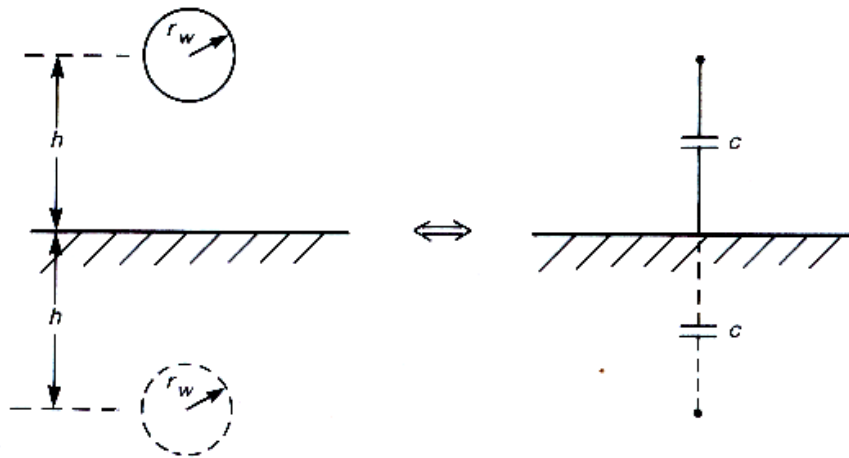
# The per-unit-length Parameters (Above GND )




$2C$

Why?

$L/2$

**FIGURE 4.9** Determination of the per-unit-length capacitance of a wire above a ground plane with the method of images.
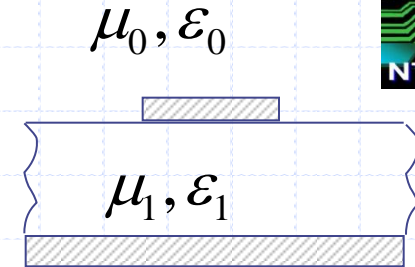
## d. How to determine L,C for microstrip-line.



- 1) This is inhomogeneous medium.
- 2) Numerical method should be used to solve the C of this structure, such as Finite element, Finite Difference...
- 3) But  $\ell_e$  can be obtained by


$$\ell_e C_0 = \mu_0 \epsilon_0 \Rightarrow \ell_e = \frac{\mu_0 \epsilon_0}{C_0}$$

where  $C_0$  is the capacitance when  $\epsilon_1$  medium is replaced by  $\epsilon_0$  medium.

# Analysis approach for $Z_0$ and $T_d$ (Strip line)

Approximate electrostatic solution

1.

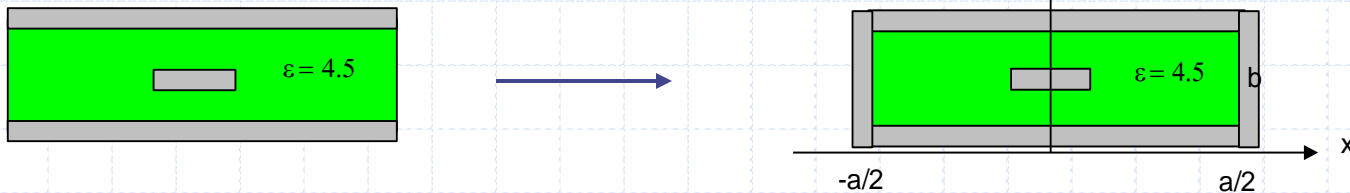

2.

The fields in TEM mode must satisfy Laplace equation

$$\nabla_t^2 \Phi(x, y) = 0$$

where  $\Phi$  is the electric potential

The boundary conditions are

$$\Phi(x, y) = 0 \text{ at } x = \pm a / 2$$

$$\Phi(x, y) = 0 \text{ at } y = 0, b$$

## Analysis approach for $Z_0$ and $T_d$

3. Since the center conductor will contain the surface charge, so

$$\Phi(x, y) = \begin{cases} \sum_{\substack{n=1 \\ \text{odd}}}^{\infty} A_n \cos \frac{n\pi x}{a} \sinh \frac{n\pi y}{a} & \text{for } 0 \leq y \leq b/2 \\ \sum_{\substack{n=1 \\ \text{odd}}}^{\infty} B_n \cos \frac{n\pi x}{a} \sinh \frac{n\pi}{a} (b - y) & \text{for } b/2 \leq y \leq b \end{cases}$$

Why?

4. The unknowns  $A_n$  and  $B_n$  can be solved by two known conditions:

$$\left\{ \begin{array}{l} \text{The potential at } y = b/2 \text{ must continuous} \\ \text{The surface charge distribution for the strip: } \rho_s = \begin{cases} 1 & \text{for } |x| \leq W/2 \\ 0 & \text{for } |x| \geq W/2 \end{cases} \end{array} \right.$$

# Analysis approach for $Z_0$ and $T_d$

5.

$$\begin{cases} V = -\int_0^{b/2} E_y(x=0, y) dy = -\int_0^{b/2} -\partial\Phi(x, y) / \partial y(x=0, y) dy \\ Q = \int_{-w/2}^{w/2} \rho_s(x) dx = W(C / m) \end{cases}$$

6.

$$C = \frac{Q}{V} = \frac{W}{\sum_{\substack{n=1 \\ \text{odd}}}^{\infty} \frac{2a \sin(n\pi W / 2a) \sinh(n\pi b / 2a)}{(n\pi)^2 \epsilon_0 \epsilon_r \cosh(n\pi b / 2a)}}$$

$$Z_0 = \frac{1}{v_p C} = \frac{\sqrt{\epsilon_r}}{cC}$$

*Answers!!*



7.

$$T_d = \sqrt{\epsilon_r} / c$$



# Analysis approach for $Z_0$ and $T_d$ (Microstrip Line)

1.

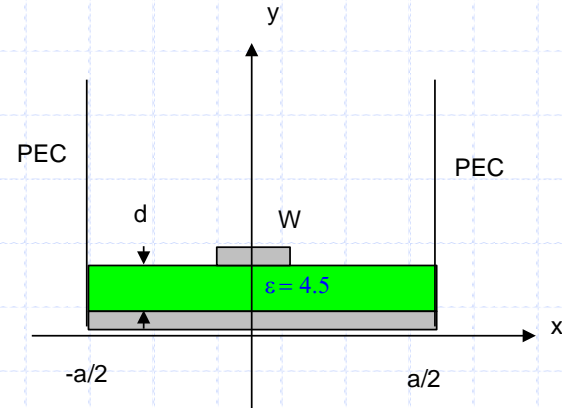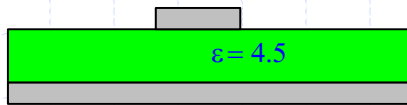

2.

The fields in Quasi - TEM mode must satisfy Laplace equation

$$\nabla_t^2 \Phi(x, y) = 0$$

where  $\Phi$  is the electric potential

The boundary conditions are

$$\Phi(x, y) = 0 \text{ at } x = \pm a / 2$$

$$\Phi(x, y) = 0 \text{ at } y = 0, \infty$$

## Analysis approach for $Z_0$ and $T_d$ (Microstrip Line)

3. Since the center conductor will contain the surface charge, so

$$\Phi(x, y) = \begin{cases} \sum_{\substack{n=1 \\ \text{odd}}}^{\infty} A_n \cos \frac{n\pi x}{a} \sinh \frac{n\pi y}{a} & \text{for } 0 \leq y \leq d \\ \sum_{\substack{n=1 \\ \text{odd}}}^{\infty} B_n \cos \frac{n\pi x}{a} e^{-n\pi y/a} & \text{for } d \leq y \leq \infty \end{cases}$$

4. The unknowns  $A_n$  and  $B_n$  can be solved by two known conditions and the orthogonality of  $\cos$  function :

$$\left\{ \begin{array}{l} \text{The potential at } y = d \text{ must continuous} \\ \text{The surface charge distribution for the strip: } \rho_s = \begin{cases} 1 & \text{for } |x| \leq W/2 \\ 0 & \text{for } |x| \geq W/2 \end{cases} \end{array} \right.$$

## Analysis approach for $Z_0$ and $T_d$ (Microstrip Line)

5.

$$\begin{cases} V = -\int_0^{b/2} E_y(x=0, y) dy = -\int_0^{b/2} -\partial\Phi(x, y) / \partial y(x=0, y) dy = \sum_{\substack{n=1 \\ \text{odd}}}^{\infty} A_n \sinh \frac{n\pi d}{a} \\ Q = \int_{-w/2}^{w/2} \rho_s(x) dx = W(C/m) \end{cases}$$

6.

$$C = \frac{Q}{V} = \frac{W}{\sum_{\substack{n=1 \\ \text{odd}}}^{\infty} \frac{4a \sin(n\pi W / 2a) \sinh(n\pi d / 2a)}{(n\pi)^2 W \epsilon_0 [\sinh(n\pi d / a) + \epsilon_r \cosh(n\pi d / a)]}}$$

## Analysis approach for $Z_0$ and $T_d$ (Microstrip Line)

7. To find the effective dielectric constant  $\epsilon_e$ , we consider two cases of capacitance

1.  $C$  = capacitance per unit length of the microstrip line with the dielectric substrate  $\epsilon_r \neq 1$
2.  $C_0$  = capacitance per unit length of the microstrip line with the dielectric substrate  $\epsilon_r = 1$

$$\therefore \epsilon_e = \frac{C}{C_0}$$



8.

$$Z_0 = \frac{1}{v_p C} = \frac{\sqrt{\epsilon_e}}{c C}$$

$$T_d = \sqrt{\epsilon_e} / c$$

## Tables for $Z_0$ and $T_d$ (Microstrip Line)

$Z_0$ ( $\Omega$ )	20	28	40	50	75	90	100
$\epsilon_{\text{eff}}$	3.8	3.68	3.51	3.39	3.21	3.13	3.09
$L_0$ (nH / mm)	0.119	0.183	0.246	0.320	0.468	0.538	0.591
$C_0$ (pF / mm)	0.299	0.233	0.154	0.128	0.083	0.067	0.059
$T_0$ (ps / mm)	6.54	6.41	6.25	6.17	5.99	5.92	5.88

Fr4 : dielectric constant = 4.5

Frequency: 1GHz

## Tables for $Z_0$ and $T_d$ (Strip Line)

$Z_0$ ( $\Omega$ )	20	28	40	50	75	90	100
$\epsilon_{\text{eff}}$	4.5	4.5	4.5	4.5	4.5	4.5	4.5
$L_0$ (nH / mm)	0.141	0.198	0.282	0.353	0.53	0.636	0.707
$C_0$ (pF / mm)	0.354	0.252	0.171	0.141	0.094	0.078	0.071
$T_0$ (ps / mm)	7.09	7.09	7.09	7.09	7.09	7.09	7.09

Fr4 : dielectric constant = 4.5

Frequency: 1GHz

## Analysis approach for $Z_0$ and $T_d$ (EDA/Simulation Tool)

1. HP Touch Stone (HP ADS)

2. Microwave Office

3. Software shop on Web:

4. APPCAD




([http://softwareshop.edtn.com/netsim/si/termination/term\\_article.html](http://softwareshop.edtn.com/netsim/si/termination/term_article.html))

(<http://www.agilent.com/view/rf> or <http://www.hp.woodshot.com> )




# Concept Test for Planar Transmission Lines

- Please compare their  $Z_0$  and  $V_p$

(a)

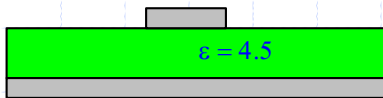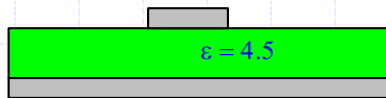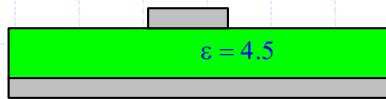


(b)

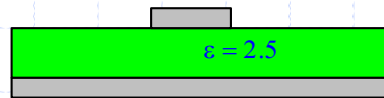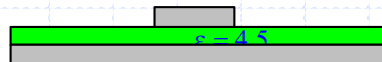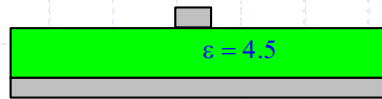











(a)

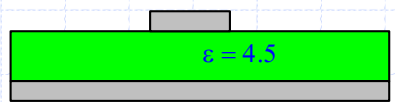

(b)

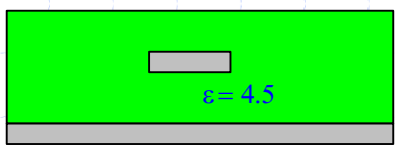


(c)

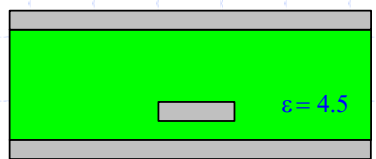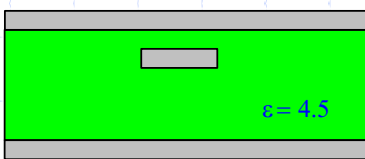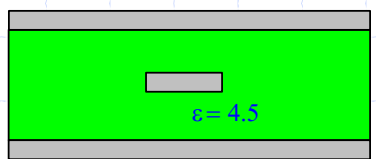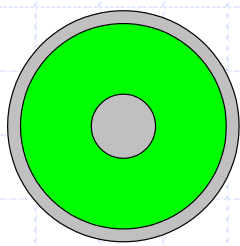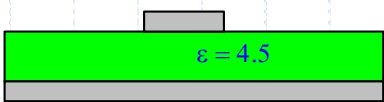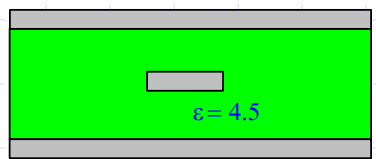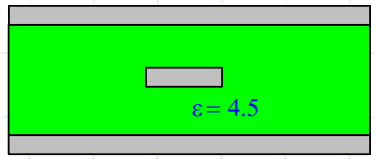









(a)

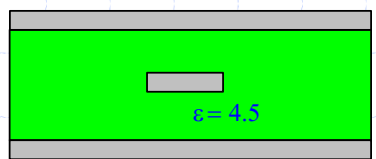


(b)

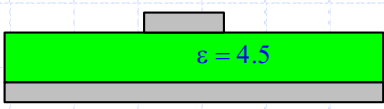

(c)

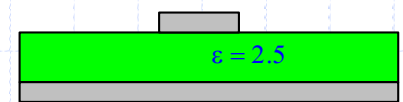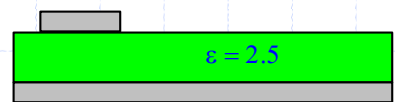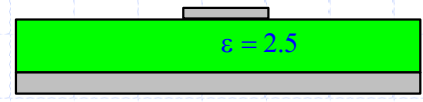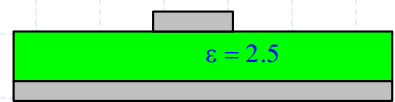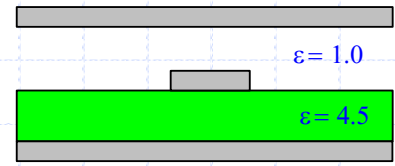

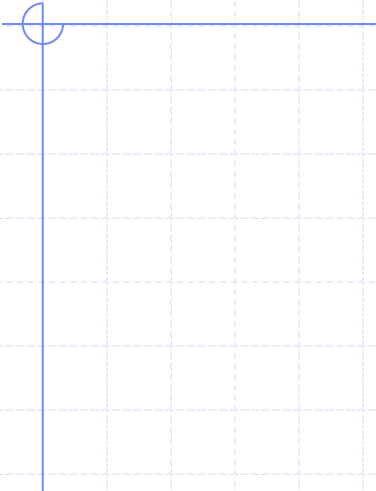

# Loss of Transmission Lines

Typically, dielectric loss is quite small  $\rightarrow G_0 = 0$ . Thus

$$Z_0 = \sqrt{\frac{R_0 + j\omega L_0}{j\omega C_0}} = \sqrt{\frac{L_0}{C_0}} (1 - jx)^{1/2}$$

$$r = \sqrt{(R_0 + j\omega L_0)(j\omega C_0)} = \alpha + j\beta$$

where  $x = \frac{R_0}{\omega L_0}$

- Lossless case :  $x = 0$
- Near Lossless:  $x \ll 1$
- Highly Lossy:  $x \gg 1$

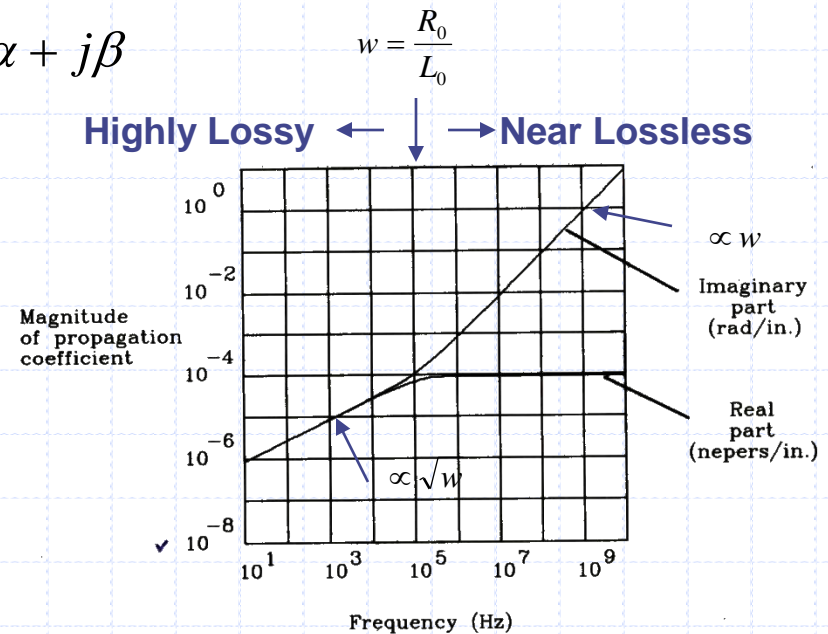


Figure 4.9 Propagation of a cable with fixed series resistance (no skin effect).

# Loss of Transmission Lines

- For Lossless case:
- For Near Lossless case:

$$\alpha = 0$$

$$\beta = \omega \sqrt{L_0 C_0}$$

$$Z_0 = \sqrt{\frac{L_0}{C_0}}$$

$$\text{Time delay } T_0 = \sqrt{L_0 C_0}$$

$$\alpha \approx \frac{R_0}{2\sqrt{L_0 / C_0}}$$

$$\beta \approx \omega \sqrt{L_0 C_0} \left[ 1 - \frac{x^2}{8} \right]$$

$$Z_0 \cong \sqrt{\frac{L_0}{C_0}} \left( 1 - j \frac{R_0}{2\omega L_0} \right) = \sqrt{\frac{L_0}{C_0}} + \frac{1}{j\omega C} \quad \text{where } C = 2T_0 / R_0$$

$$\text{Time delay } T_0 = \sqrt{L_0 C_0}$$

# Loss of Transmission Lines

- For highly loss case: (RC transmission line)

$$\alpha \approx \sqrt{\frac{\omega R_0 C_0}{2}} \left[ 1 - \frac{1}{2x} \right]$$

$$\beta \approx \sqrt{\frac{\omega R_0 C_0}{2}} \left[ 1 + \frac{1}{2x} \right]$$

$$Z_0 \approx \sqrt{\frac{R_0}{2\omega C_0}} \left[ 1 + \frac{1}{2x} \right]$$

*Nonlinear phase relationship with  $f$  introduces signal distortion*

Example of RC transmission line:  
AWG 24 telephone line in home

$$Z_0(\omega) = \left( \frac{R + i\omega L}{j\omega C} \right)^{1/2} = 648(1 + j)$$

where

$$R = 0.0042\Omega / \text{in}$$

$$L = 10\text{nH} / \text{in}$$

$$C = 1\text{pF} / \text{in}$$

$$\omega = 10,000\text{rad} / \text{s} (1600\text{Hz}) : \text{voice band}$$

*That's why telephone company terminate the lines with 600 ohm*

# Loss of Transmission Lines ( Dielectric Loss)

**TABLE 5.3 SOME TYPICAL LINE PARAMETERS**

Case	$L_o$ (nH/cm)	$C_o$ (pF/cm)	$R_o$ ( $\Omega$ /cm)	$Z_o$ ( $\Omega$ )	$T_o$ (ps/cm)	$\epsilon_r$	$R_o/\omega L_o$ <sup>a</sup>
PCB	5	1	0.050 <sup>b</sup>	70.7	70.7	4.5	0.0023
MCM	5	1	5	70.7	70.7	4.5	0.23
Chip	2.2	2	500	32.9	65.8	3.9	52.5

<sup>a</sup> $\omega = 2\pi f = 2\pi(0.35)/T_r = 4.4 \times 10^9$  radian at  $T_r = 0.5$  ns.

<sup>b</sup>4-mil width, 1-oz Cu.

The loss of dielectric loss is described by the loss tangent


$$\tan \delta_D = \frac{G}{wC}$$

FR4 PCB  $\tan \delta_D = 0.035$


$$\therefore \alpha_D = \frac{GZ_0}{2} = (wC \tan \delta_D Z_0) / 2 = \pi f \tan \delta_D \sqrt{LC}$$

# Loss of Transmission Lines (Skin Effect)

- Skin Effect

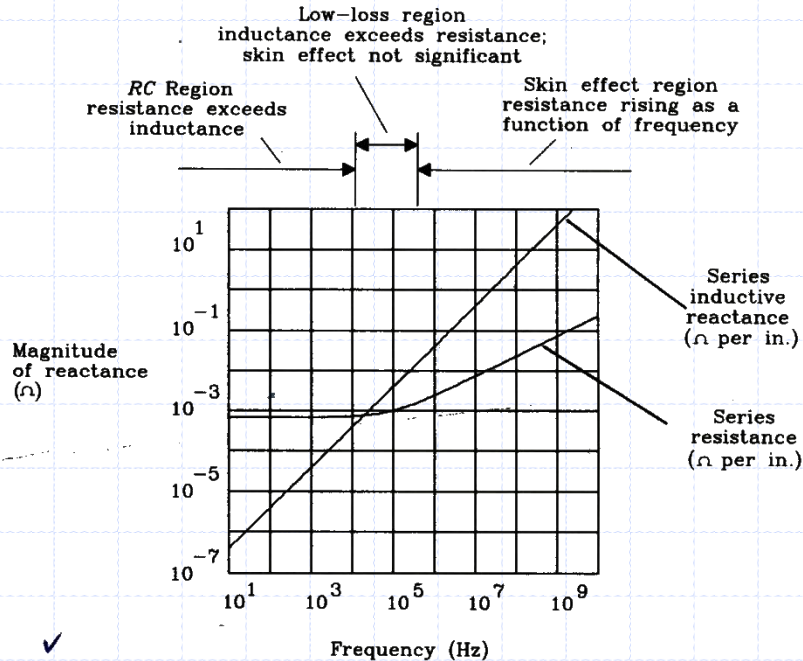


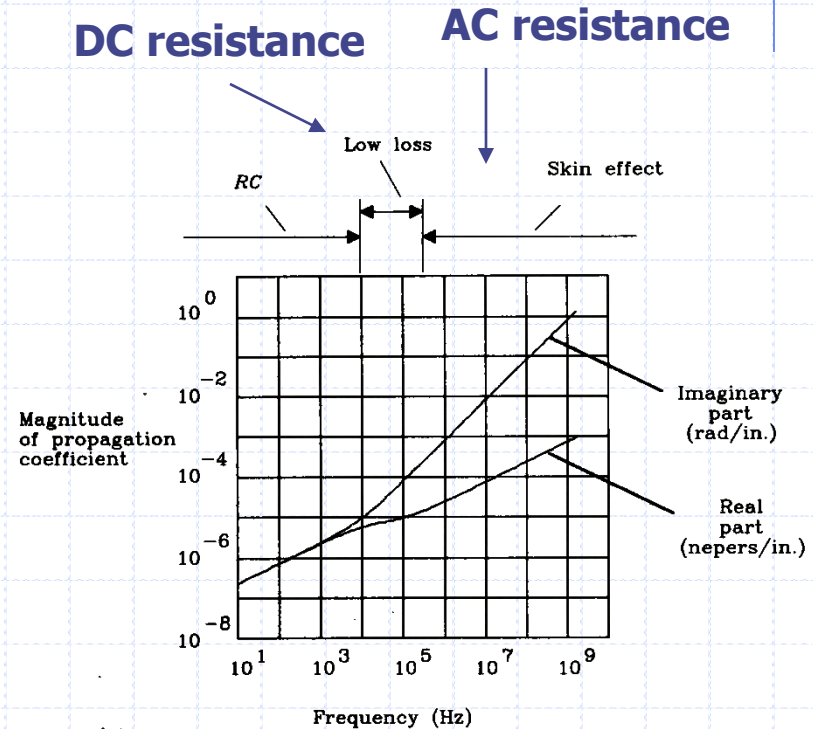✓ **Figure 4.10** Series resistance and series inductive reactance of RG-58/U coax versus frequency.



✓ **Figure 4.11** Propagation coefficient of RG-58/U includes skin effect.

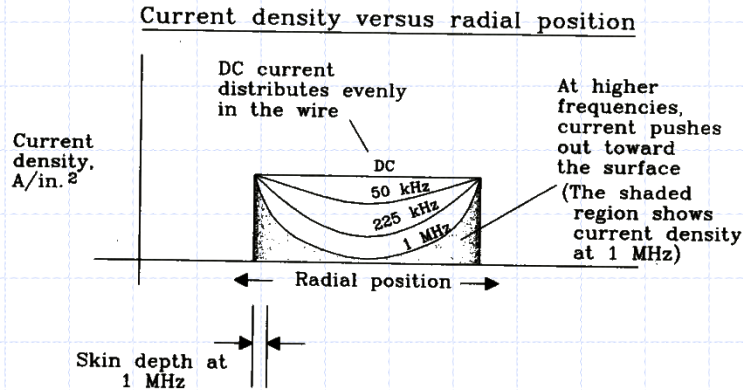
# Loss of Transmission Lines (Skin Effect)



$$\delta_s = \frac{1}{\alpha} = \sqrt{\frac{2}{w\mu\sigma}}$$

$$R(w) = \frac{1}{\sigma} \left( \frac{\text{length}}{\text{area}} \right) \propto \sqrt{\frac{w}{\sigma}}$$

Cross section of wire

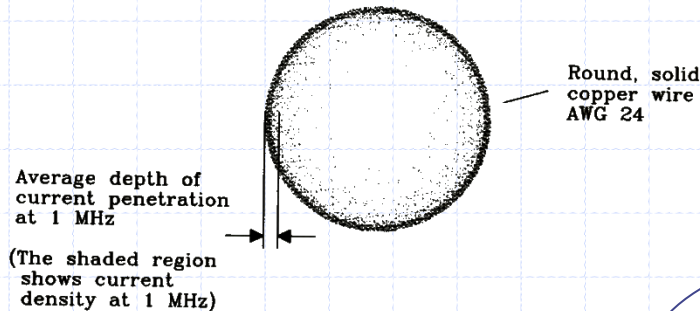

✓ Figure 4.12 Distribution of current in a round wire.

NOTE: In the near lossless region ( $R/wL \ll 1$ ), the characteristic impedance  $Z_0$  is not much affected by the skin effect


$$\therefore R(w) \propto \sqrt{w}$$

$$\therefore R(w)/wL \propto (1/\sqrt{w}) \ll 1$$



# Loss of Transmission Lines (Skin Effect)

$f$ (MHz)	100	200	400	800	1200	1600	2000
$\delta_s = \sqrt{\frac{1}{f\mu\sigma}}$	6.6um	4.7um	3.3um	2.4um	1.9um	1.7um	1.5um
$R_s$ ( $\Omega$ )	2.6m ohm	3.7m ohm	5.2m ohm	7.4m ohm	9.0m ohm	10.8m ohm	11.6m ohm
Trace resistance	1.56 ohm	2.22 ohm	3.12 ohm	4.44 ohm	5.4 ohm	6.48 ohm	7.0 ohm

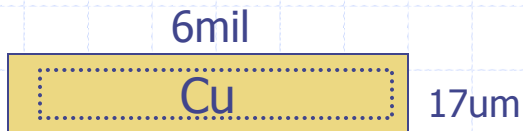

$$\text{Skin depth resistance } R_s = \sqrt{\frac{\pi\mu f}{\sigma}} (\Omega)$$

$$\mu = 4\pi \times 10^{-7} H / m$$

$$\sigma(\text{Cu}) = 5.8 \times 10^7 S / m$$

$$\text{Length of trace} = 20\text{cm}$$

# Loss Example: Gigabit differential transmission lines

For comparison: (Set Conditions)

1. Differential impedance = 100
2. Trace width fixed to 8mil
3. Coupling coefficient = 5%
4. Metal : 1 oz Copper

## Question:

1. Which one has larger loss by skin effect?
2. Which one has larger loss of dielectric?

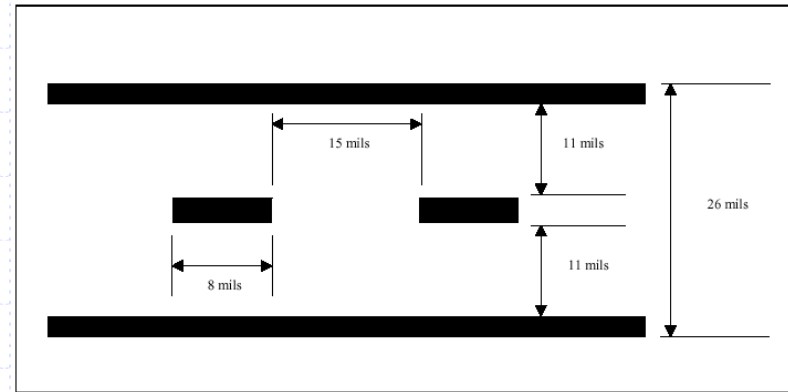


Figure 14 - Single Stripline Coplanar Geometry

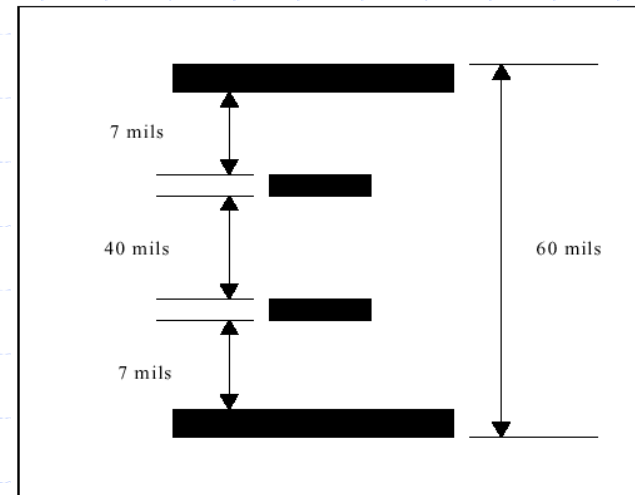


Figure 15 - Dual Stripline Geometry

## Loss Example: Gigabit differential transmission lines

### Skin effect loss

<b>Frequency</b>	<b>Stripline Resistance <math>\Omega</math> / feet</b>	<b>Dual Stripline Resistance <math>\Omega</math> / feet</b>	<b>Percent Difference</b>
500 MHz	6.144	6.648	8.2%
1.5 GHz	10.668	11.508	7.9%
2.5 GHz	13.728	14.832	8.0%

**Table 3 - Simulated Results of Skin Effect Losses**

# Loss Example: Gigabit differential transmission lines

## Skin effect loss

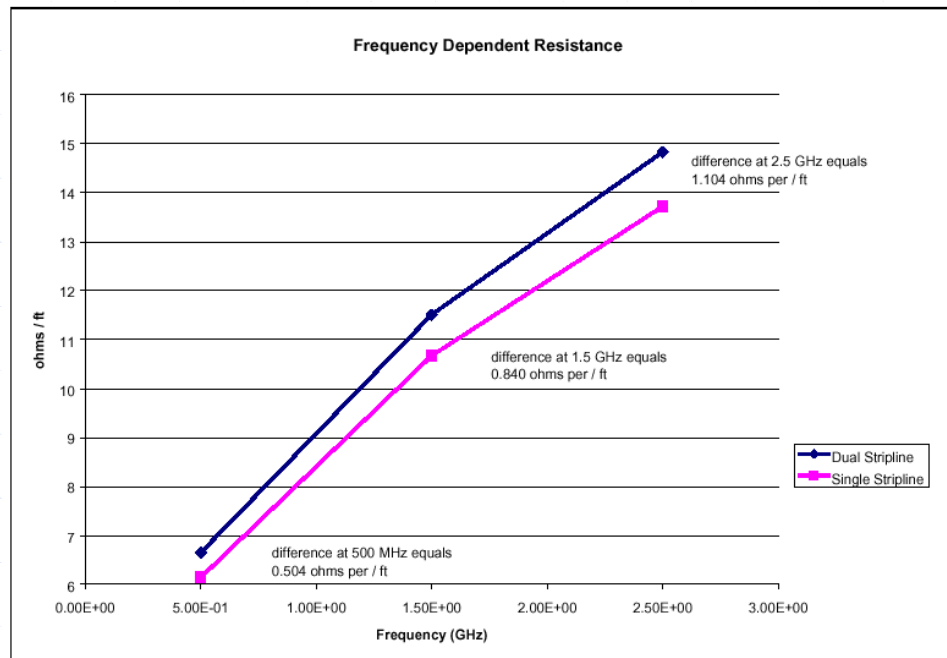


Figure 18 - Graph of Simulated Results of Skin Effect Losses

Why?

# Loss Example: Gigabit differential transmission lines

Look at the field distribution of the common-mode coupling

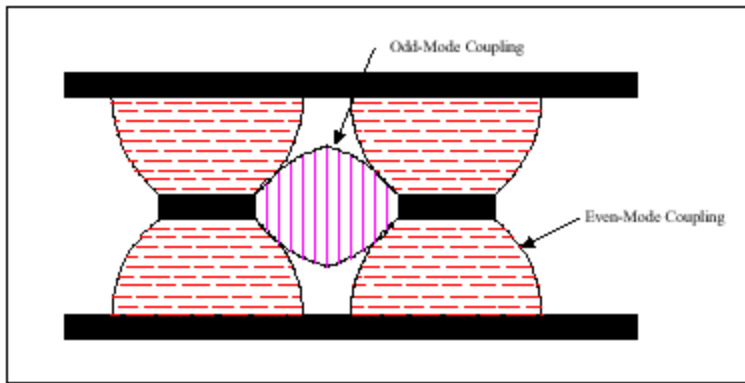


Figure 11 - Coplanar Differential Single Stripline Routing Geometry

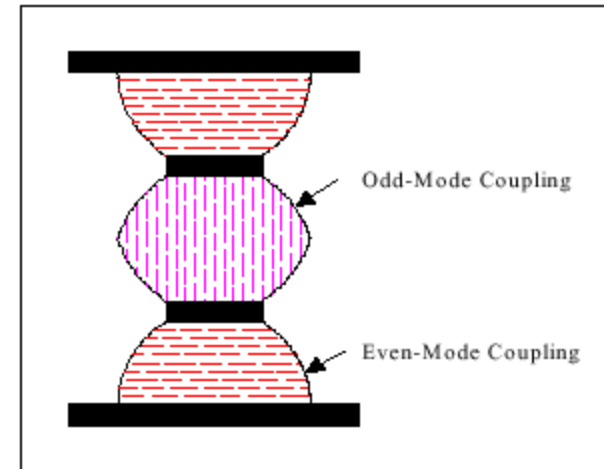


Figure 12 - Differential Routing in a Dual Stripline Geometry

Coplanar structure has more surface for current flowing

## Loss Example: Gigabit differential transmission lines

How about the dielectric loss ? Which one is larger?

## Loss Example: Gigabit differential transmission lines

The answer is dual stripline has larger loss. Why ?



The field density in the dielectric between the trace and GND is higher for dual stripline.

## Loss Example: Gigabit differential transmission lines


Which one has higher ability of rejecting common-mode noise ?

## Loss Example: Gigabit differential transmission lines



The answer is coplanar stripline. Why ?

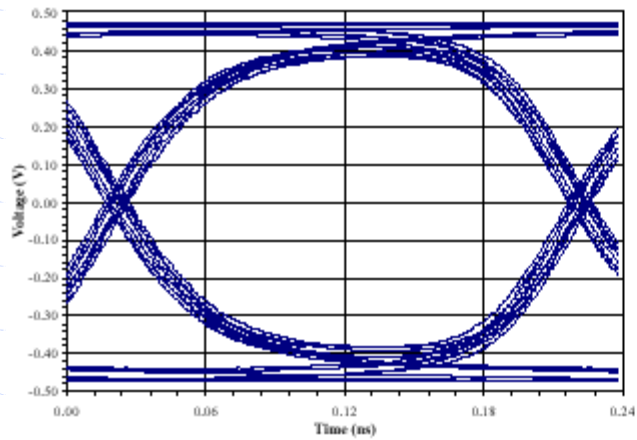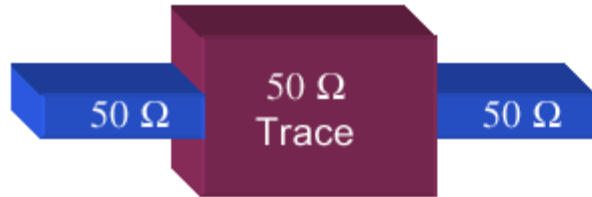

769 mV Opening, 6.25% Jitter

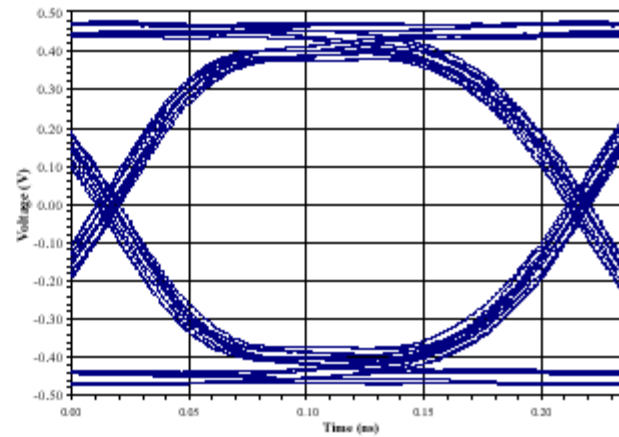

754 mV Opening, 6.25% Jitter

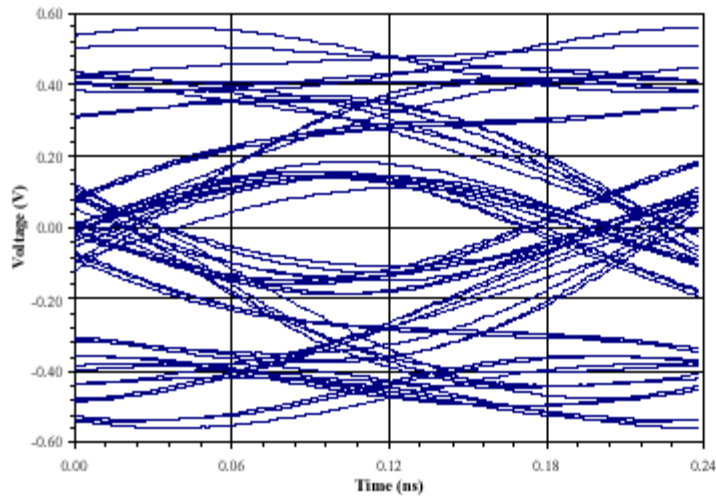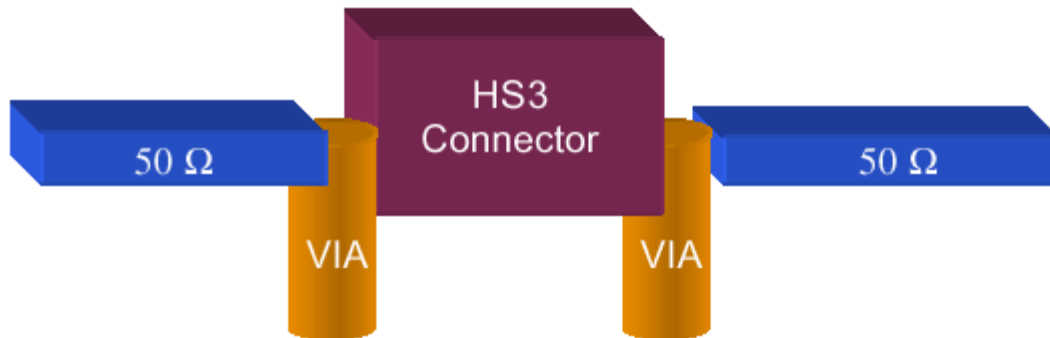

218 mV Opening, 34.4% Jitter


-The output waveform shown results from a 1-volt, 32-bit inverting K28.5 input bit pattern (5 Gbps, 60ps edges) that is applied to a system with two through-holes, two AMP HS3 connectors, and a 12 mil, 50 Ohm stripline trace that is ~18" long.

<b>Material</b>	<b><math>\epsilon_r^*</math> @ 1 MHz</b>	<b><math>\epsilon_r^*</math> @ 1 GHz</b>	<b><math>\tan \delta^*</math> @ 1 GHz</b>	<b>Relative Cost**</b>
<b>FR4</b>	<b>4.30</b>	<b>4.05</b>	<b>0.020</b>	<b>1</b>
<b>GETEK</b>	<b>4.15</b>	<b>4.00</b>	<b>0.015</b>	<b>1.1</b>
<b>ROGERS 4350/4320</b>	<b>3.75</b>	<b>3.60</b>	<b>0.009</b>	<b>2.1</b>
<b>ARLON CLTE</b>	<b>3.15</b>	<b>3.05</b>	<b>0.004</b>	<b>6.8</b>


\* Measured from test data

\*\*Cost factor derived from 10" by 20", 12-layer backplane

## FR4

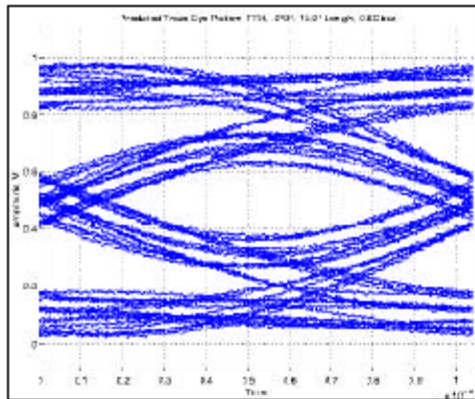

## GETEK

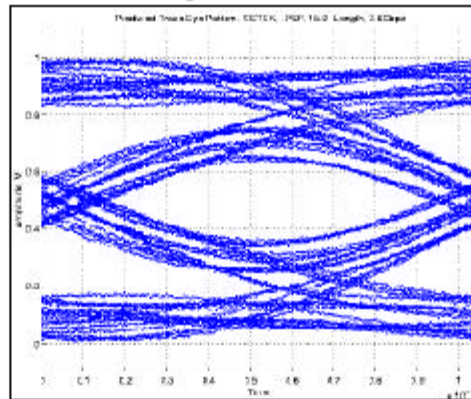

### FR4:

Jitter = 0.30 UI  
Opening = 238 mV

### GETEK:

Jitter = 0.28 UI  
Opening = 268 mV


### ROGERS 4350:

Jitter = 0.20 UI  
Opening = 426 mV


### ARLON CLTE:

Jitter = 0.19 UI  
Opening = 520 mV

## ROGERS 4350

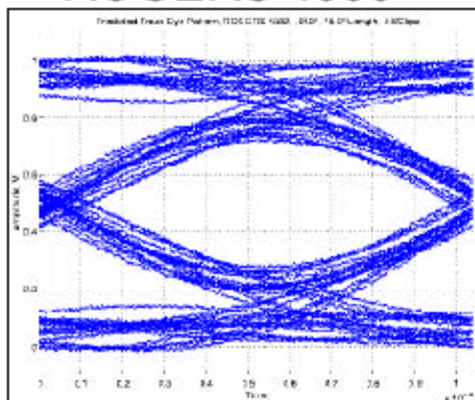

## ARLON CLTE

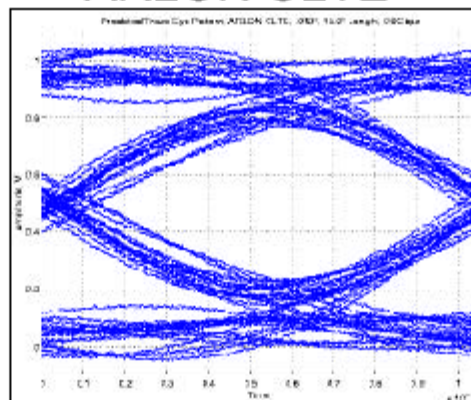


-The output waveforms shown result from a 1-volt, 32-bit inverting K28.5 input bit pattern (10 Gbps, 60ps edges) that is applied to a 12 mil, 50 Ohm stripline trace that is 18" long.
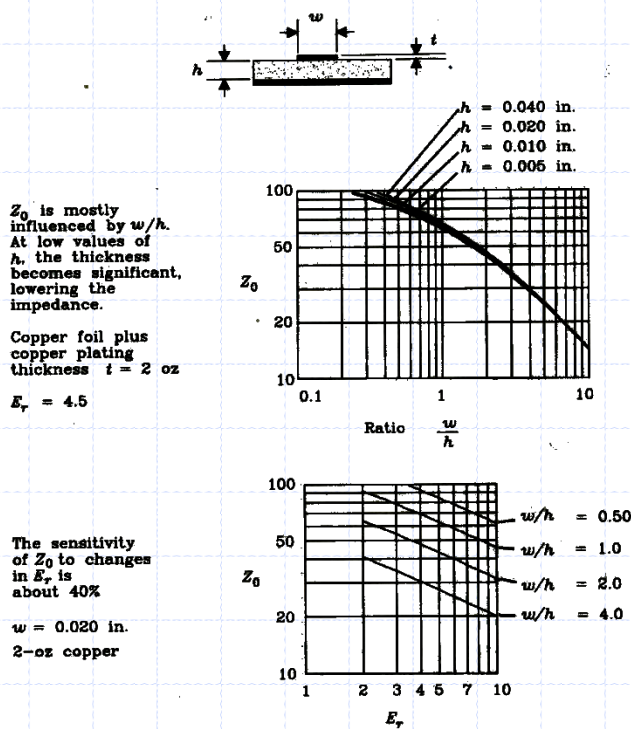
# Intuitive concept to determine $Z_0$ and $T_d$

- How physical dimensions affect impedance and delay

*Sensitivity* is defined as percent change in impedance per percent change in line width, *log-log plot* shows sensitivity directly.



$Z_0$  is mostly influenced by  $w/h$ , the sensitivity is about 100%. It means 10% change in  $w/h$  will cause 10% change of  $Z_0$


The sensitivity of  $Z_0$  to changes in  $\epsilon_r$  is about 40%

✓ Figure 4.31 Characteristic impedance of a microstrip transmission line versus geometry and permittivity. (See formulas in Appendix C.)

# Intuitive concept to determine $Z_0$ and $T_d$


## • Striplines

### impedance

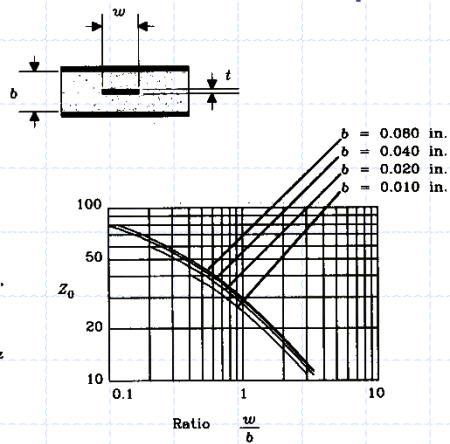

$Z_0$  is mostly influenced by  $w/h$ . At low values of  $h$ , the thickness becomes significant, lowering the impedance.

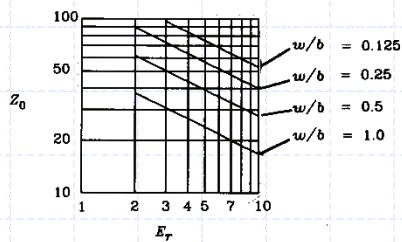Copper foil thickness  $t = 2$  oz  
 $E_r = 4.5$




The sensitivity of  $Z_0$  to changes in  $E_r$  is exactly  $1/2$

$w = 0.010$  in.  
 1-oz copper


✓ **Figure 4.33** Characteristic impedance of a stripline transmission line versus geometry and permittivity. (See formulas in Appendix C.)

### Delay

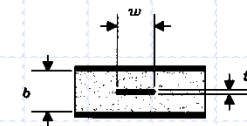

Comparison of impedance formula in Appendix C with simple formula set. The simple formula blows up when used with wide traces.

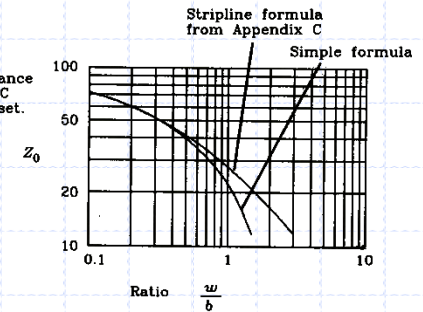
$b = 0.020$  in.  
 1-oz copper  
 $E_r = 4.5$



Propagation delay, ps/in.

The sensitivity of  $T_p$  to changes in  $E_r$  is exactly  $1/2$ .

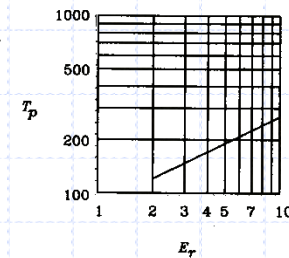Only  $E_r$  controls propagation delay; parameters  $b$ ,  $w$ , and  $t$  don't matter.



✓ **Figure 4.34** Characteristic impedance of a stripline transmission line.

# Ground Perforation: BGA via and impedance

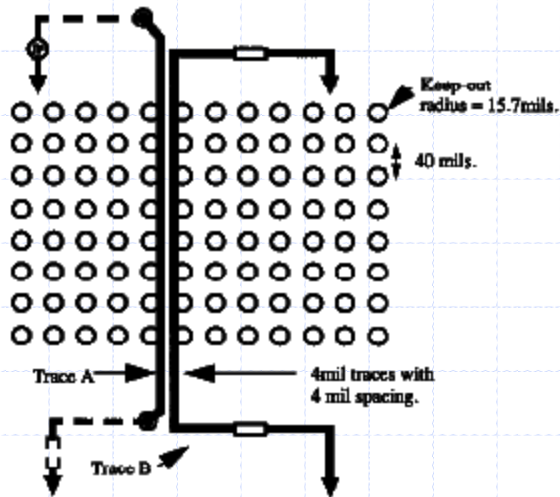


Figure 1. Section of a typical 1600pin BGA pin field with signal traces running through. Drawing is not to scale.

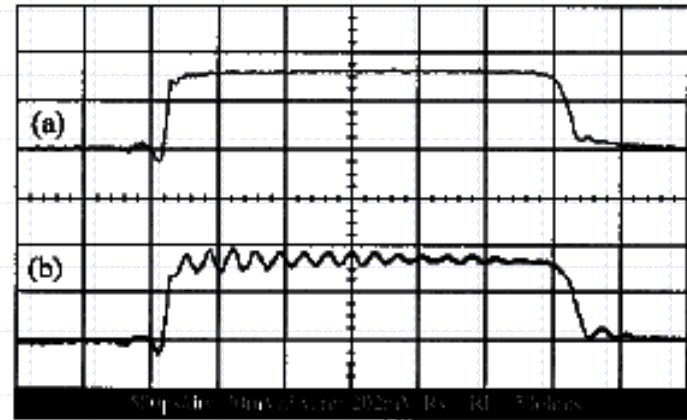


Figure 2: Characteristic Impedance measurements for a 68.8ohm (ideal value) trace over (a) solid reference plane, and (b) perforated reference plane.

# Ground Perforation: Cross-talk (near end)

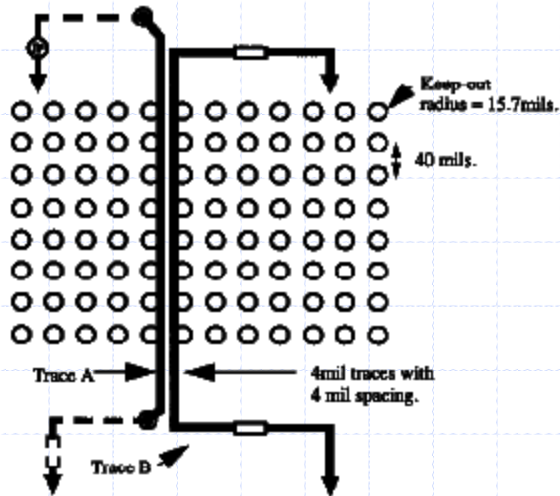


Figure 1. Section of a typical 1600pin BGA pin field with signal traces running through. Drawing is not to scale.

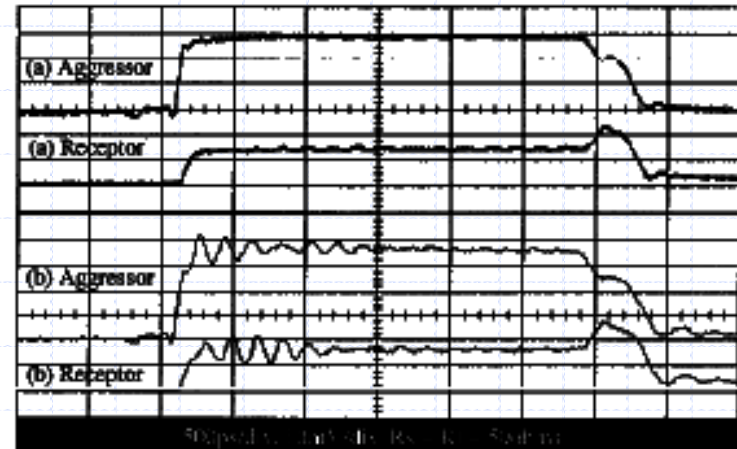


Figure 3: Near-end crosstalk measured for (a) solid reference plane and (b) perforated reference plane with both ends of Trace B terminated in 50ohm.

# Ground Perforation : Cross-talk (far end)

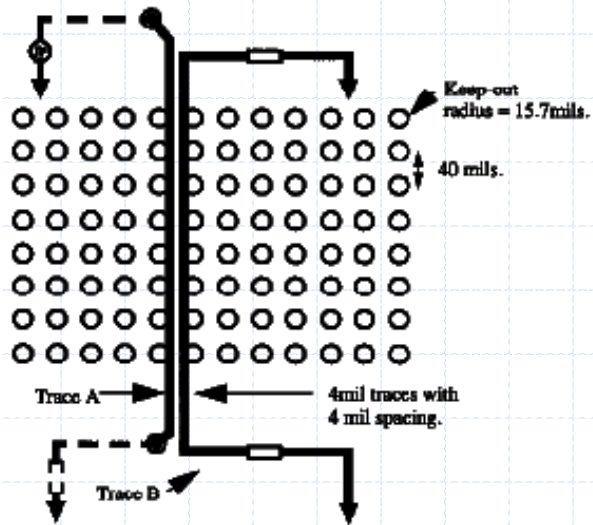


Figure 1. Section of a typical 1600pin BGA pin field with signal traces running through. Drawing is not to scale.


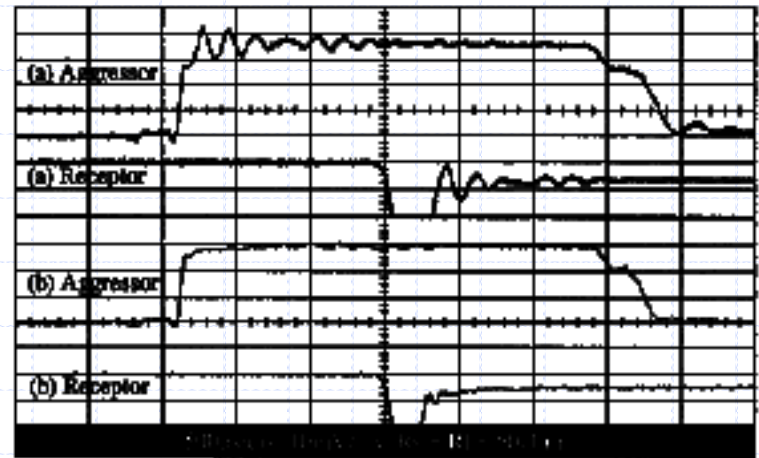


Figure 4: Far-end crosstalk measured for (a) perforated reference plane and (b) solid reference plane with both ends of Trace B terminated in 50ohm.

## Example(II): Transmission line on non-ideal GND
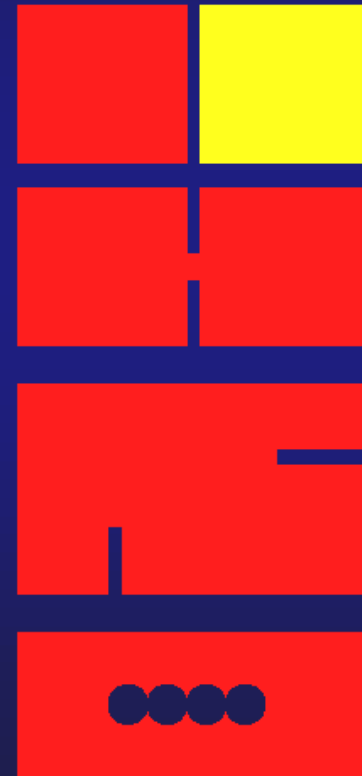
### Reasons for splits or slits on GND planes

- DC isolation between different supply voltages.
- AC isolation of digital from low noise analog circuits.
- Low cost method of removing unwanted resonances from the power distribution system.
- Nearby touching via holes.



## Example(II): Transmission line on non-ideal GND


### Disadvantages of Image Plane Slits and Splits

- Transverse slits in the image planes present a discontinuity to the flow of AC currents.
- Result in significant signal degradation.
- Help generate common mode currents that result in significant radiation.

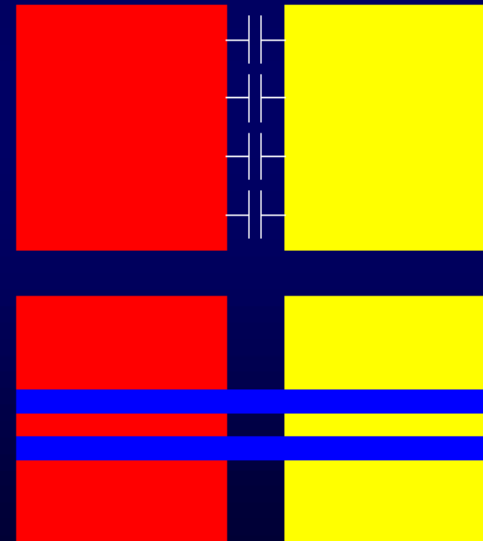
## Example(II): Transmission line on non-ideal GND

Two most commonly used:


- AC shorting (stitching) the two separated planes with capacitors.
- Using differential lines to cross the split.



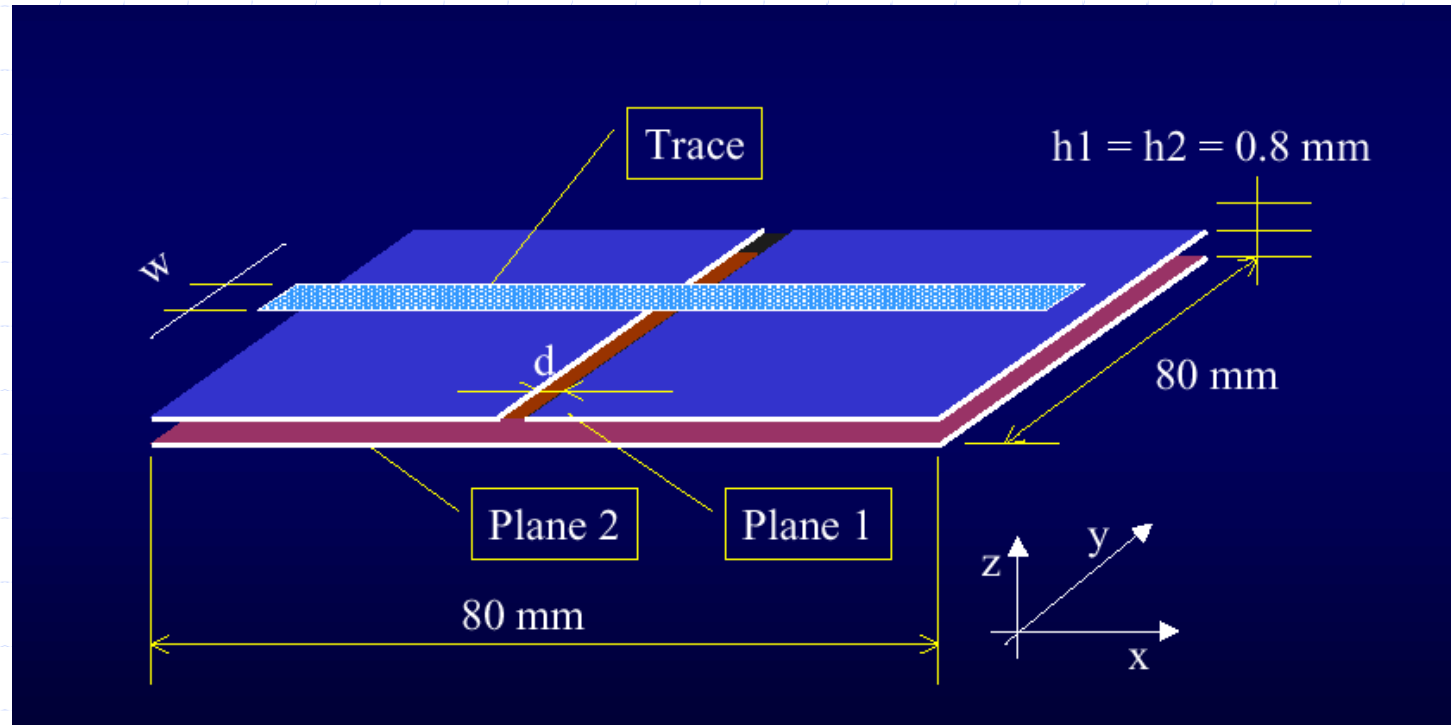
## Example(II): Transmission line on non-ideal GND


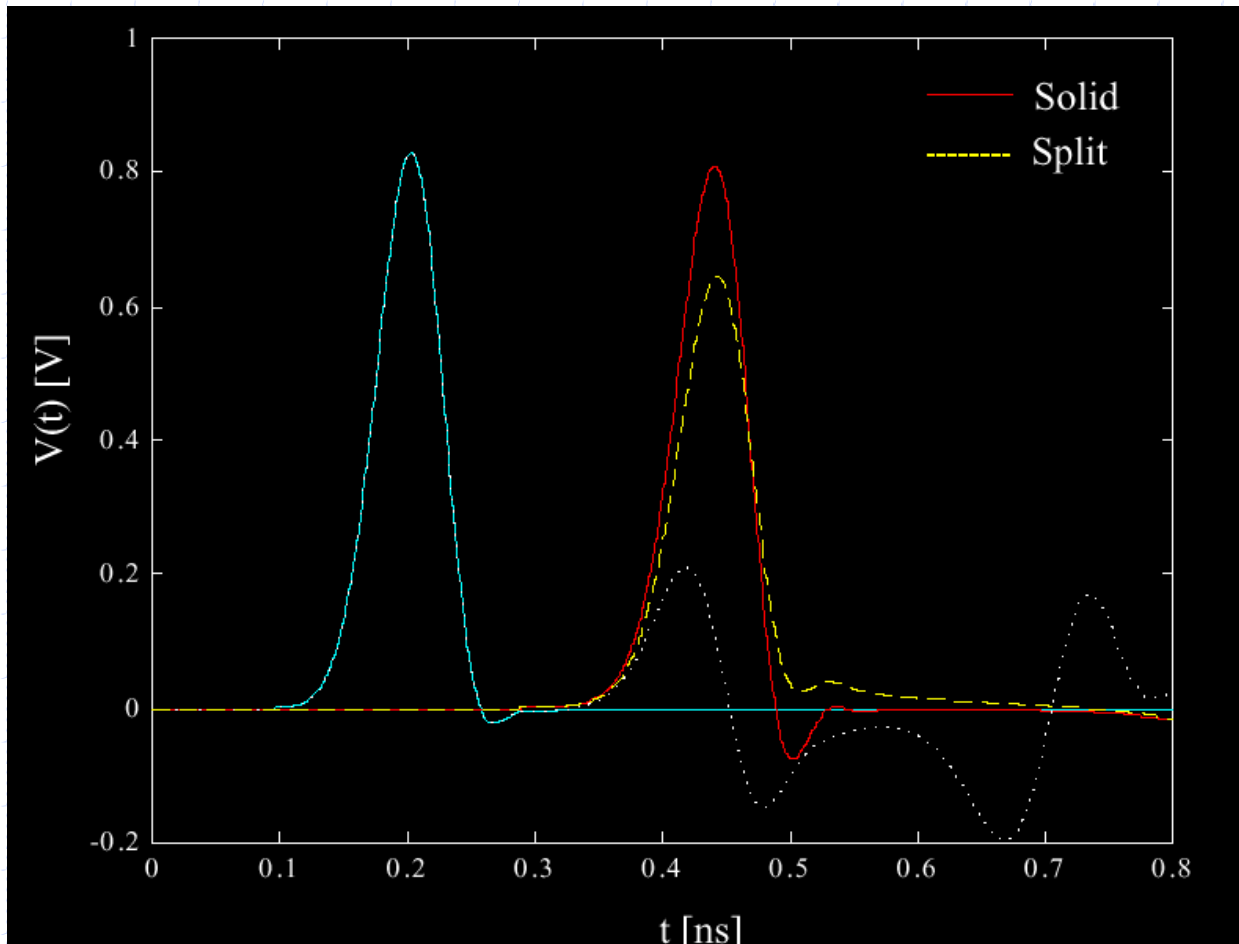
## Example(II): Transmission line on non-ideal GND



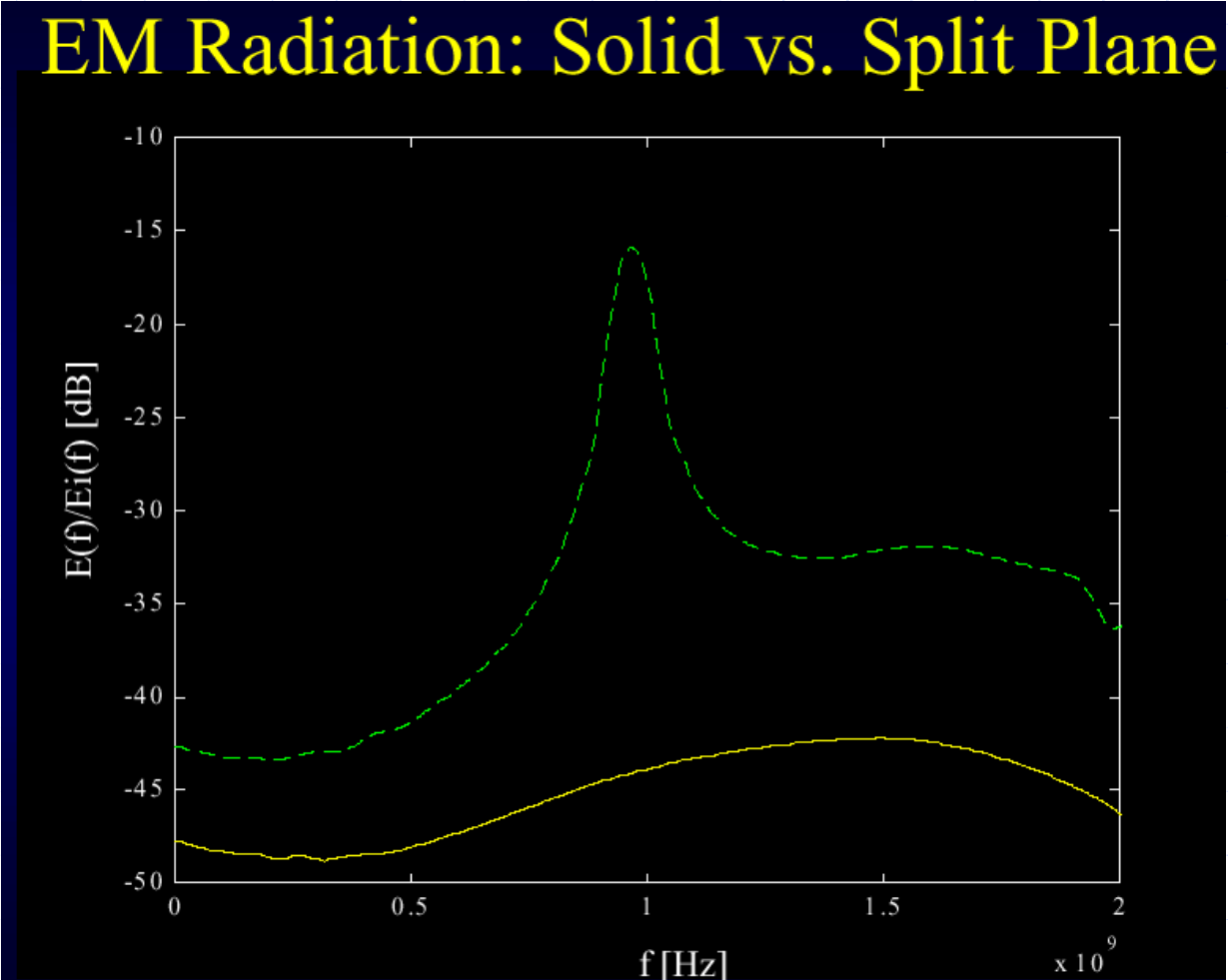
## Example(II): Transmission line on non-ideal GND




## Example(II): Transmission line on non-ideal GND

### Differential Microstrip

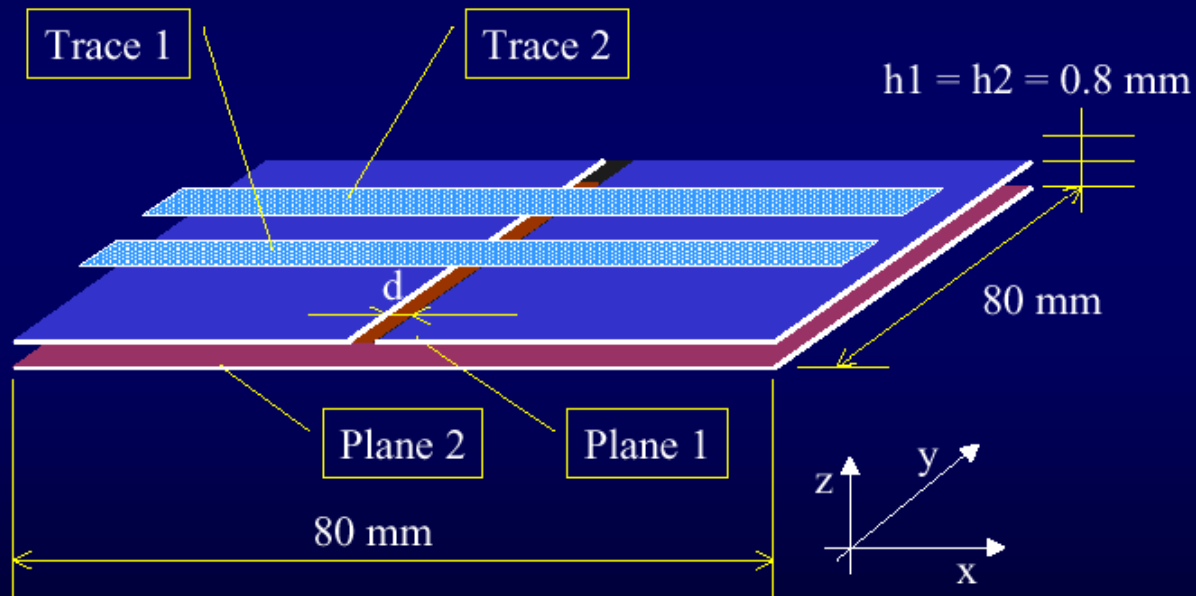


Input side

## Signal Quality: Single vs. Diff. (I)

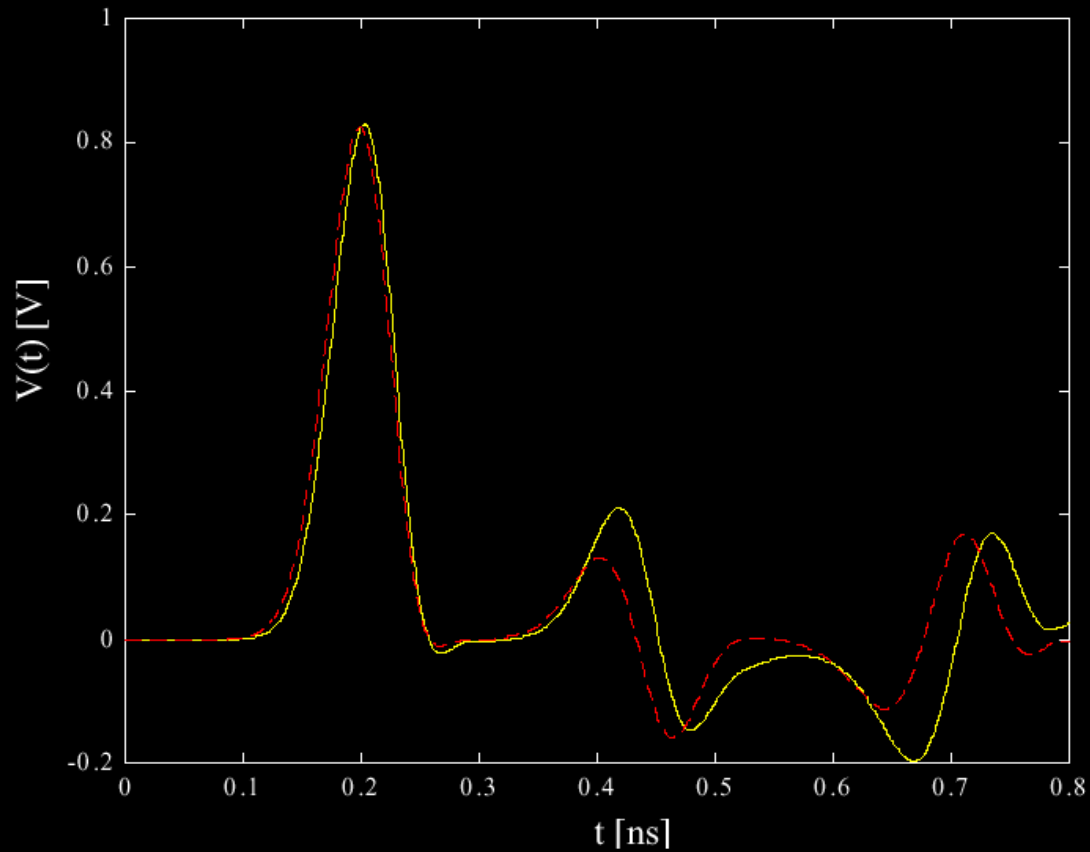


Output side


## Signal Quality: Single vs. Diff. (O)

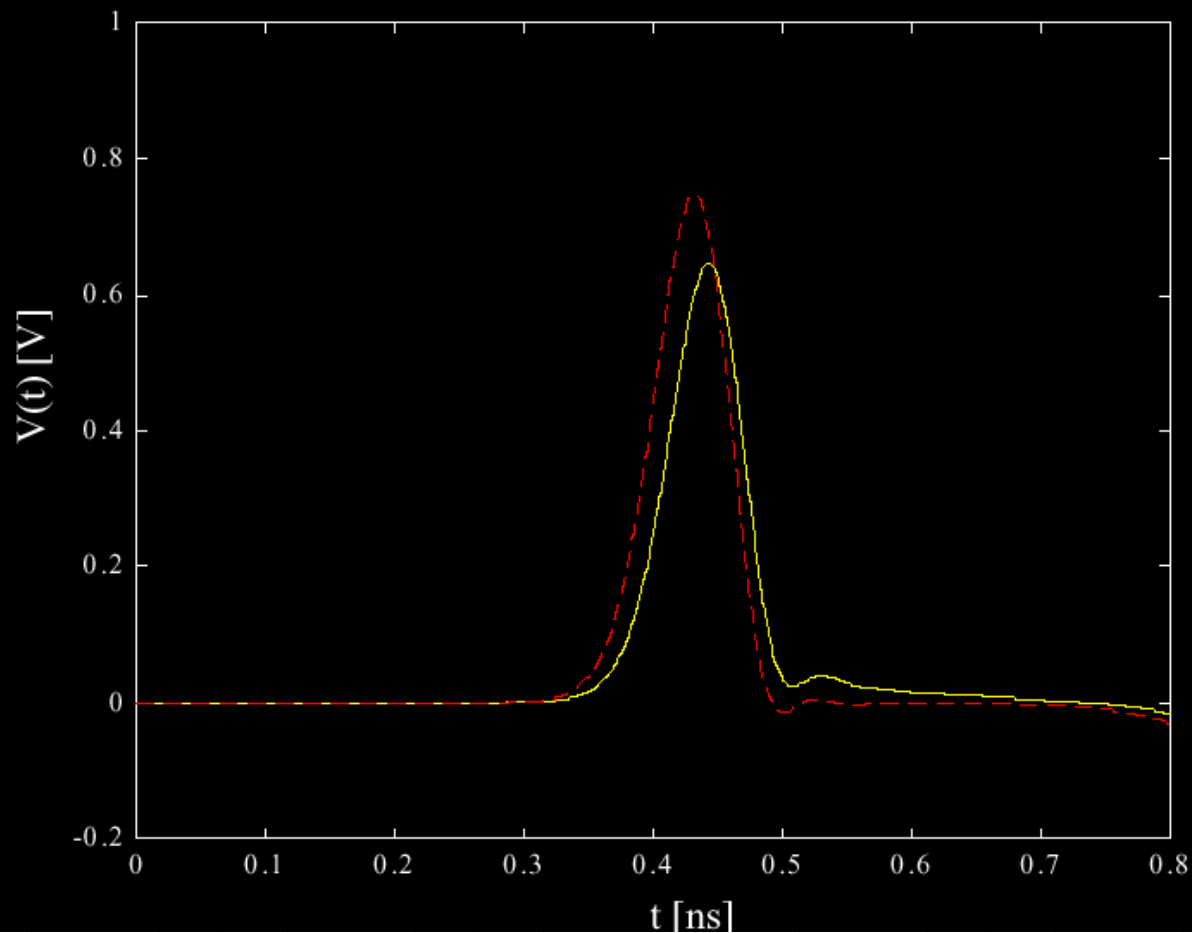


## EM Radiation: Single vs. Diff.

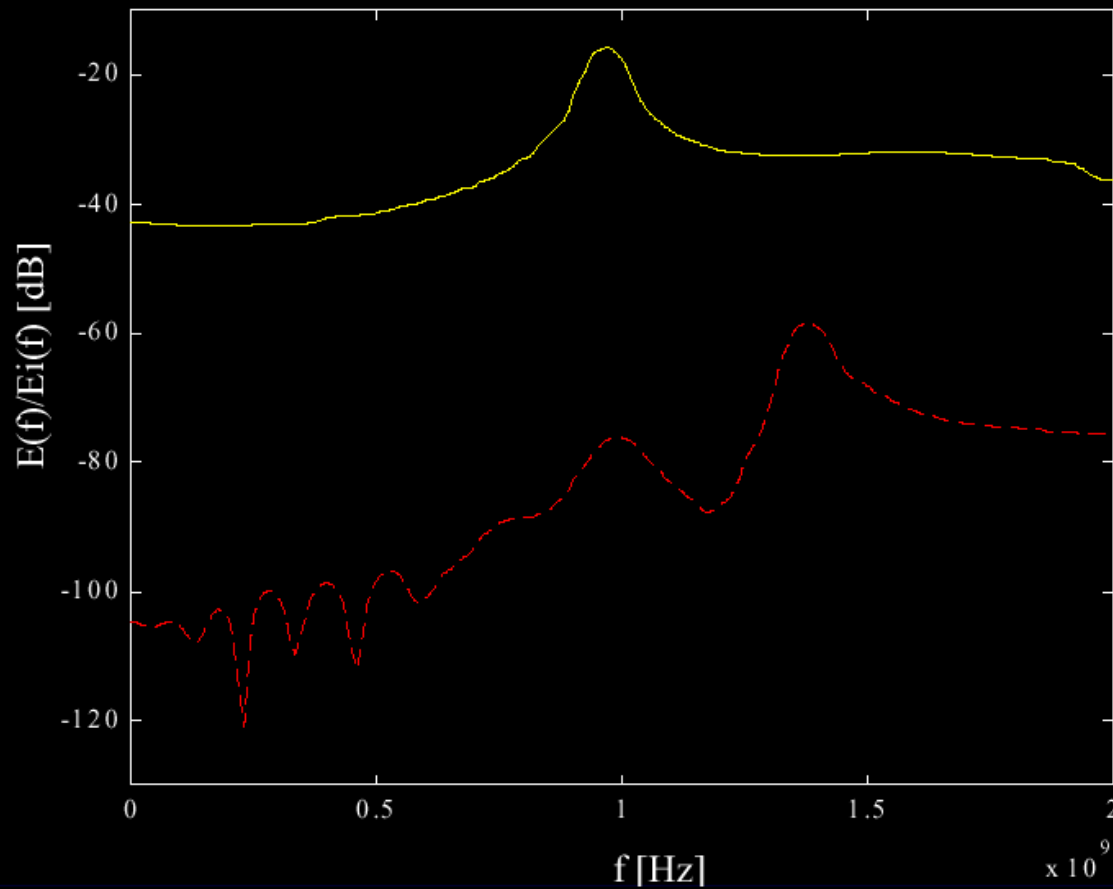

# Signal Quality: Tighter Coupling


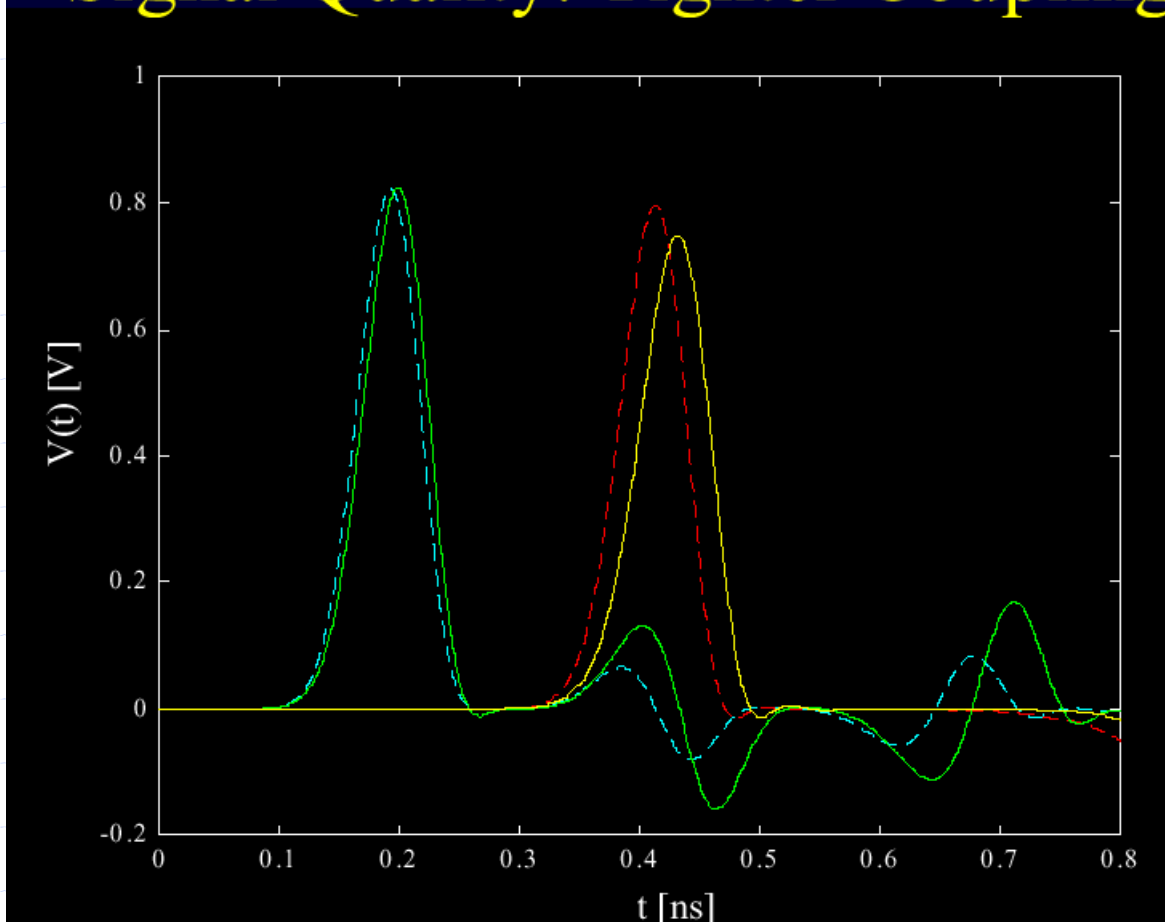


# EM Radiation: Tighter Coupling

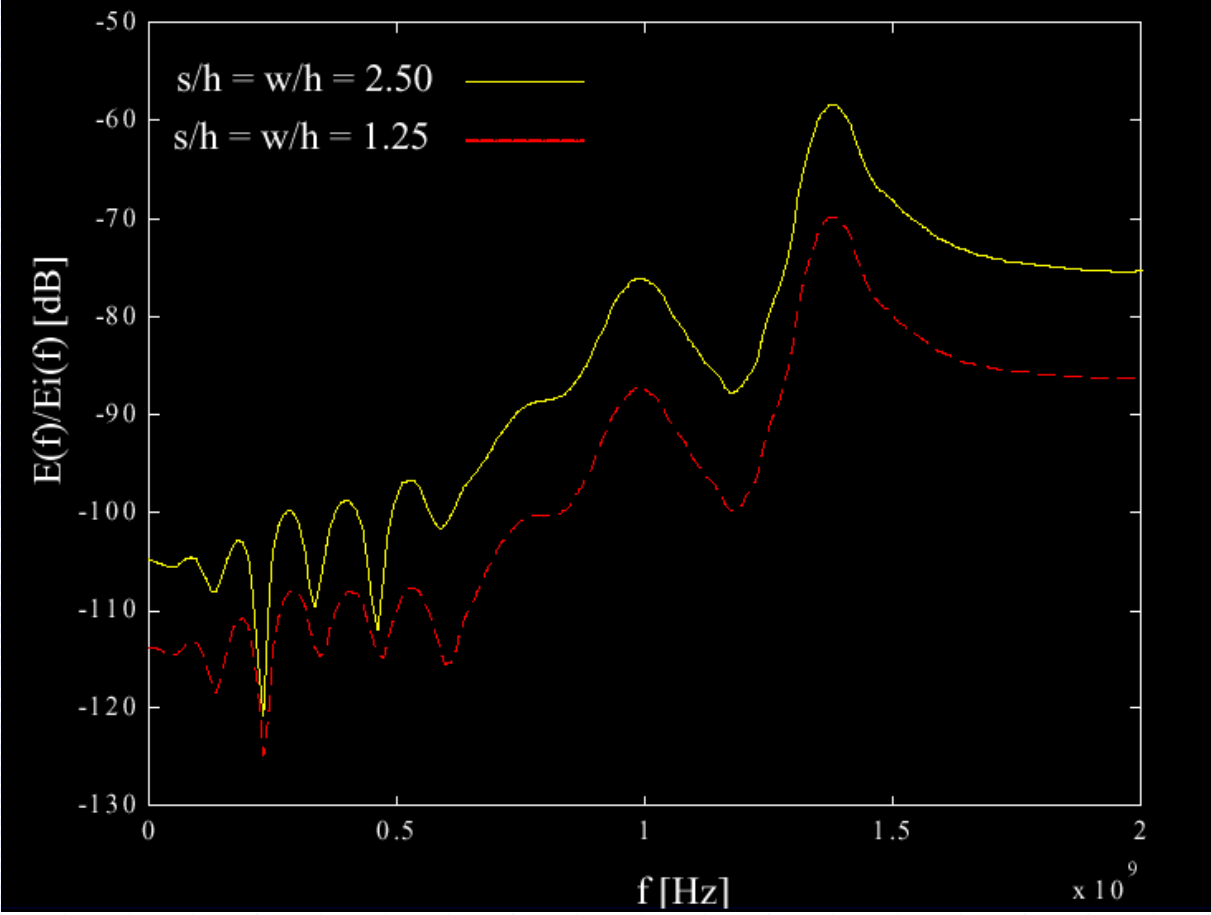

# Example: Rambus RDRAM and RIMM Design

## RDRAM Signal Routing

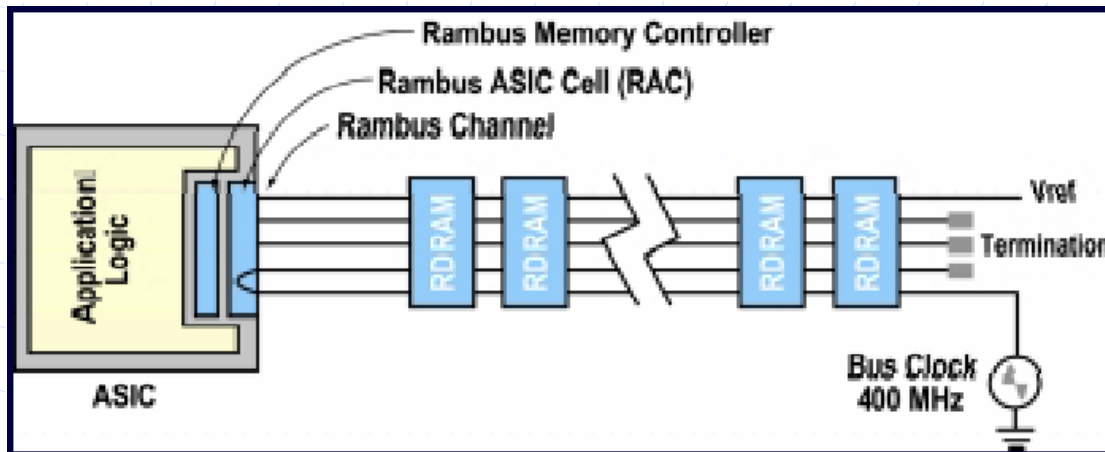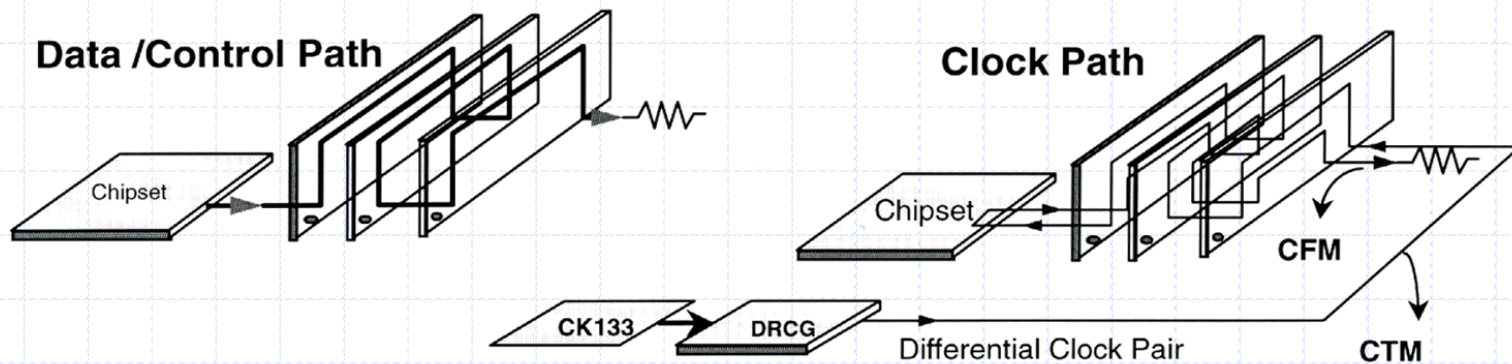

# Example: Rambus RDRAM and RIMM Design

- Power:

$V_{DD} = 2.5V$ ,  $V_{term} = 1.8V$ ,  $V_{ref} = 1.4V$

- Signal:

0.8V Swing: Logic 0 -> 1.8V, Logic 1 -> 1.0V

2x400MHz CLK: 1.25ns timing window, 200ps rise/fall time

Timing Skew: only allow 150ps - 200ps


- Rambus channel architecture:

(30 controlled impedance and matched transmission lines)

- Two 9-bit data buses (DQA and DQB)
- A 3-bit ROW bus
- A 5-bit COL bus
- CTM and CFM differential clock buses

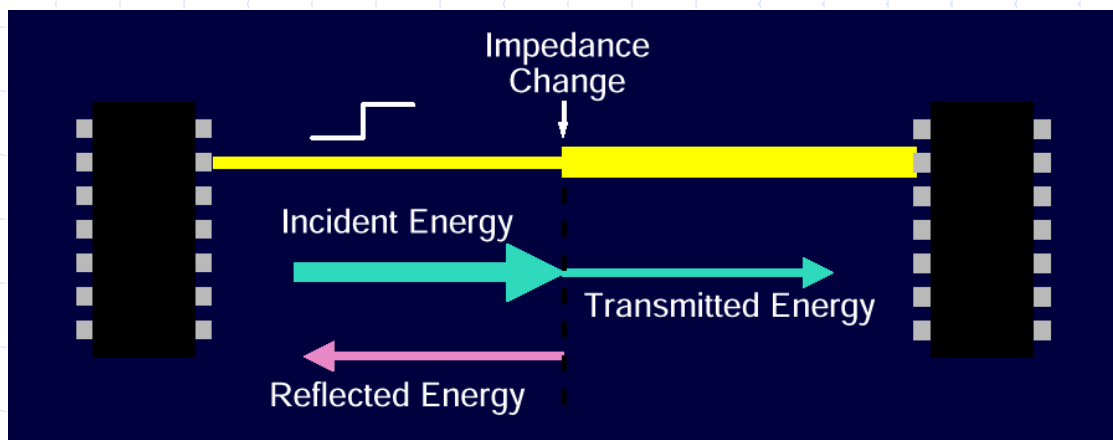
## Example: Rambus RDRAM and RIMM Design

- RDRAM Channel is designed for  $28 \Omega \pm 10\%$
- Impedance mismatch causes signal reflections
- Reflections reduce voltage and timing margins
- PCB process variation  $\rightarrow Z_0$  variation  $\rightarrow$  Channel error




# Example: Rambus RDRAM and RIMM Design

- Intel suggested coplanar structure

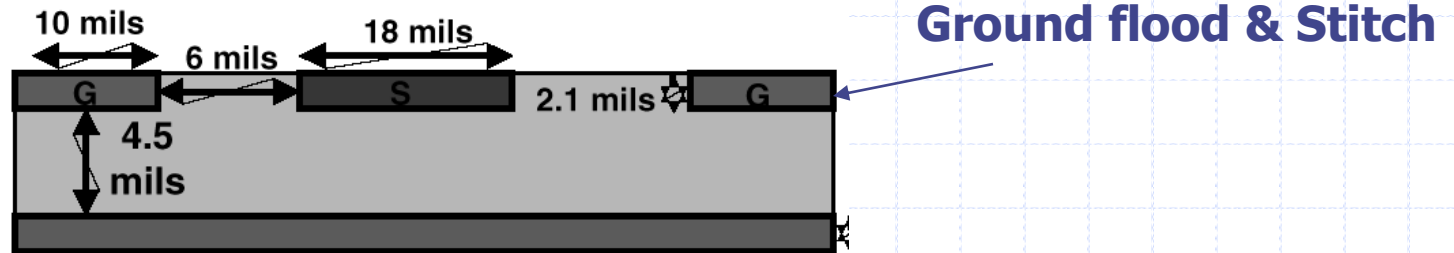

- Intel suggested strip structure

RIMM 282 (UNLOADED)

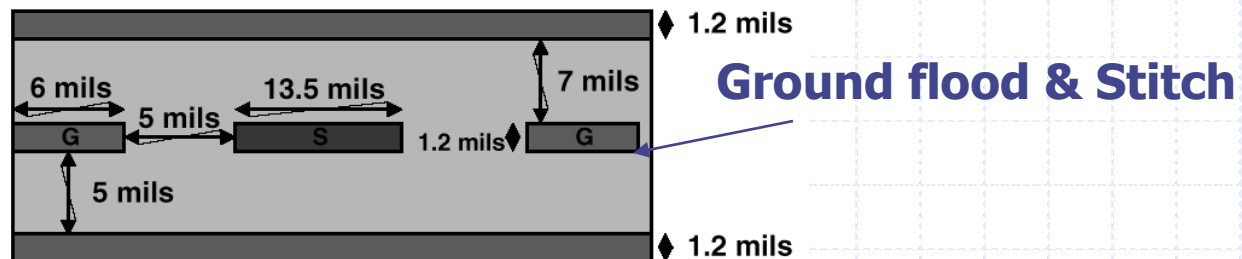


# Example: Rambus RDRAM and RIMM Design

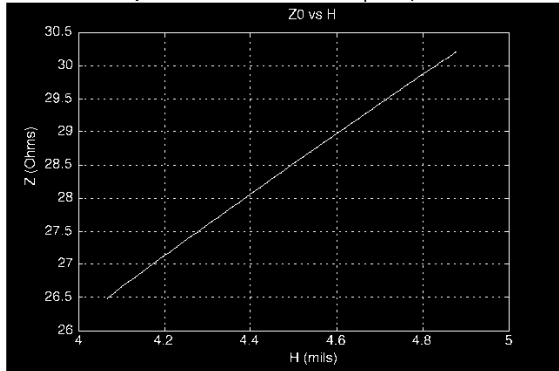
## PCB Parameter sensitivity:

- H tolerance is hardest to control
- W & T have less impact on  $Z_0$


**Z0 vs H** (W=18mils, T=1.4mils,  $\epsilon_r=4.5$ )



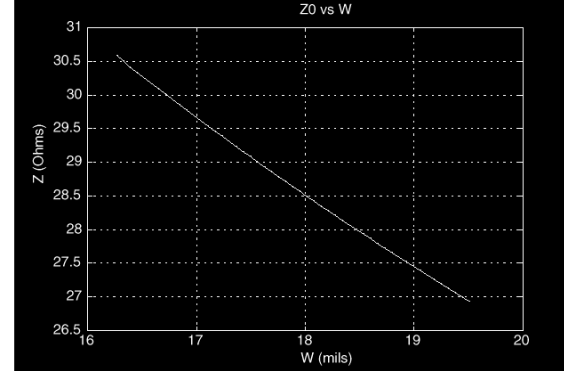
**Z0 vs W** (H=4.5mils, T=1.4mils,  $\epsilon_r=4.5$ )



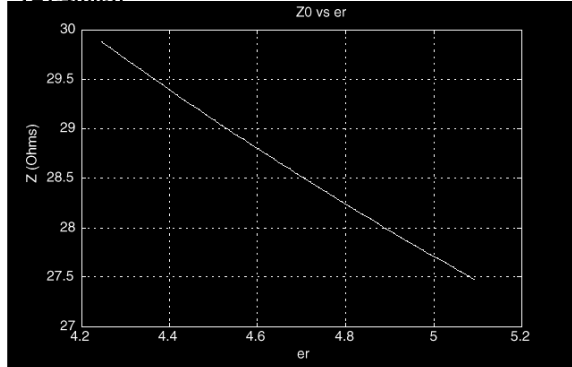**Z0 vs  $\epsilon_r$**  (H=4.5mils, W=18mils, T=1.4mils)




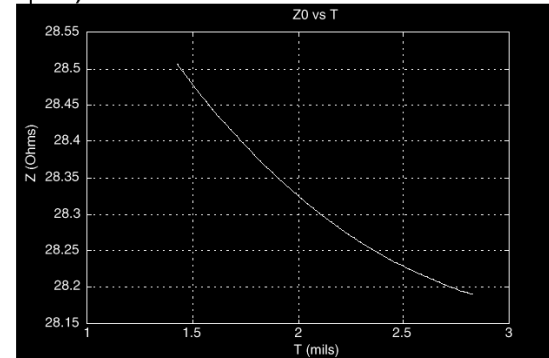**Z0 vs T** (H=4.5mils, W=18mils,  $\epsilon_r=4.5$ )


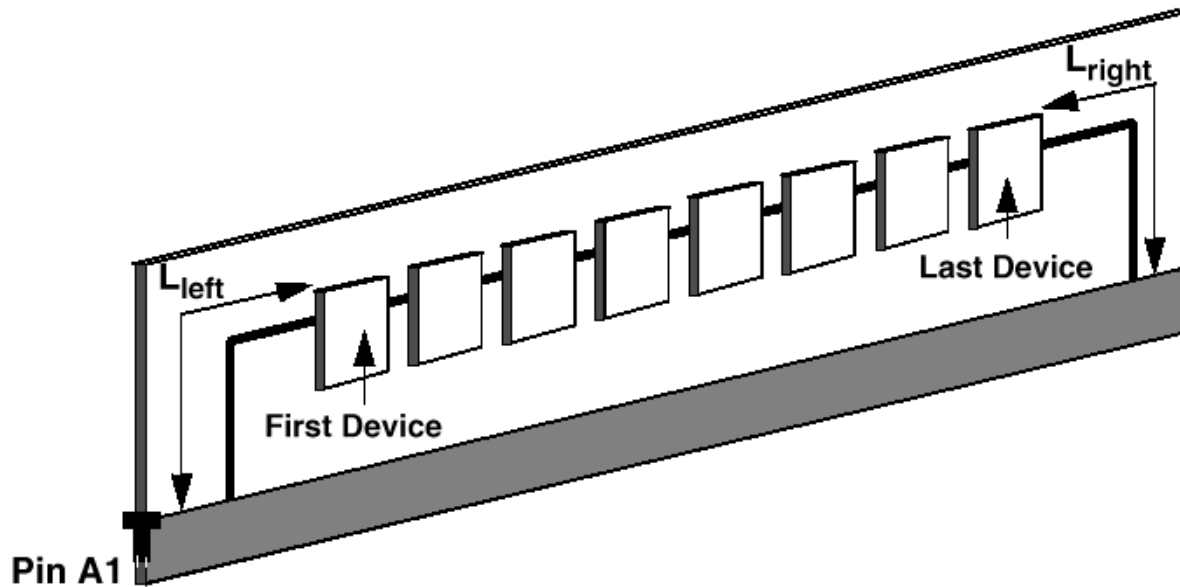
# Example: Rambus RDRAM and RIMM Design

- How to design Rambus channel in *RIMM Module* with uniform  $Z_0 = 28 \text{ ohm}$  ??
- How to design Rambus channel in *RIMM Module* with propagation delay variation in  $\pm 20\text{ps}$  ??



# Example: Rambus RDRAM and RIMM Design

## Impedance Control: (Why?)


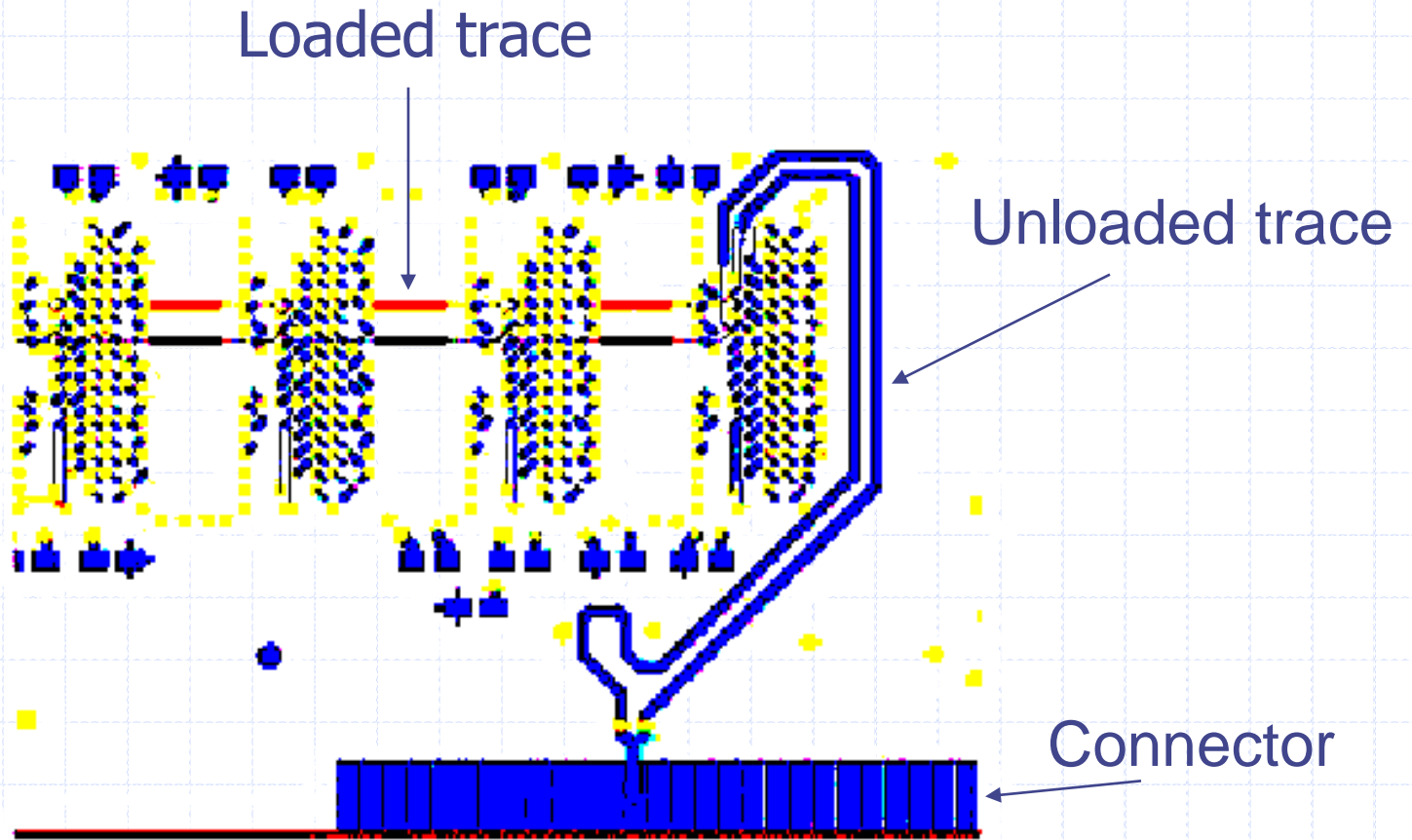


Figure 5-12: High-Speed CMOS Signal Routing

# Example: Rambus RDRAM and RIMM Design

## Multi-drop Buses

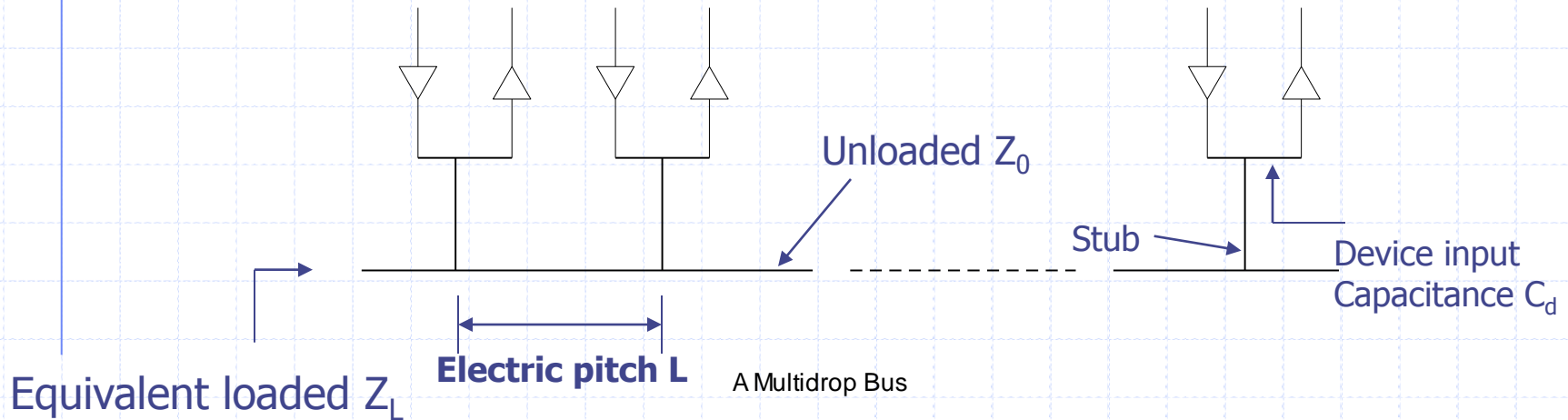


$$Z_L = \sqrt{\frac{L_0}{C_T}} = \sqrt{\frac{L_0}{\frac{C_L}{L} + \frac{L_0}{Z_0^2}}} = 28\Omega \text{ (for Rambus design)}$$

where  $C_T$  is the per - unit - length equivalent capacitance at length  $L$ , including the loading capacitance and the unloaded trace capacitance  
 $C_L$  is the loading capacitance including the device input capacitance  $C_d$ , the stub trace capacitance, and the via effect.
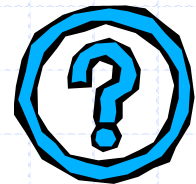
# Example: Rambus RDRAM and RIMM Design

In typical RIMM module design

$C_L = 0.2\text{pF} + 0.1\text{pF} + 2.2\text{pF}$ , and  
 If you design unloaded trace  $Z_0 = 56\Omega$   
 the electric pitch  $L = 7.06\text{mm}$  to reach loaded  $Z_L = 28\Omega$



$$\therefore L_0 = Z_0 \tau = 56\Omega \times 6.77 \text{ psec} / \text{mm} = 379 \text{ pH} / \text{mm} = 9.5 \text{ pH} / \text{mil}$$

$$C_T = \frac{C_L}{L} + \frac{L_0}{Z_0^2} = \frac{2.5\text{pF}}{7.06\text{mm}} + \frac{379 \text{ pH} / \text{mm}}{56\Omega^2} = 0.475 \text{ pF} / \text{mm}$$

$$\therefore Z_L = \sqrt{\frac{L_0}{C_T}} = 28.3\Omega$$

# Example: Rambus RDRAM and RIMM Design

- Modulation trace

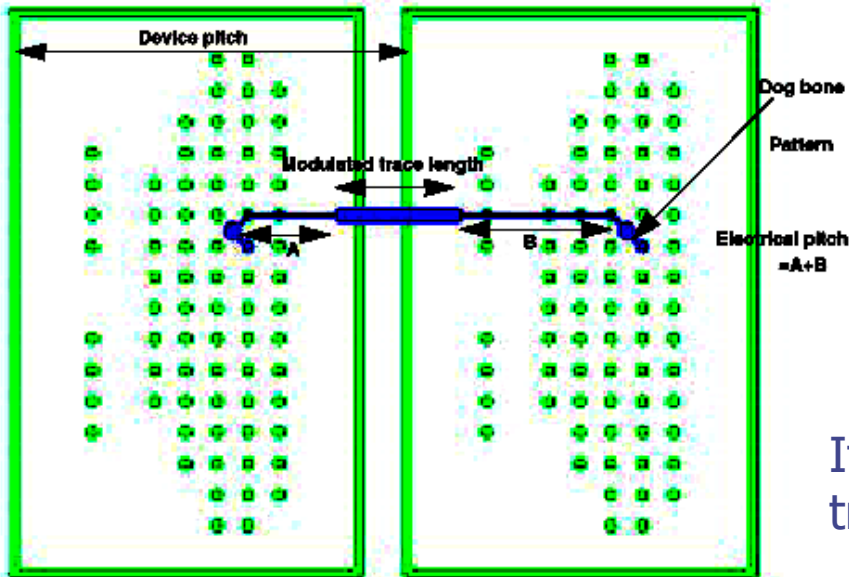


Figure 5-5: 8 Device Single-Sided Edge-Bonded Module Device and Electrical Pitch

**Device pitch** = Device height + Device space

**Electrical pitch** L is designed as


$$L = \frac{C_L Z_L^2}{\frac{\tau}{Z_0} (Z_0^2 - Z_L^2)}$$

If device pitch > electric pitch, modulation trace of 28ohm should be used.

**Modulation trace length**  
= **Device pitch** – **Electric pitch**
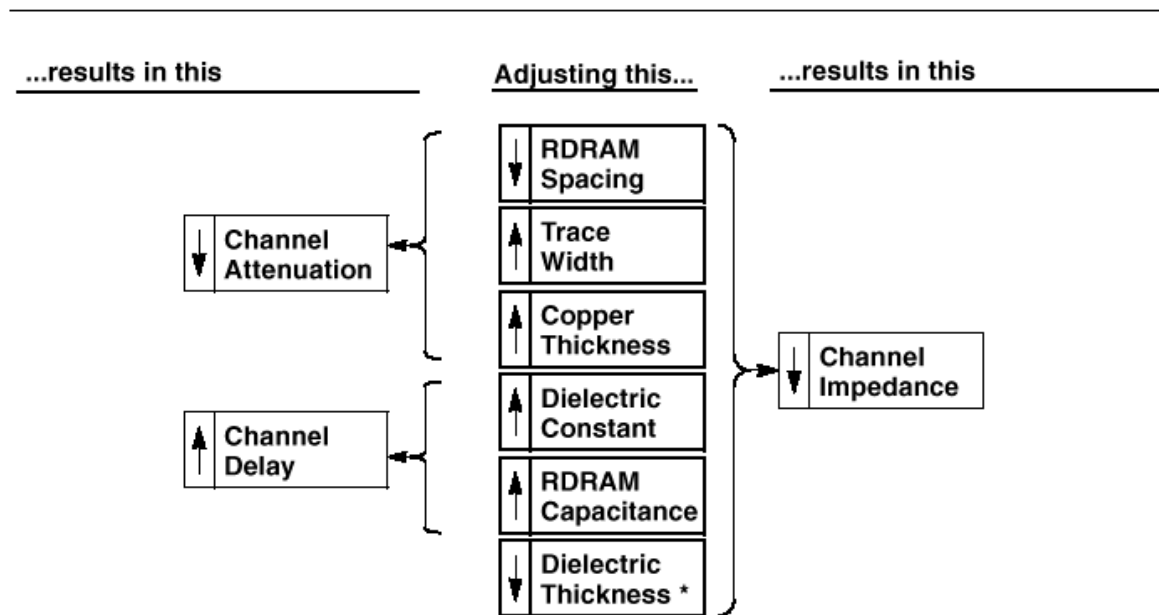
# Example: Rambus RDRAM and RIMM Design

- Effect of PCB parameter variations on three key module electric characteristics



\*: affects attenuation and delay indirectly

Figure 2-3: PCB Design Parameter Relationships

# Example: Rambus RDRAM and RIMM Design

- Controlling propagation delay:
  - *Bend compensation*
  - *Via Compensation*
  - *Connector compensation*

## Bend Compensation

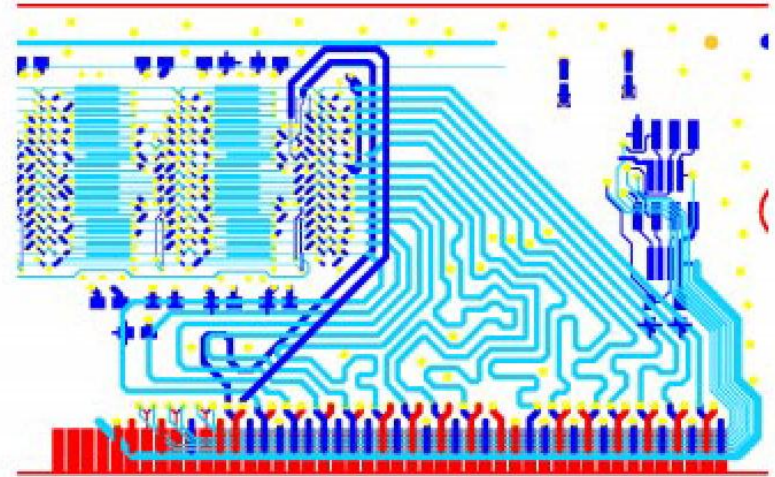


Figure 5-11: Delay Matching (Right Side)

- Rule of thumb: 0.3ps faster delay of every bend
- Solving strategies:
  1. Using same numbers of bends for those critical traces(difficult)
  2. Compensate each bend by a 0.3ps delay line.

# Example: Rambus RDRAM and RIMM Design

## Via Compensation (delay)

For a 8 layers PCB, a via with 50mil length can be modeled as (L, C) = (0.485nH, 0.385pF).

$$\therefore \text{Delay } T_0 = \sqrt{LC} = 13.7 \text{ psec}$$

$$\text{Impedance } Z_0 = \frac{1}{\sqrt{LC}} \approx 38\Omega \quad \leftarrow \text{ Inductive}$$

Rule of thumb: delay of a specific via depth can be calculated by scaling the inductance value which is proportional to via length.

$$\therefore 30\text{mil via has delay } \approx 13.7 \times \sqrt{\frac{30\text{mil}}{50\text{mil}}} = 10.6 \text{ psec}$$


This delay difference can be compensated by adding a 1.566mm to the unloaded trace (56Ω)



# Example: Rambus RDRAM and RIMM Design


## Via Compensation (impedance)
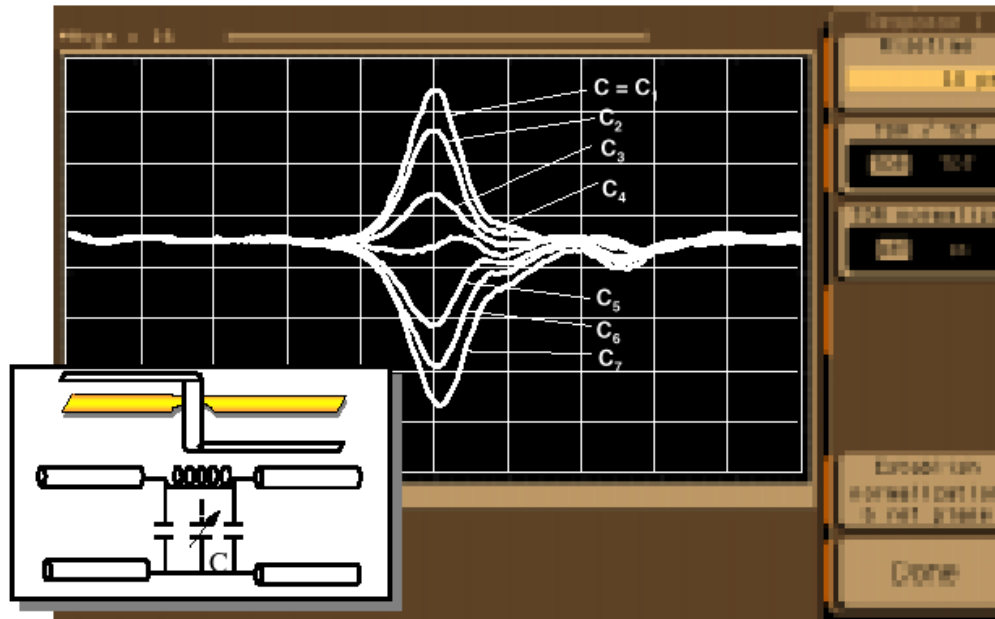
### Compensation and Overcompensation at a Via



# Example: Rambus RDRAM and RIMM Design

## Connector Compensation

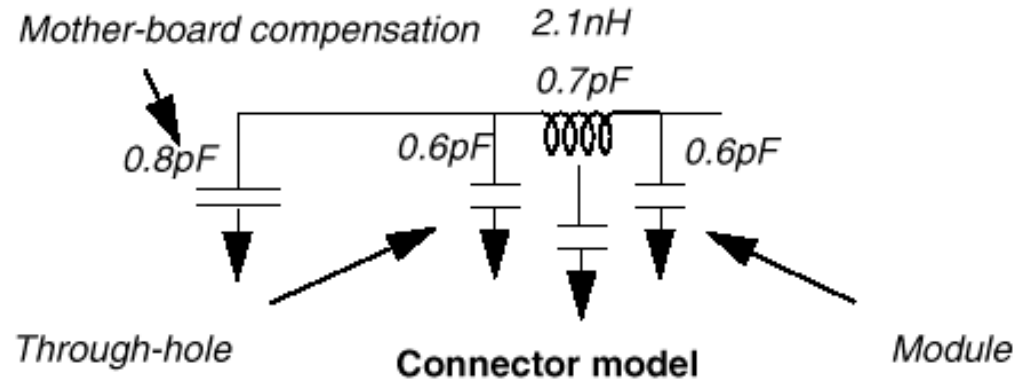

$$C_{\text{pin}} = 0.7\text{ pF}, C_{\text{via}} = 0.6\text{ pF}, C_{\text{pad}} = 0.6\text{ pF}, C_{\text{mb}} = 0.8\text{ pF} \Rightarrow C_{\text{total}} = 2.7\text{ pF}$$

$$L_{\text{pin}} = 2.1\text{ nH}$$

$$Z = \sqrt{L_{\text{pin}} / C_{\text{total}}} = 27.9\Omega$$

# Example: EMI resulting from a trace near a PCB edge

## Experiment setup and trace design

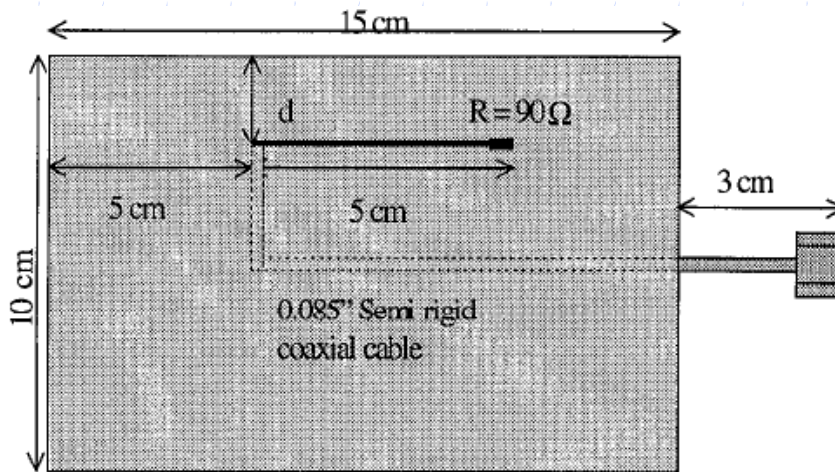



Figure 1: Geometry of PCB layout.

Table 1. Comparison of height above PCB reference plane and trace proximity to board edge ( $d$ ).

Height (mils)	$d$ (mils)	$d/h$	Termination
45	25	0.55	90 $\Omega$
45	75	1.67	90 $\Omega$
45	275	6.11	90 $\Omega$
45	575	12.8	90 $\Omega$
45	1956 (centered)	43.5	90 $\Omega$
90	1956 (centered)	21.7	116 $\Omega$
22	1956 (centered)	88.9	60 $\Omega$
22	25	1.14	60 $\Omega$

# Example: EMI resulting from a trace near a PCB edge


## Measurement Setup

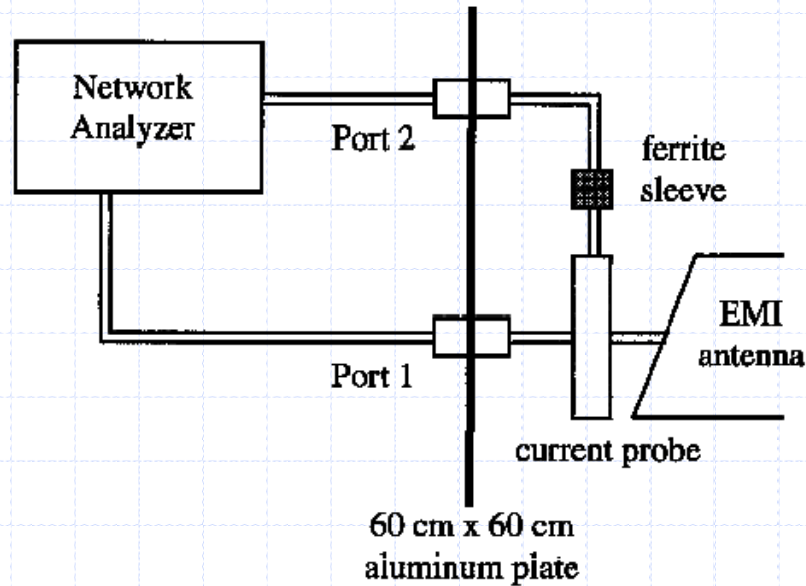

**Figure 2: Test setup for measuring the  $|S_{21}|$  with a current probe.**

# Example: EMI resulting from a trace near a PCB edge

EMI caused by Common-mode current : **magnetic coupling**  
 Measured by current probe

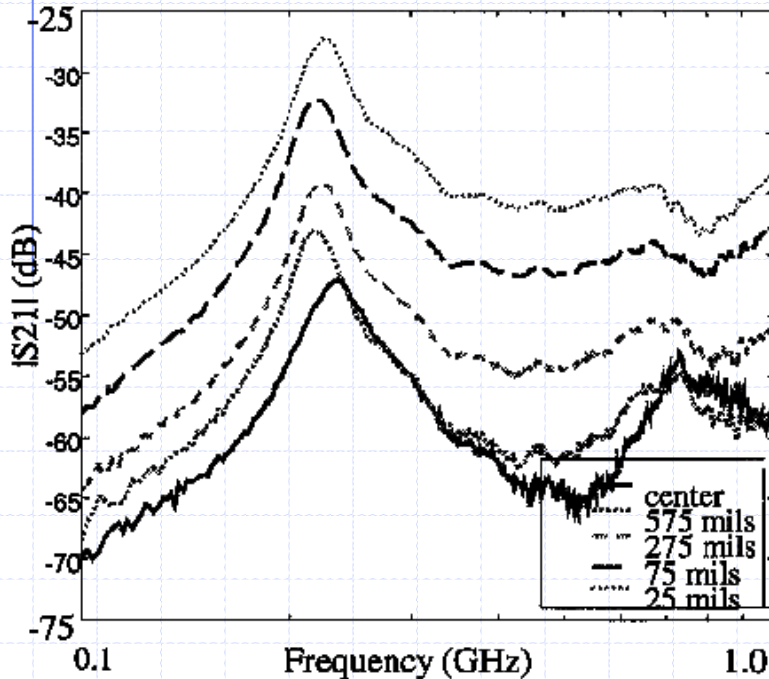

**Table 2. Increase in |S<sub>21</sub>| as the trace nears the PCB edge. The reference is a centered trace.**

Distance from Edge (d)	Δ S <sub>21</sub>   (dB)
25 mils.	17.6
75 mils.	13.1
275 mils.	6.61
475 mils.	3.33

**Figure 3: |S<sub>21</sub>| measurements with a current probe.**

## Example: EMI resulting from a trace near a PCB edge

EMI measured by the monopole : E field


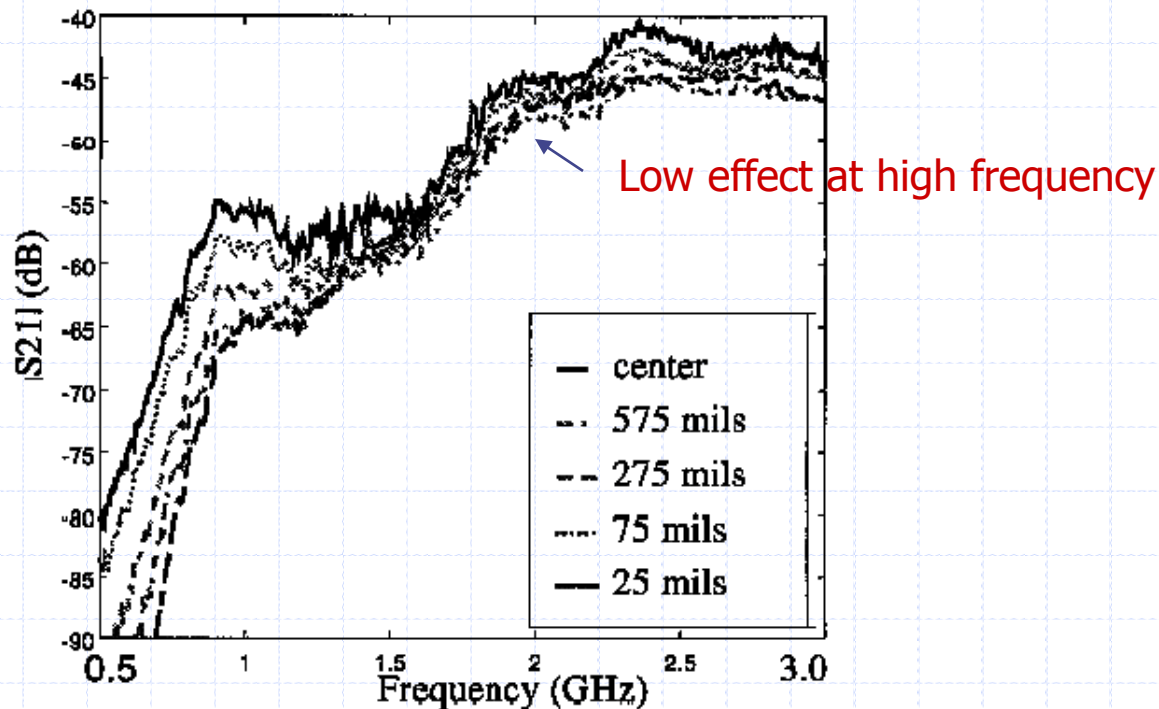


Figure 4:  $|S_{21}|$  measurements using a 3 cm monopole probe.

# Example: EMI resulting from a trace near a PCB edge

## Trace height effect on EMI

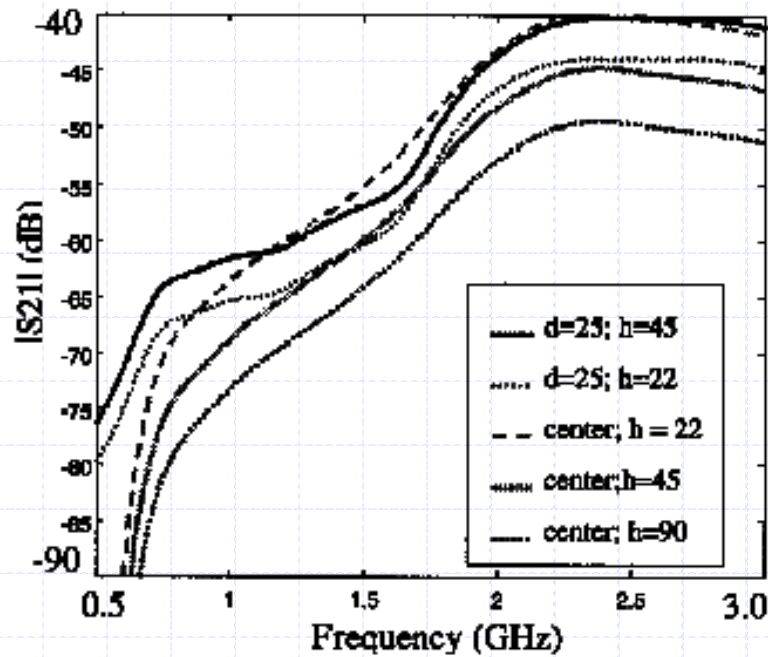

**Figure 8: Comparison of the near-electric field radiation for different trace heights above the reference plane for a centered trace, and trace 25 mils from edge.**

# Reference

1. Howard W. Johnson, “High-speed digital design”, Prentice-Hall, 1993
2. Ron K. Poon, “Computer Circuits Electrical Design”, Prentice-Hall, 1995
3. David M. Pozar, “Microwave Engineering”, John Wiley & Sons, 1998
4. William J. Dally, “Digital System Engineering”, Cambridge, 1998
5. Rambus, “Direct Rambus RIMM Module Design Guide, V. 0.9”, 1999