

Lecture 3 Terminated Transmission Line

1. Voltage, Current and Input Impedance of A Terminated Line
2. Input Reflection Coefficient and Input Impedance
3. Matched Load, Short-circuit Load and Open-circuit Load
4. Quarter-wave Transformer
5. Voltage Standing Wave Ratio
6. Transmission Line with A Source and A Load
7. Reflected Power and Delivered Power
8. Code Example

1. Voltage, Current and Input Impedance of A Terminated Line

$$V(z) = V_0^+ e^{-\gamma z} + V_0^- e^{+\gamma z}$$


Ampl. of voltage wave
propagating in positive z
direction at $z = 0$.

Ampl. of voltage wave
propagating in negative z
direction at $z = 0$.


$$V(z) = V^+(z) + V^-(z)$$

$$V^+(z) = V_0^+ e^{-\gamma z}$$

$$V^-(z) = V_0^- e^{+\gamma z}$$

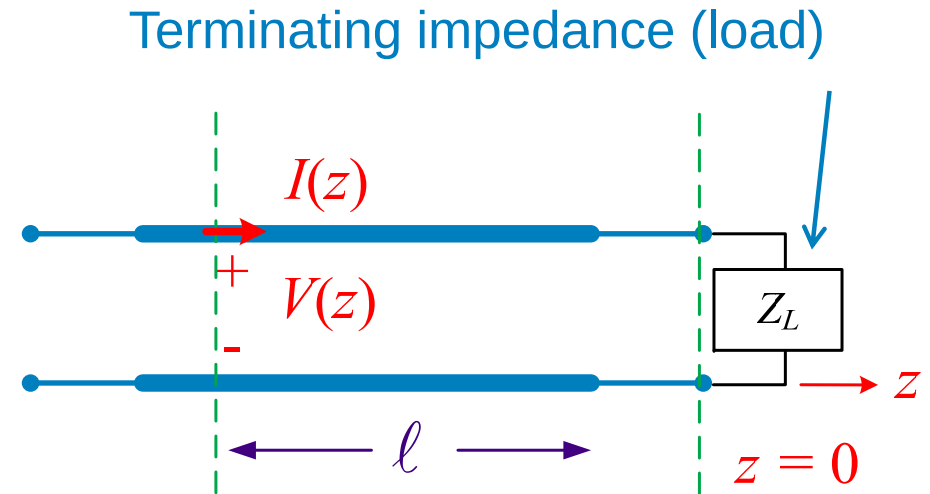

Understanding the wave propagation

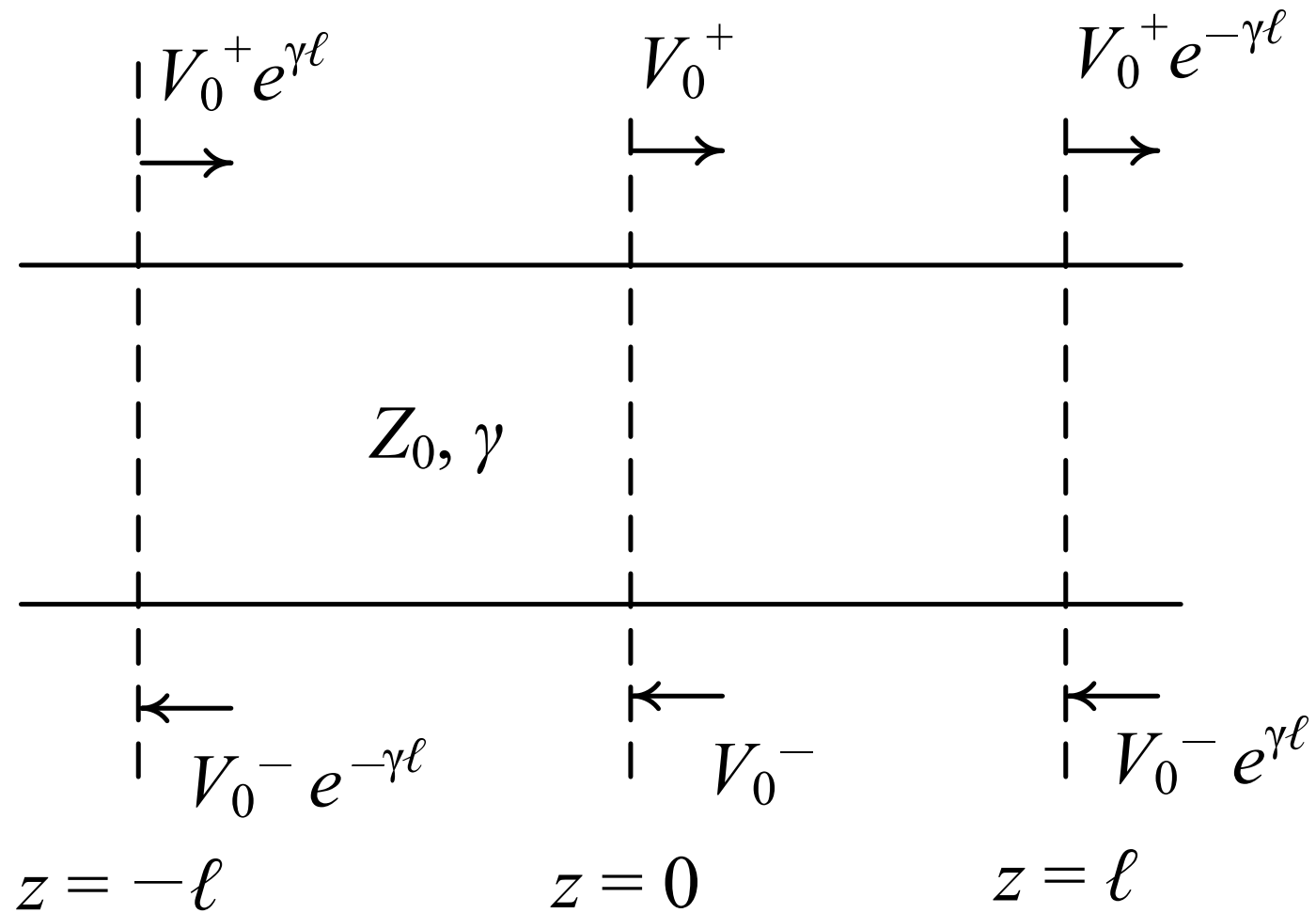

Voltage and current:


$$V(z) = V_0^+ e^{-\gamma z} + V_0^- e^{+\gamma z}$$

What is $V(-\ell)$?

$$V(-\ell) = V_0^+ e^{\gamma \ell} + V_0^- e^{-\gamma \ell}$$

propagating
forwards

propagating
backwards

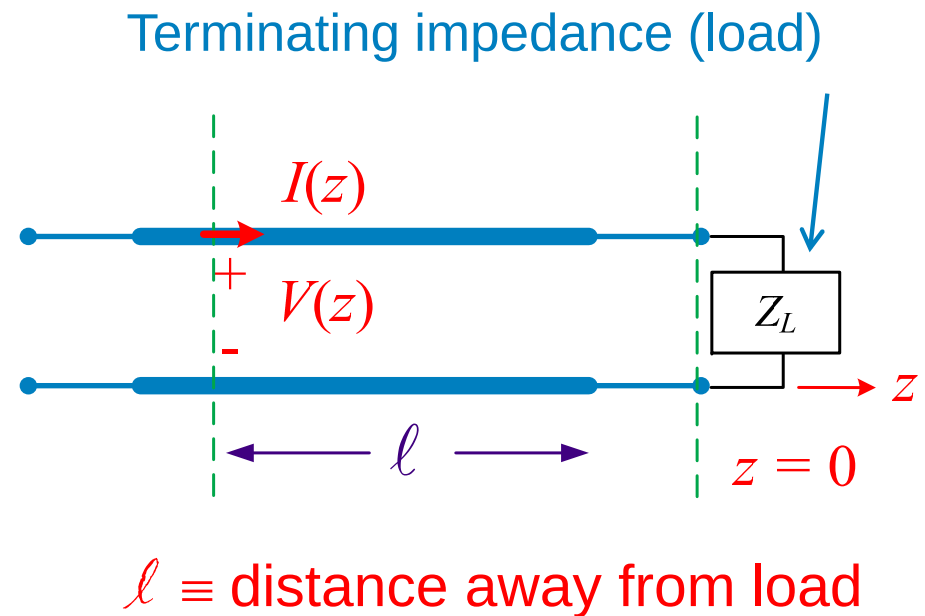


The current at $z = -\ell$ is then

$$I(-\ell) = \frac{V_0^+}{Z_0} e^{\gamma \ell} - \frac{V_0^-}{Z_0} e^{-\gamma \ell}$$

from

$$\frac{dV(z)}{dz} = -(R + j\omega L)I(z),$$

Load reflection coefficient:

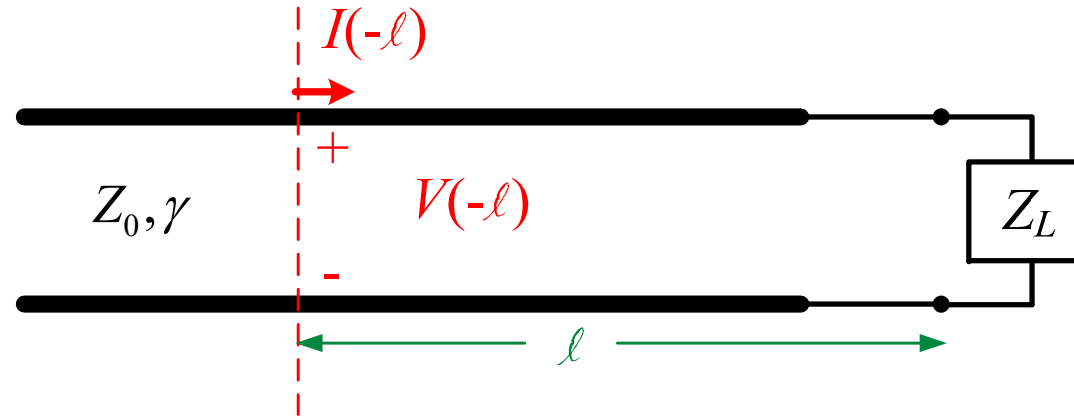

Total volt. at distance ℓ from the load

$$V(-\ell) = V_0^+ e^{\gamma\ell} + V_0^- e^{-\gamma\ell} = V_0^+ e^{\gamma\ell} \left(1 + \underbrace{\frac{V_0^-}{V_0^+}}_{\Gamma_L} e^{-2\gamma\ell} \right)$$

Ampl. of volt. wave prop. towards load, at the load position ($z = 0$).

Ampl. of volt. wave prop. away from load, at the load position ($z = 0$).

$\Gamma_L \equiv$ Load reflection coefficient


$\Gamma_\ell \equiv$ Reflection coefficient at $z = -\ell$

$$= V_0^+ e^{\gamma\ell} (1 + \Gamma_L e^{-2\gamma\ell})$$

Similarly,

$$I(-\ell) = \frac{V_0^+}{Z_0} e^{\gamma\ell} (1 - \Gamma_L e^{-2\gamma\ell})$$

Input impedance:

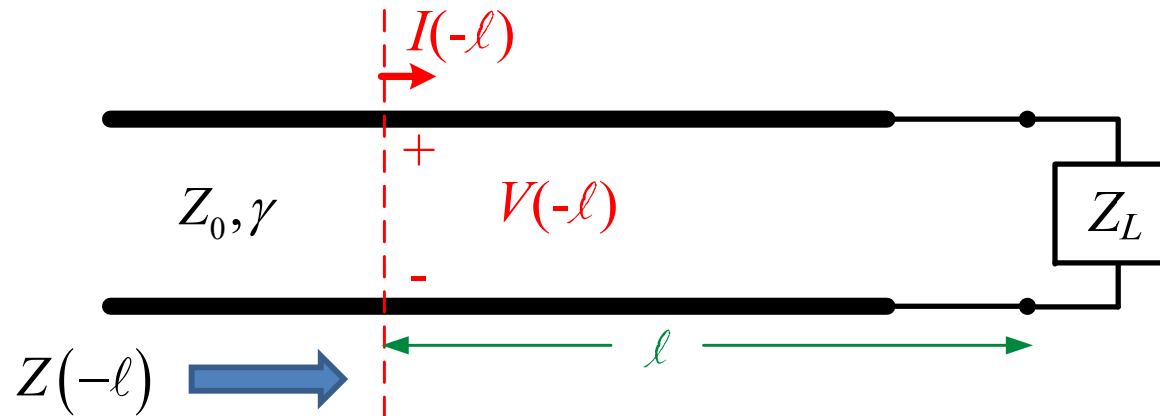

$$V(-\ell) = V_0^+ e^{\gamma \ell} (1 + \Gamma_L e^{-2\gamma \ell})$$

$$I(-\ell) = \frac{V_0^+}{Z_0} e^{\gamma \ell} (1 - \Gamma_L e^{-2\gamma \ell})$$

$$Z(-\ell) = \frac{V(-\ell)}{I(-\ell)} = Z_0 \left(\frac{1 + \Gamma_L e^{-2\gamma \ell}}{1 - \Gamma_L e^{-2\gamma \ell}} \right)$$

Input impedance seen “looking” towards load at $z = -\ell$.

At the load ($\ell = 0$):

$$Z(0) = Z_0 \left(\frac{1 + \Gamma_L}{1 - \Gamma_L} \right) \equiv Z_L$$

$$\Rightarrow \Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0}$$

Reflection Coefficient

$$\Gamma = \Gamma_r + j\Gamma_i$$

$$0 \leq |\Gamma| \leq 1 \quad \text{if } \operatorname{Re}(Z_L) \geq 0 \text{ (passive load)}$$

$$|\Gamma| = 0 \text{ if } Z_L = Z_0 : \text{no reflection}$$

$$|\Gamma| = 1 \text{ if } Z_L = 0 \text{ (short), } \infty \text{ (open), } jX \text{ (reactive) : total reflection}$$

$$|\Gamma| \text{ (dB)} = -20 \log_{10} |\Gamma|$$

$$\text{RL (return loss)} = 20 \log_{10} |\Gamma|$$

At the load ($\ell = 0$):

$$Z(0) = Z_0 \left(\frac{1 + \Gamma_L}{1 - \Gamma_L} \right) \equiv Z_L \quad \Rightarrow \quad \Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0}$$

Recall

$$Z(-\ell) = Z_0 \left(\frac{1 + \Gamma_L e^{-2\gamma\ell}}{1 - \Gamma_L e^{-2\gamma\ell}} \right)$$

Thus,

$$Z(-\ell) = Z_0 \left(\frac{1 + \left(\frac{Z_L - Z_0}{Z_L + Z_0} \right) e^{-2\gamma\ell}}{1 - \left(\frac{Z_L - Z_0}{Z_L + Z_0} \right) e^{-2\gamma\ell}} \right)$$

Simplifying, we have

$$\begin{aligned} Z(-\ell) &= Z_0 \left(\frac{1 + \left(\frac{Z_L - Z_0}{Z_L + Z_0} \right) e^{-2\gamma\ell}}{1 - \left(\frac{Z_L - Z_0}{Z_L + Z_0} \right) e^{-2\gamma\ell}} \right) = Z_0 \left(\frac{(Z_L + Z_0) + (Z_L - Z_0) e^{-2\gamma\ell}}{(Z_L + Z_0) - (Z_L - Z_0) e^{-2\gamma\ell}} \right) \\ &= Z_0 \left(\frac{(Z_L + Z_0) e^{+\gamma\ell} + (Z_L - Z_0) e^{-\gamma\ell}}{(Z_L + Z_0) e^{+\gamma\ell} - (Z_L - Z_0) e^{-\gamma\ell}} \right) \\ &= Z_0 \left(\frac{Z_L \cosh(\gamma\ell) + Z_0 \sinh(\gamma\ell)}{Z_0 \cosh(\gamma\ell) + Z_L \sinh(\gamma\ell)} \right) \end{aligned}$$

sinh: 싸인에이취

Hence, we have

$$Z(-\ell) = Z_0 \left(\frac{Z_L + Z_0 \tanh(\gamma\ell)}{Z_0 + Z_L \tanh(\gamma\ell)} \right)$$

$$\gamma = \cancel{\alpha} + j\beta = j\beta$$


$$V(-\ell) = V_0^+ e^{j\beta\ell} (1 + \Gamma_L e^{-2j\beta\ell})$$

$$I(-\ell) = \frac{V_0^+}{Z_0} e^{j\beta\ell} (1 - \Gamma_L e^{-2j\beta\ell})$$

$$Z(-\ell) = Z_0 \left(\frac{1 + \Gamma_L e^{-2j\beta\ell}}{1 - \Gamma_L e^{-2j\beta\ell}} \right)$$

$$Z(-\ell) = Z_0 \left(\frac{Z_L + jZ_0 \tan(\beta\ell)}{Z_0 + jZ_L \tan(\beta\ell)} \right)$$

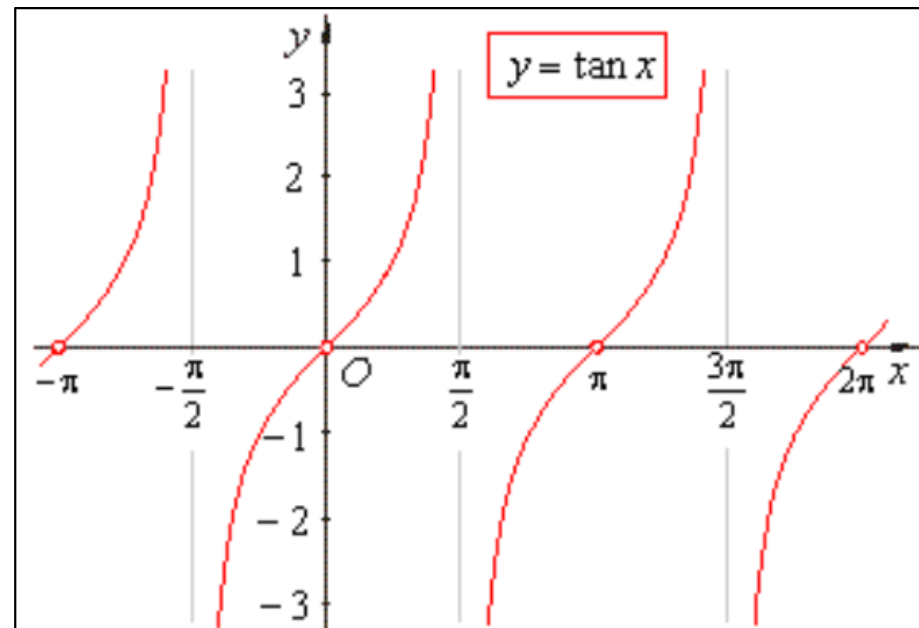Note: $\tanh(\gamma\ell) = \tanh(j\beta\ell) = j \tan(\beta\ell)$



Impedance is periodic
with period $\lambda_g/2$

tan repeats when

$$\beta\ell = \pi$$

$$\frac{2\pi}{\lambda_g} \ell = \pi$$


$$\Rightarrow \ell = \lambda_g / 2$$

$$\cos x = \frac{e^{jx} + e^{-jx}}{2} ; \cosh x = \frac{e^x + e^{-x}}{2} ; \cosh(jx) = \cos x$$

$$\sin x = \frac{e^{jx} - e^{-jx}}{2j} ; \sinh x = \frac{e^x - e^{-x}}{2} ; \sinh(jx) = j \sin x$$

$$\tanh x = \frac{\sinh x}{\cosh x} ; \tanh(jx) = \frac{\sinh(jx)}{\cosh(jx)} = \frac{j \sin x}{\cos x} = j \tan x$$

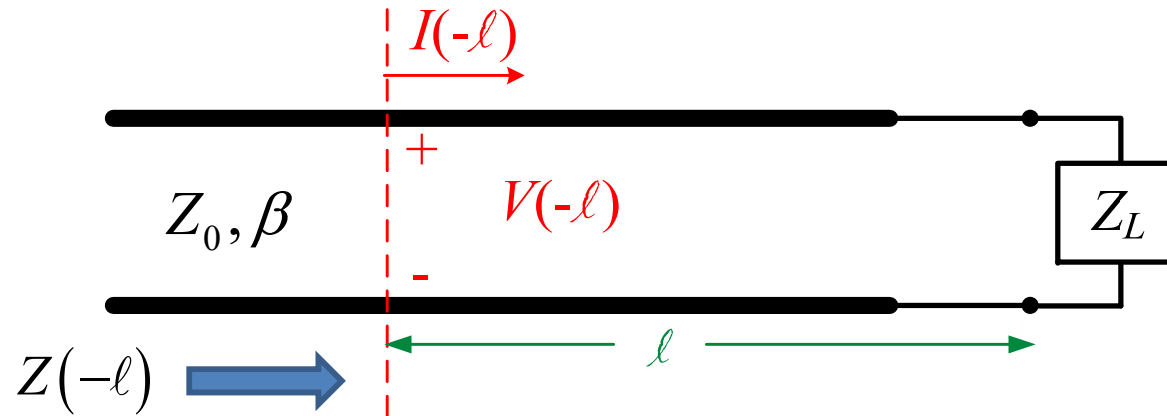For the remainder of our transmission line discussion we will assume that the transmission line is lossless.



$$V(-\ell) = V_0^+ e^{j\beta\ell} (1 + \Gamma_L e^{-2j\beta\ell})$$

$$I(-\ell) = \frac{V_0^+}{Z_0} e^{j\beta\ell} (1 - \Gamma_L e^{-2j\beta\ell})$$


$$\begin{aligned} Z(-\ell) &= \frac{V(-\ell)}{I(-\ell)} = Z_0 \left(\frac{1 + \Gamma_L e^{-2j\beta\ell}}{1 - \Gamma_L e^{-2j\beta\ell}} \right) \\ &= Z_0 \left(\frac{Z_L + jZ_0 \tan(\beta\ell)}{Z_0 + jZ_L \tan(\beta\ell)} \right) \end{aligned}$$

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0}$$

$$\boxed{\lambda_g = \frac{2\pi}{\beta}}$$

$$v_p = \frac{\omega}{\beta}$$

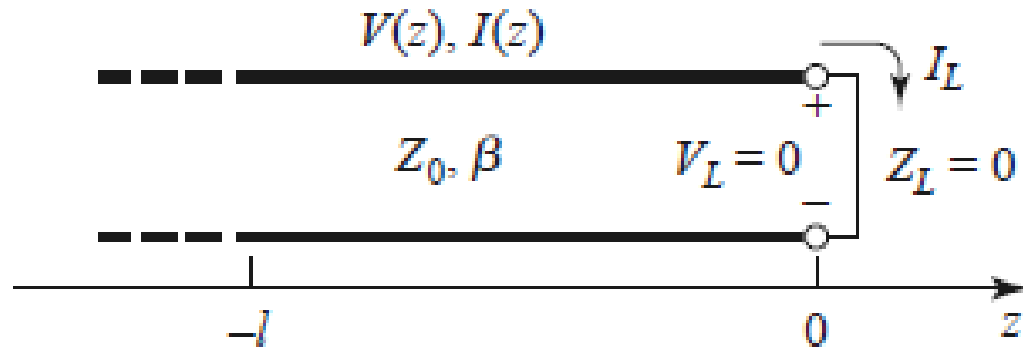2. Input Impedance and Input Reflection Coefficient



$$\Gamma_{\text{in}} = \Gamma(-\ell) = \frac{V_0^- e^{-\gamma \ell}}{V_0^+ e^{\gamma \ell}} = \Gamma(0) e^{-2\gamma \ell}$$

$$\Gamma_{\text{in}} = \Gamma(-\ell) = \frac{V_0^- e^{-j\beta \ell}}{V_0^+ e^{j\beta \ell}} = \Gamma(0) e^{-j2\beta \ell}$$

$$V(-\ell) = V_0^+ (1 + \Gamma_{\text{in}}), \quad I(-\ell) = V_0^+ (1 - \Gamma_{\text{in}}) / Z_0$$

$$\boxed{Z_{\text{in}} = \frac{V(-\ell)}{I(-\ell)} = Z_0 \frac{1 + \Gamma_{\text{in}}}{1 - \Gamma_{\text{in}}}}$$

$$\boxed{\Gamma_{\text{in}} = \frac{Z_{\text{in}} - Z_0}{Z_{\text{in}} + Z_0}}$$

Exercise:

The reflection coefficient at the load is given by $\Gamma_L = 0.8 e^{j45^\circ}$. The line is lossless and has characteristic impedance of 50Ω .

- 1) Find the reflection coefficient at $0.2\lambda_g$ away from the load.
- 2) Find the input impedance at $0.2\lambda_g$ away from the load.

(Solution)

$$1) \Gamma_{in} = \Gamma(0)e^{-j2\beta\ell} = 0.8e^{j45^\circ} e^{-j2(2\pi/\lambda_g)(0.2\lambda_g)} = 0.8e^{j45^\circ} e^{-j0.8\pi} = 0.8e^{-j99^\circ}$$

$$2) Z_{in} = Z_0 \frac{1 + \Gamma_{in}}{1 - \Gamma_{in}} = 50 \frac{1 + 0.8e^{-j90^\circ}}{1 - 0.8e^{-j90^\circ}} = 11.0 - j48.8 \Omega$$

Example: Reflection coefficient and input impedance of a terminated transmission line

Transmission line length $L = 0.1 \lambda_g$; Load impedance $Z_L = 40 + j 70 \Omega$

Characteristic impedance $Z_0 = 50 \Omega$

- 1) Find the input reflection coefficient.
- 2) Find the input impedance from the reflection coefficient.
- 3) Find the input impedance using Z_L and L .

(Solution)

$$1) \Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{40 + j70 - 50}{40 + j70 + 50} = 0.620e^{j60.3^\circ}$$

$$\begin{aligned}\Gamma_{in} &= \Gamma_L e^{-j2\beta L} = 0.620e^{j60.3^\circ} e^{-j2(2\pi/\lambda_g)0.1\lambda_g} = 0.620e^{j60.3^\circ} e^{-j0.4\pi} \\ &= 0.620e^{j60.3^\circ} e^{-j72^\circ} = 0.620e^{-j11.7^\circ}\end{aligned}$$


$$2) Z_{in} = Z_0 \frac{1 + \Gamma_{in}}{1 - \Gamma_{in}} = 50 \frac{1 + 0.620e^{-j11.7^\circ}}{1 - 0.620e^{-j11.7^\circ}} = 180.9 - j73.9 \Omega$$

$$3) Z_{in} = Z_0 \frac{Z_L + jZ_0 \tan \beta \ell}{Z_0 + jZ_L \tan \beta \ell}$$

$$\beta \ell = (2\pi / \lambda_g) 0.1 \lambda_g = 0.2\pi ; \quad \tan(0.2\pi) = 0.723$$

$$Z_{in} = 50 \frac{40 + j70 + j50 \times 0.723}{50 + (40 + j70) \times j0.723} = 50 \frac{40 + j106.2}{-0.61 + j28.9} = 182.2 - j73.0 \Omega$$

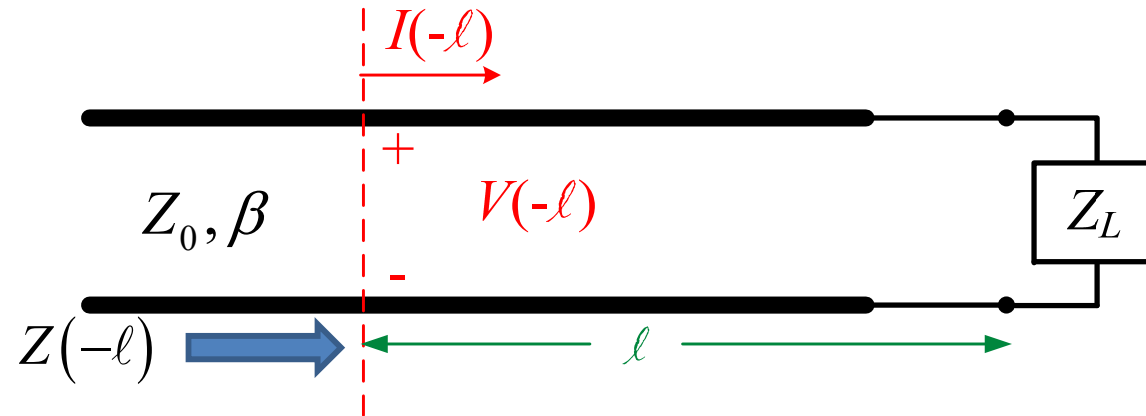3. Matched Load, Short-circuit Load, and Open-circuit Load



(A) Matched load: ($Z_L = Z_0$)

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = 0$$

No reflection from the load

$$\Rightarrow V(-\ell) = V_0^+ e^{+j\beta\ell}$$

$$I(-\ell) = \frac{V_0^+}{Z_0} e^{+j\beta\ell}$$

$$\Rightarrow Z(-\ell) = Z_0$$

For any ℓ


Short-circuit Load → Inductor

(B) Short circuit load: ($Z_L = 0$)

$$\Gamma_L = \frac{0 - Z_0}{0 + Z_0} = -1$$


$$\Rightarrow Z(-\ell) = jZ_0 \tan(\beta\ell) = j\omega L$$

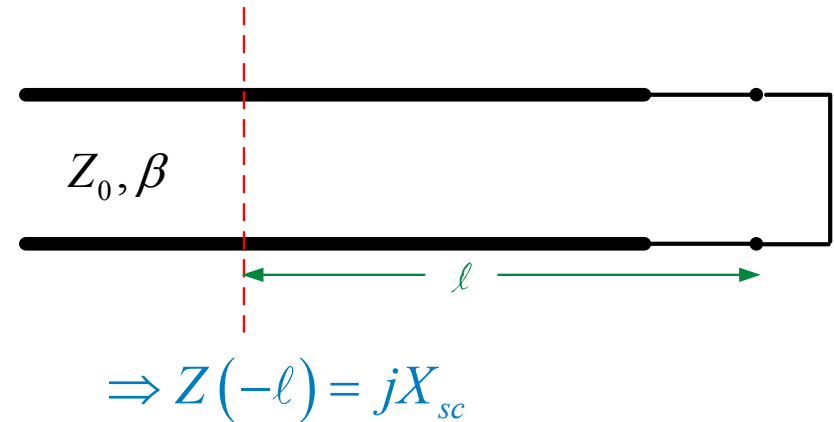Note: $\beta\ell = 2\pi \frac{\ell}{\lambda_g}$ Always imaginary!




$$X_{sc} = Z_0 \tan(\beta\ell)$$
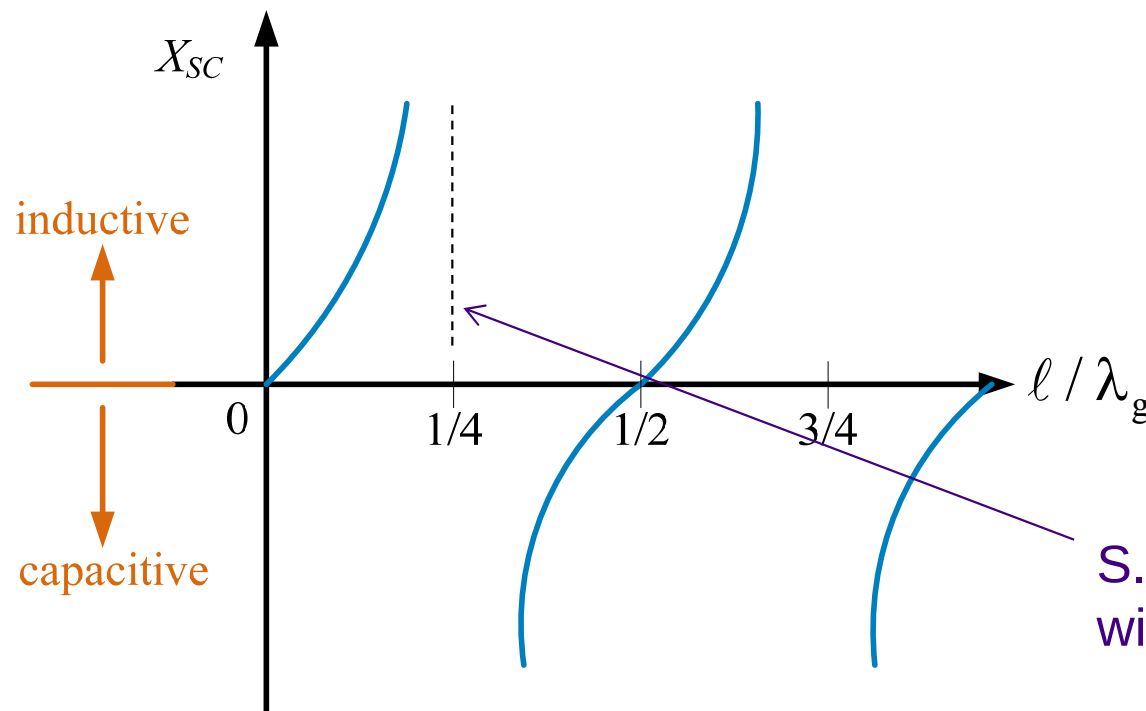
$$\beta\ell < \pi/2 \rightarrow \ell < \lambda_g/4$$




S.C. can become an O.C. with a $\lambda_g/4$ trans. line


Short-circuit Load

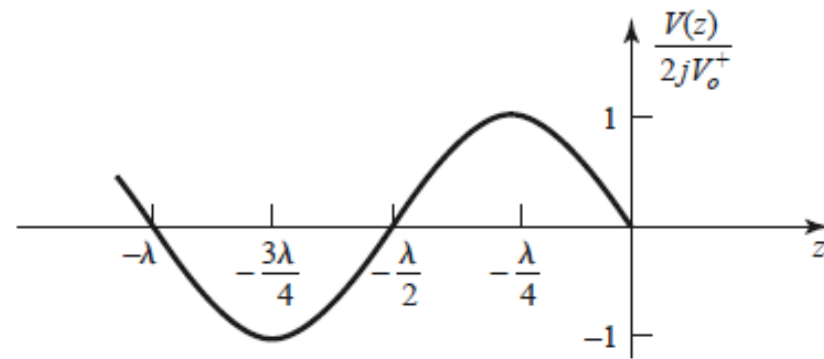


(a)

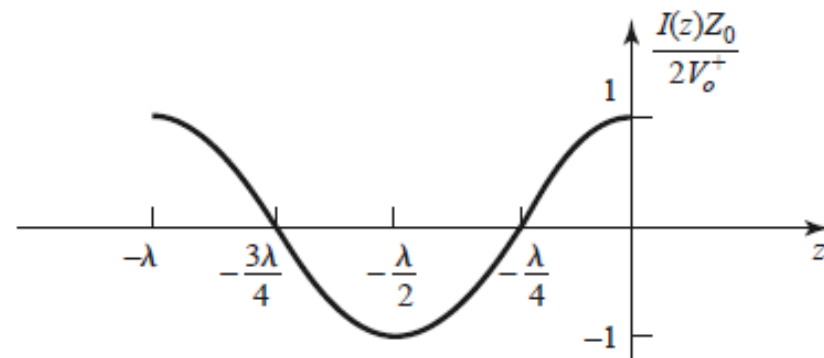

(b)

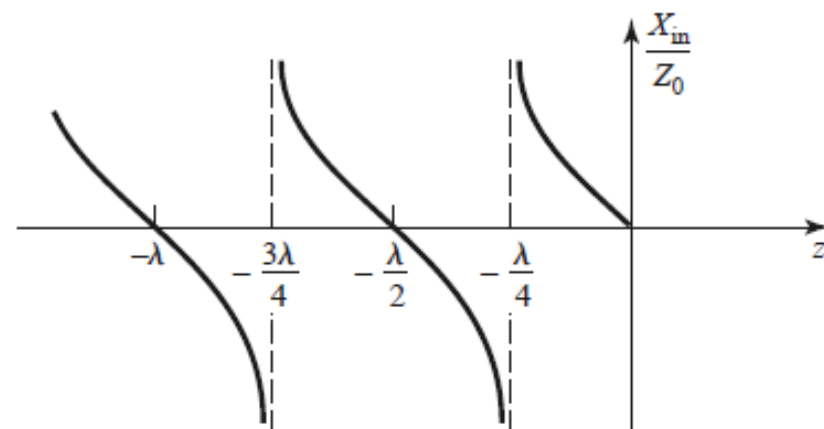

Open-circuit Load → Capacitor

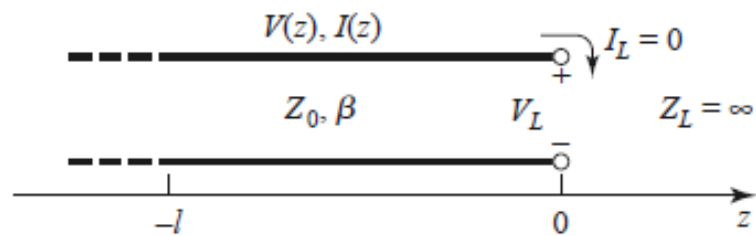


$$Z_L = \infty$$

$$\boxed{\Gamma_L = 1}$$


$$Z_{\text{in,short}} = Z_0 \frac{Z_L + jZ_0 \tan \beta \ell}{Z_0 + jZ_L \tan \beta \ell}$$

$$\boxed{= -jZ_0 \cot \beta \ell \equiv -j \frac{1}{\omega C}}$$

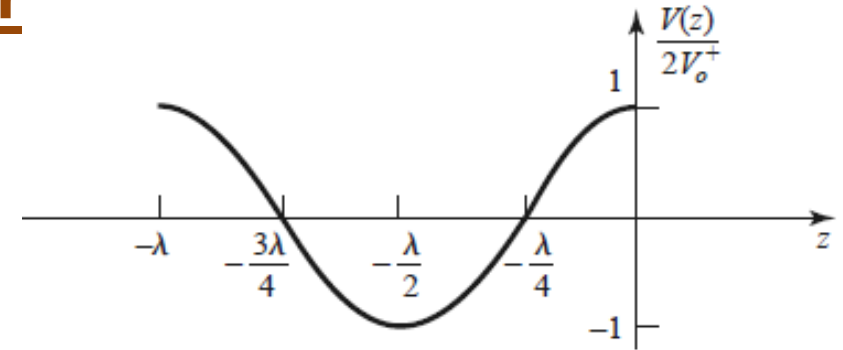
$$\beta \ell < \pi / 2 \rightarrow \boxed{\ell < \lambda_g / 4}$$




(a)

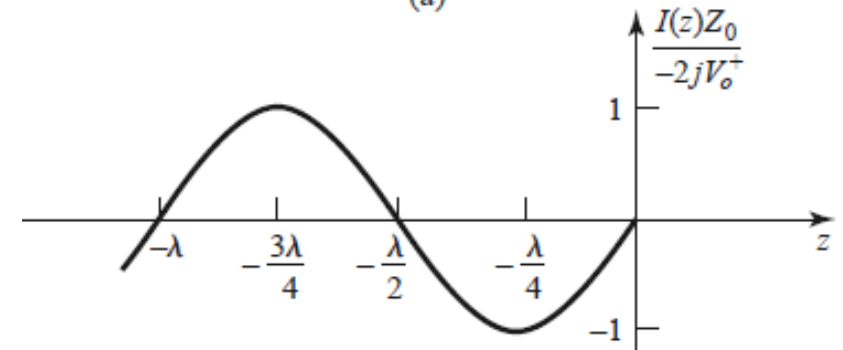

(b)

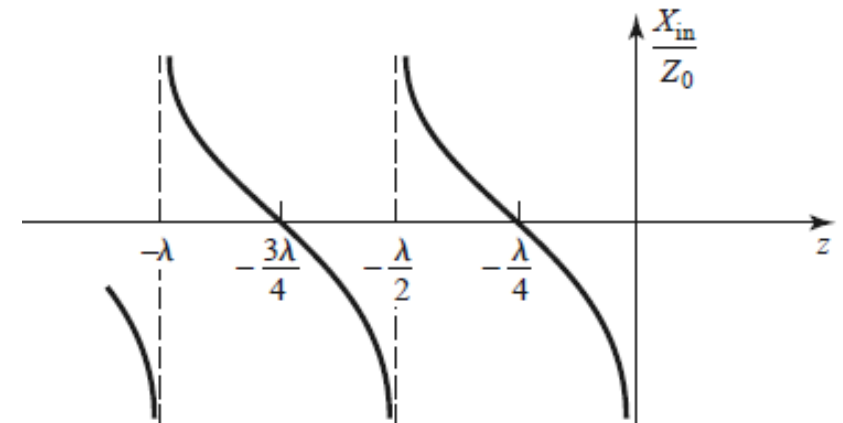

Transmission Line Stub Equivalence

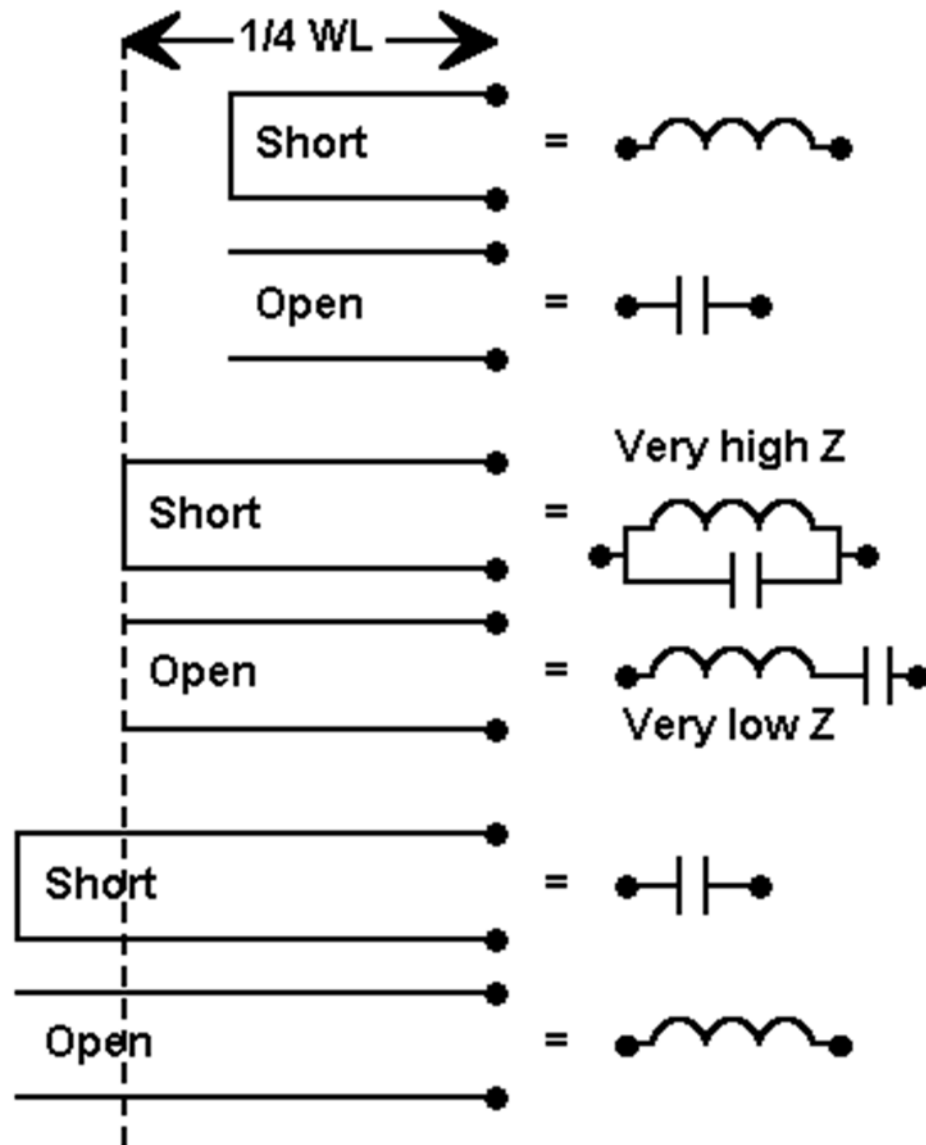

Transmission line stub equivalences

Z_0 from Short and Open Circuit Tests

$$Z_{\text{in,short}} = jZ_0 \tan \beta\ell$$

$$Z_{\text{in,open}} = -jZ_0 \cot \beta\ell$$

$$Z_{\text{in,open}} Z_{\text{in,short}} = Z_0^2 \rightarrow \boxed{Z_0 = \sqrt{Z_{\text{in,open}} Z_{\text{in,short}}}}$$

$$-\frac{Z_{\text{in,short}}}{Z_{\text{in,open}}} = \tan^2 \beta\ell \rightarrow \boxed{\beta = \frac{1}{\ell} \tan^{-1} \sqrt{-\frac{Z_{\text{in,short}}}{Z_{\text{in,open}}}}}$$

Example: Short-open test of a transmission line

$f = 10$ MHz, transmission line length $L = 2$ m

Open-circuit input impedance $Z_S = j 36$; Short-circuit input impedance $Z_O = -j 69$

Find Z_0 and β , λ_g , ϵ_r the line.

(Answer)

$$Z_0 = \sqrt{Z_S Z_O} = \sqrt{36 \times 69} = 49.8 \, \Omega$$

$$\tan \beta L = \sqrt{-\frac{Z_S}{Z_O}} = \sqrt{\frac{36}{69}} = 0.722, \beta L = \tan^{-1} 0.722 = 0.625$$


$$\beta = 0.625 / 2 = 0.313 \text{ rad/m}$$

$$\lambda_g = 2\pi / \beta = 20.1 \text{ m}$$

$$\boxed{\lambda_g = \frac{\lambda_0}{\sqrt{\epsilon_r}}}, \epsilon_r = \left(\frac{\lambda_0}{\lambda_g} \right)^2 = (30 / 20.1)^2 = 2.23$$

Using Transmission Lines to Synthesize Loads

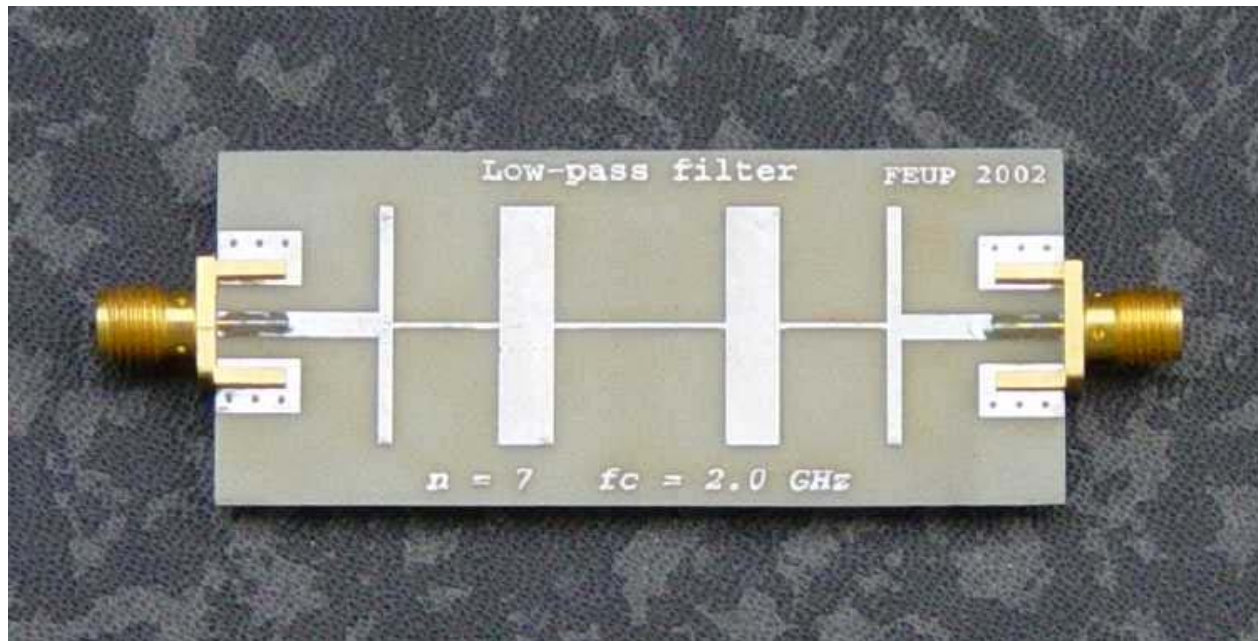This is very useful in microwave engineering.



A microwave filter constructed from microstrip.

Exercise:

$$f = 300 \text{ MHz}$$

Transmission line: length = $0.1 \lambda_g$, $Z_0 = 50 \Omega$

- 1) Find the equivalent capacitance of an open-circuit transmission line.
- 2) Find the equivalent inductance of a short-circuit transmission line.

(Solution)

$$\beta L = \frac{2\pi}{\lambda_g} 0.1 \lambda_g = 0.1\pi$$

$$1) -jZ_0 \cot \beta L = -j \frac{1}{\omega C}$$

$$C = \frac{1}{(2\pi f)Z_0 \cot \beta L} = \frac{1}{2\pi \times 100 \times 10^6 \times 50 \times \cot(0.1\pi)} = 10.3 \text{ pF}$$

$$2) jZ_0 \tan \beta L = j\omega L$$

$$L = \frac{Z_0 \tan \beta L}{\omega} = \frac{50 \tan(0.1\pi)}{2\pi \times 100 \times 10^6} = 25.9 \text{ nH}$$

4. Quarter-wave Transformer


$$Z_{in} = Z_{0T} \left(\frac{Z_L + jZ_{0T} \tan \beta \ell}{Z_{0T} + jZ_L \tan \beta \ell} \right)$$

$$\beta \ell = \beta \frac{\lambda_g}{4} = \frac{2\pi}{\lambda_g} \frac{\lambda_g}{4} = \frac{\pi}{2}$$

$$\Rightarrow Z_{in} = Z_{0T} \left(\frac{jZ_{0T}}{jZ_L} \right)$$

so

$$Z_{in} = \frac{Z_{0T}^2}{Z_L}$$

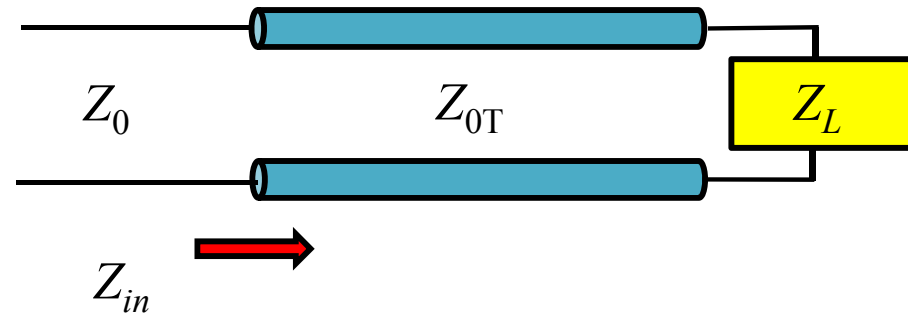

$$\Gamma_{in} = 0 \Rightarrow Z_{in} = Z_0$$

$$\Rightarrow Z_0 = \frac{Z_{0T}^2}{Z_L}$$

This requires Z_L to be real.

Hence

$$Z_{0T} = [Z_0 Z_L]^{1/2}$$

Exercise:

A load with impedance $Z_L = 20 \, \Omega$ is connected to a quarter-wave transformer with propagation constant $\beta = 4\pi \text{ rad/m}$ and characteristic impedance Z_0 for matching with a source impedance of $75 \, \Omega$. Find the length and characteristic impedance of the quarter-wave transformer

(Solution)

$$\beta = 4\pi = \frac{2\pi}{\lambda_g} \rightarrow \lambda_g = 0.5 \text{ m}$$

$$L = \frac{\lambda_g}{4} = 0.125 \text{ m}$$

$$Z_0 = \sqrt{Z_L Z_S} = \sqrt{20 \times 75} = 38.7 \, \Omega$$


5. Voltage Standing Wave Ratio

$$\begin{aligned} V(-\ell) &= V_0^+ e^{j\beta\ell} (1 + \Gamma_L e^{-2j\beta\ell}) \\ &= V_0^+ e^{j\beta\ell} (1 + |\Gamma_L| e^{j\phi_L} e^{-2j\beta\ell}) \end{aligned}$$

$$|V(-\ell)| = |V_0^+| |1 + |\Gamma_L| e^{j\phi_L} e^{-j2\beta\ell}|$$

$$V_{\max} = |V_0^+| (1 + |\Gamma_L|), \quad \phi_L - 2\beta\ell = 2n\pi$$

$$V_{\min} = |V_0^+| (1 - |\Gamma_L|), \quad \phi_L - 2\beta\ell = 2n\pi + \pi$$

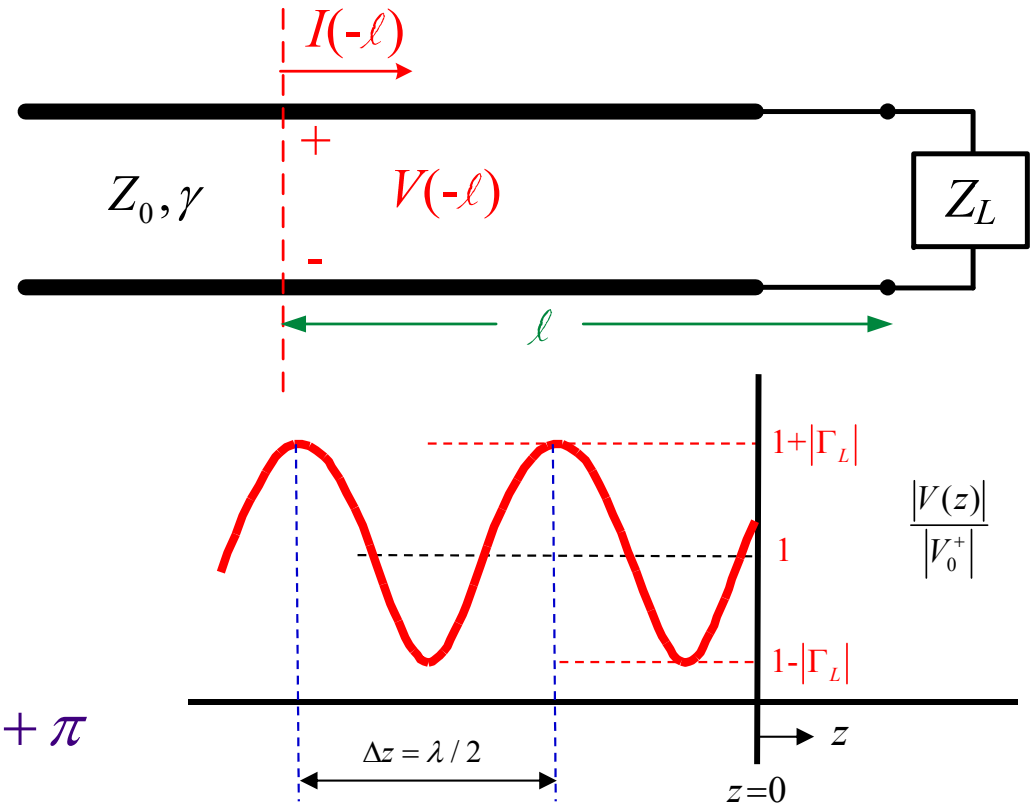

$$\text{Voltage Standing Wave Ratio (VSWR)} = \frac{V_{\max}}{V_{\min}}$$

$$\text{VSWR} = \frac{1 + |\Gamma_L|}{1 - |\Gamma_L|}$$

Exercise:


A load with impedance $Z_L = 20 - j20 \Omega$ is connected to a transmission line with characteristic impedance $Z_0 = 50 \Omega$. Find the VSWR on the transmission line.

(Solution)

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{20 - j20 - 50}{20 - j20 + 50} = \frac{-30 - j20}{70 - j20} = 0.495e^{-j130.4^\circ}$$

$$\text{VSWR} = \frac{1 + |\Gamma_L|}{1 - |\Gamma_L|} = \frac{1 + 0.495}{1 - 0.495} = 2.96$$

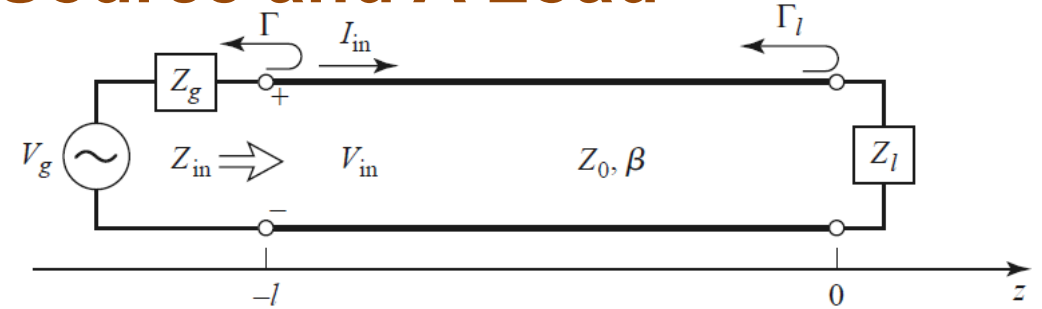6. Transmission Line with A Source and A Load



$$Z_{in} = Z_0 \frac{1 + \Gamma_\ell e^{-2j\beta\ell}}{1 - \Gamma_\ell e^{-2j\beta\ell}} = Z_0 \frac{Z_\ell + j Z_0 \tan \beta\ell}{Z_0 + j Z_\ell \tan \beta\ell}, \quad (2.67)$$

where Γ_ℓ is the reflection coefficient of the load:

$$\Gamma_\ell = \frac{Z_\ell - Z_0}{Z_\ell + Z_0}. \quad (2.68)$$

The voltage on the line can be written as

$$V(z) = V_o^+ (e^{-j\beta z} + \Gamma_\ell e^{j\beta z}), \quad (2.69)$$

and we can find V_o^+ from the voltage at the generator end of the line, where $z = -\ell$:

$$V(-\ell) = V_g \frac{Z_{in}}{Z_{in} + Z_g} = V_o^+ (e^{j\beta\ell} + \Gamma_\ell e^{-j\beta\ell}),$$

so that

$$V_o^+ = V_g \frac{Z_{in}}{Z_{in} + Z_g} \frac{1}{(e^{j\beta\ell} + \Gamma_\ell e^{-j\beta\ell})}. \quad (2.70)$$

This can be rewritten, using (2.67), as

$$V_o^+ = V_g \frac{Z_0}{Z_0 + Z_g} \frac{e^{-j\beta\ell}}{(1 - \Gamma_\ell \Gamma_g e^{-2j\beta\ell})}, \quad (2.71)$$

Exercise:

A load with impedance $Z_L = 20 - j20 \Omega$ is connected to a transmission line whose length is 0.2 wavelength and whose characteristic impedance Z_0 is 50Ω . The other end of the transmission line is connected to a voltage source $V_s = 10e^{j45^\circ}$ with internal impedance Z_s of $40 + j60 \Omega$.

- 1) Find the voltage at the input of the transmission line.
- 2) Find the voltage at the load.
- 3) Find the power dissipated at the load.

(Solution)

$$1) \Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{20 - j20 - 50}{20 - j20 + 50} = \frac{36.1e^{j213.7^\circ}}{72.8e^{-j15.9^\circ}} = 0.496e^{j229.6^\circ}$$

$$\Gamma_{in} = \Gamma_L e^{-j2(2\pi/\lambda_g)0.2\lambda_g} = 0.496e^{j229.6^\circ} e^{-j0.8\pi} = 0.496e^{j85.6^\circ} = 0.0381 + j0.495$$

$$Z_{in} = Z_0 \frac{1 + \Gamma_{in}}{1 - \Gamma_{in}} = 50 \frac{1 + 0.0381 + j0.495}{1 - 0.0381 - j0.495} = 50 \frac{1.0381 + j0.495}{0.962 - j0.495} = 32.2 + j42.3 \Omega$$

$$V_{in} = V_s \frac{Z_{in}}{Z_s + Z_{in}} = 10e^{j45^\circ} \frac{32.2 + j42.3}{40 + j60 + 32.2 + j42.3} = 4.25e^{j42.9^\circ}$$

$$2) V_{\text{in}} = V_{0,\text{in}}^+ (1 + \Gamma_{\text{in}})$$

$$V_{0,\text{in}}^+ = \frac{V_{\text{in}}}{1 + \Gamma_{\text{in}}} = \frac{4.25e^{j42.9^\circ}}{1 + 0.496e^{j85.6^\circ}} = 3.70e^{j17.4^\circ}$$

$$V_L = V_{0,\text{in}}^+ e^{-j(2\pi/\lambda_g)0.2\lambda_g} (1 + \Gamma_L) = 3.70e^{j17.4^\circ} e^{-j0.4\pi} (1 + 0.496e^{j229.6^\circ}) = 2.87e^{-j83.7^\circ}$$

$$3) P_L = \frac{1}{2} \text{Re} \frac{|V_L|}{Z_L^*} = \frac{1}{2} \text{Re} \frac{2.87^2}{(20 - j20)^*} = \frac{1}{2} \times 0.103 = 0.0515 \text{ W}$$

7. Reflected Power and Delivered Power

$$V(z) = V_o^+ (e^{-j\beta z} + \Gamma e^{j\beta z}),$$

$$I(z) = \frac{V_o^+}{Z_0} (e^{-j\beta z} - \Gamma e^{j\beta z}).$$

$$P_{\text{avg}} = \frac{1}{2} \text{Re}\{V(z)I(z)^*\} = \frac{1}{2} \frac{|V_o^+|^2}{Z_0} \text{Re}\{1 - \Gamma^* e^{-2j\beta z} + \Gamma e^{2j\beta z} - |\Gamma|^2\},$$

$$P_{\text{avg}} = \frac{1}{2} \frac{|V_o^+|^2}{Z_0} (1 - |\Gamma|^2),$$

$$P_i = \frac{1}{2} \frac{|V_o^+|^2}{Z_0} : \text{incident power}$$

$$P_r = \frac{1}{2} \frac{|V_o^+|^2}{Z_0} |\Gamma|^2 : \text{reflected power}$$

$$P_{\text{avg}} = P_i - P_r : \text{power delivered to the load}$$

Exercise:

A load with impedance $Z_L = 20 - j20 \Omega$ is connected to a transmission line with characteristic impedance $Z_0 = 50 \Omega$. A voltage of $20e^{j45^\circ}$ is incident on the load.

- 1) Find the power P_i incident on the load.
- 2) Find the power P_r reflected from the load.
- 3) Find the power P_L delivered to the load.

(Solution)

$$1) P_i = \frac{1}{2} \frac{|V_0^+|^2}{Z_0} = \frac{1}{2} \frac{20^2}{50} = 4 \text{ W}$$

$$2) \Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{20 - j20 - 50}{20 - j20 + 50} = \frac{-30 - j20}{70 - j20}, |\Gamma_L|^2 = \frac{30^2 + 20^2}{70^2 + 20^2} = \frac{13}{53}$$

$$P_r = |\Gamma_L|^2 P_i = \frac{13}{53} \times 4 = \frac{52}{53} = 0.98 \text{ W}$$

$$3) P_L = P_i - P_r = 4 - 0.98 = 3.02 \text{ W}$$

8. Code Example

Given,

$Z_L = R_L + jX_L$: load impedance (Ω)

Z_0 : characteristic impedance (Ω)

L : line length in wavelength

Find

$\Gamma_{\text{in}} = |\Gamma_{\text{in}}| e^{j\varphi}$: input reflection coefficient in polar form

$|\Gamma_{\text{in}}|$ (dB) : reflection coefficient in dB

$Z_{\text{in}} = R_{\text{in}} + jX_{\text{in}}$: input impedance

(Equations)

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0}, \quad \Gamma_{\text{in}} = \Gamma_L e^{-j2\beta L} = \Gamma_L e^{-j2(2\pi/\lambda)L} = \Gamma_L e^{-j2 \times 2\pi(L/\lambda)}$$

$$|\Gamma_{\text{in}}| \text{ (dB)} = 20 \log_{10} |\Gamma_{\text{in}}|, \quad Z_{\text{in}} = Z_0 \frac{1 + \Gamma_{\text{in}}}{1 - \Gamma_{\text{in}}}$$

```

# Microwave Engineering, Lecture 2 Python Code
# Terminated transmission line: input reflection coefficient and input impedance
# Sample values:
# Input: RL=40, XL=40, L=0.1 wavelenth
# Output:
#
import cmath
import math
pi=3.14159265
while True:
    RL=float(input('RL (ohm)='))
    XL=float(input('XL (ohm)='))
    Z0=float(input('Z0 (ohm)='))
    L=float(input('L (wavelength)='))
    j=complex(0.,1.)
    ZL=complex(RL, XL)
    GL=(ZL-Z0)/(ZL+Z0)
    Gin=GL*cmath.exp(-j*2*2*pi*L)
    Gin_mag, Gin_phase=cmath.polar(Gin)
    Gin_dB=20*math.log(Gin_mag)
    Zin=Z0*(1+Gin)/(1-Gin)
    print('Input reflection coeffcient: mag, phase(deg)=' ,Gin_mag, Gin_phase)
    print('Input reflection coefficint (dB)=' ,Gin_dB)
    print('Zin=' ,Zin)

```

```

'''
RL (ohm) =
20
XL (ohm) =
50
Z0 (ohm) =
50
L (wavelength) =
0.2
Input reflection coeffcient: mag, phase(deg)= 0.677834389404565 -1.022307778917341
Input reflection coefficint (dB)= -7.7770456858800845
Zin= (35.91076216402567-76.8526053239948j)
RL (ohm) =
'''

```

Fin
(End)