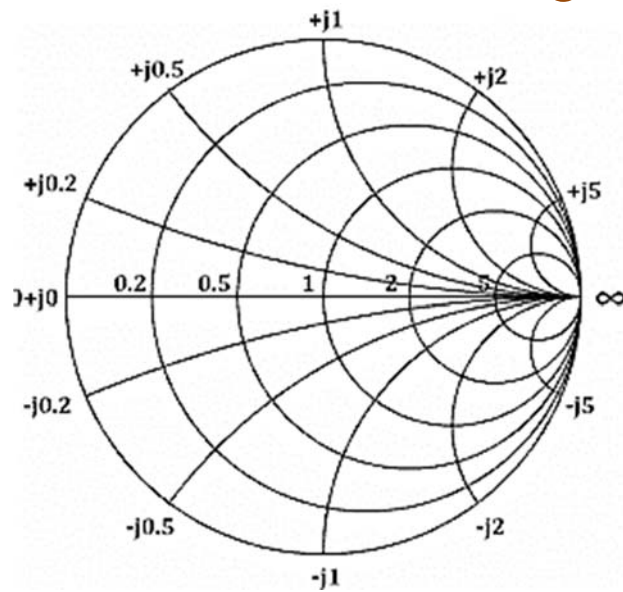


Lecture 4 Smith Chart

1. What is the Smith Chart?
2. Derivation of the Smith Chart Equations
3. The Real Smith Chart
4. Getting Familiar with the Smith Chart
5. Admittance Smith Chart – Y Chart
6. ZY Chart
7. Smith Chart Examples

1. What is the Smith Chart?

■ Z_{in} vs Γ calculation diagram



Smith chart



ARINST VR 23-6200 (\$510)

■ Invention

- Philip Smith, 1939, Electronics magazine
- Mizuhashi Tosaku, 1936, Journal of Electrical Communications Engineers of Japan

Applications

- Impedance matching: $5 - j 210 \Omega \rightarrow 50 + j 0 \Omega$
- Impedance calculation

■ Z_{in} vs Γ

$$V(-\ell) = V_0^+ e^{-j\beta\ell} [1 + \Gamma(-\ell)]$$


$$I(-\ell) = \frac{V_0^+}{Z_0} e^{-j\beta\ell} [1 + \Gamma(-\ell)]$$

$$\boxed{Z_{in} = Z = Z_0 \frac{1 + \Gamma(z)}{1 - \Gamma(z)}} \text{ (input impedance)}$$

$$\boxed{\Gamma = \frac{Z - Z_0}{Z + Z_0}} \text{ (reflection coefficient)}$$

$$\Gamma(-\ell) = \Gamma_L e^{-j2\beta\ell}$$
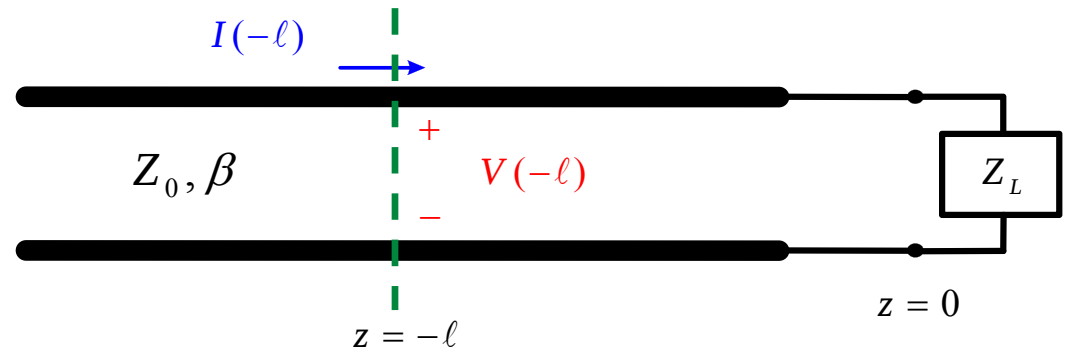
$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0}$$





2. Derivation of the Smith Chart Equations


$$z = \frac{Z}{Z_0} = r + jx = \frac{1 + \Gamma}{1 - \Gamma} = \frac{1 + u + jv}{1 - (u + jv)} \quad (\text{normalized impedance})$$


$$\Gamma = u + jv = \rho e^{j\phi} \quad (\text{reflection coefficient})$$

$$r = \frac{1 - u^2 - v^2}{(1 - u)^2 + v^2} \rightarrow \left(u - \frac{r}{1 + r}\right)^2 + v^2 = \left(\frac{1}{1 + r}\right)^2 \quad (\text{circles of constant } r)$$

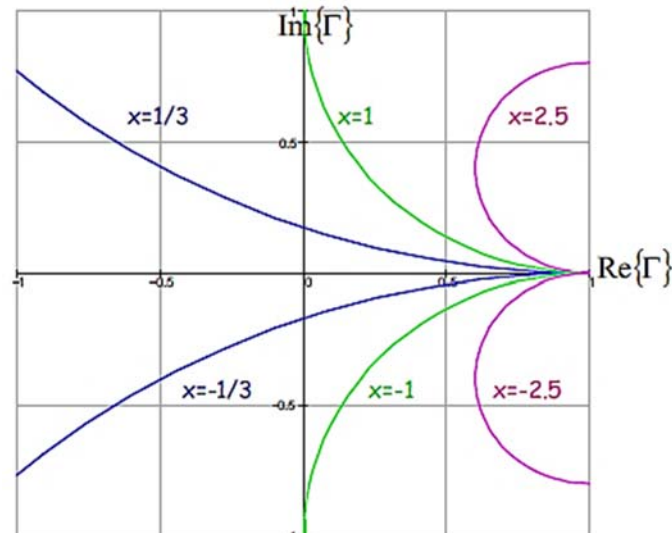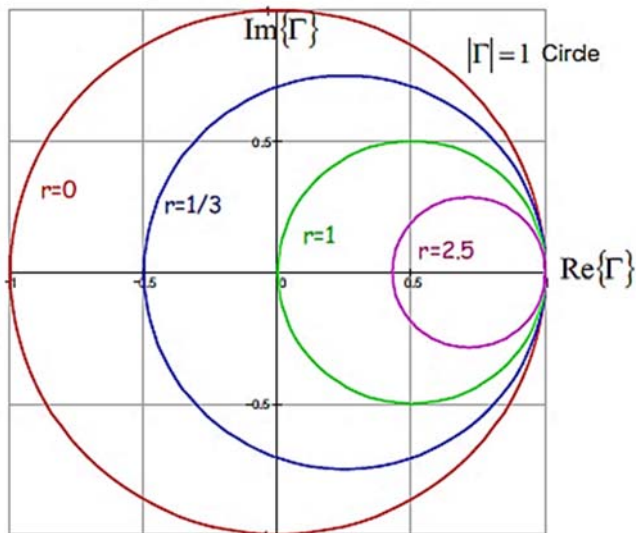
$$x = \frac{2v}{(1 - u)^2 + v^2} \rightarrow (u - 1)^2 + \left(v - \frac{1}{x}\right)^2 = \left(\frac{1}{x}\right)^2 \quad (\text{circles of constant } x)$$




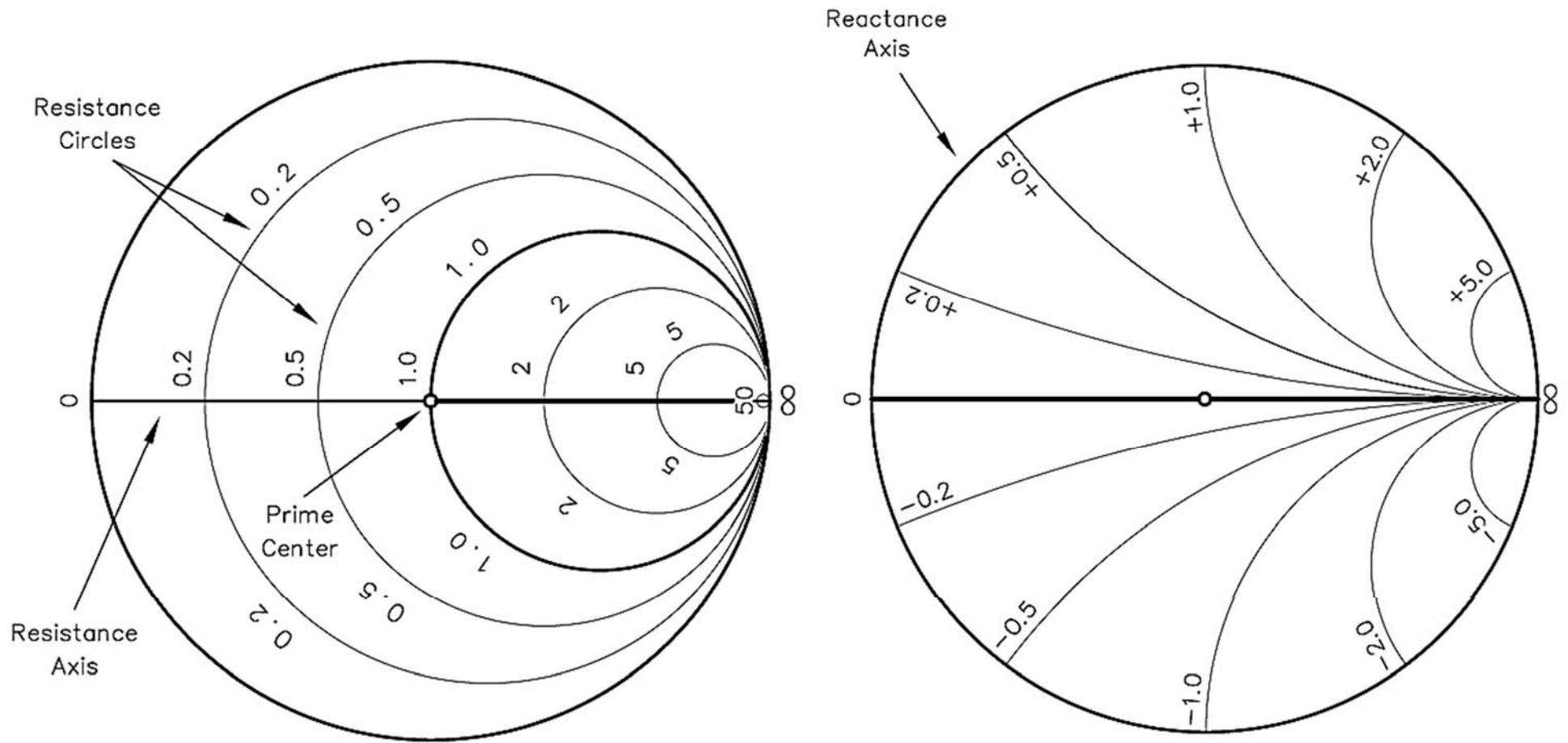


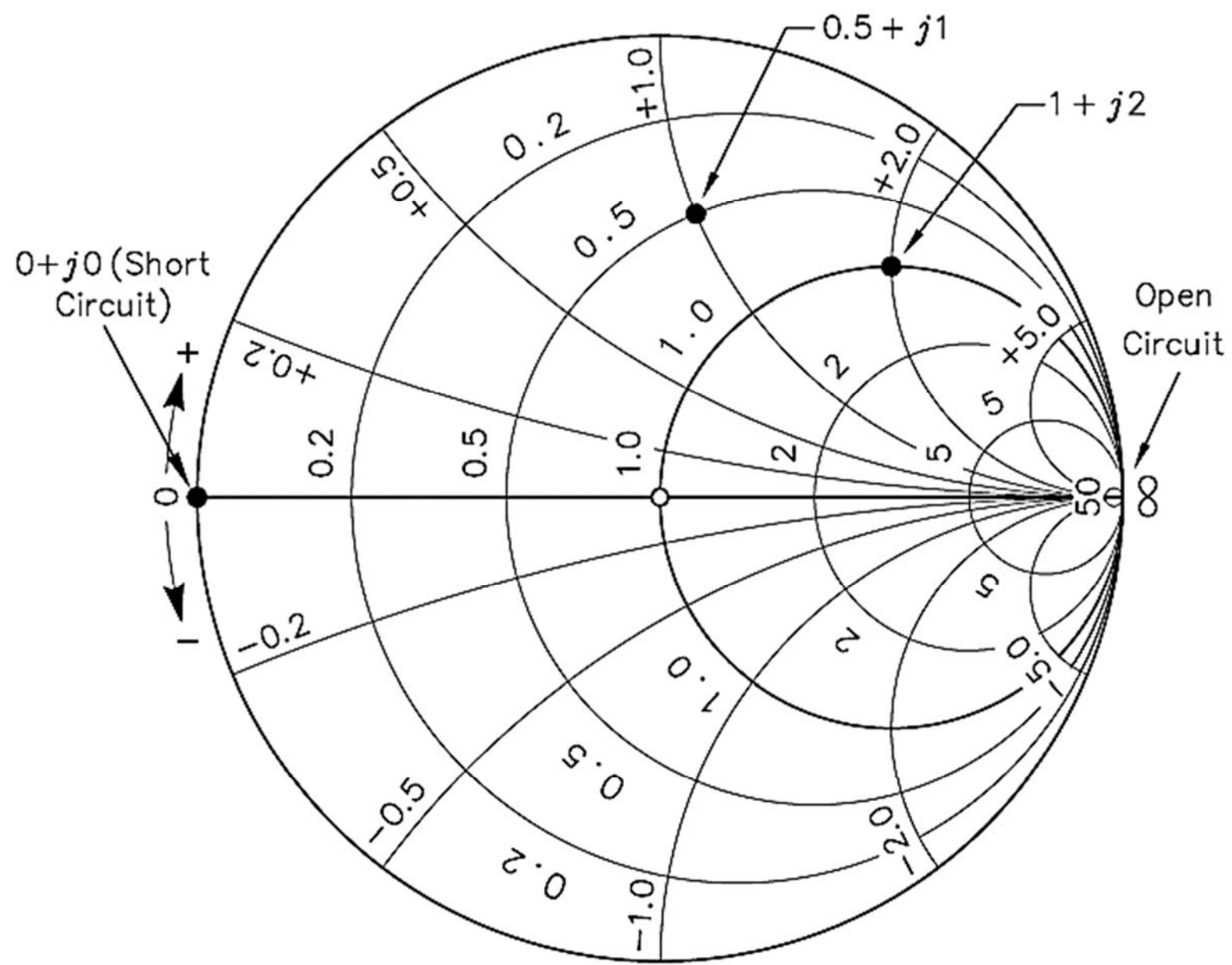

3. The Real Smith Chart

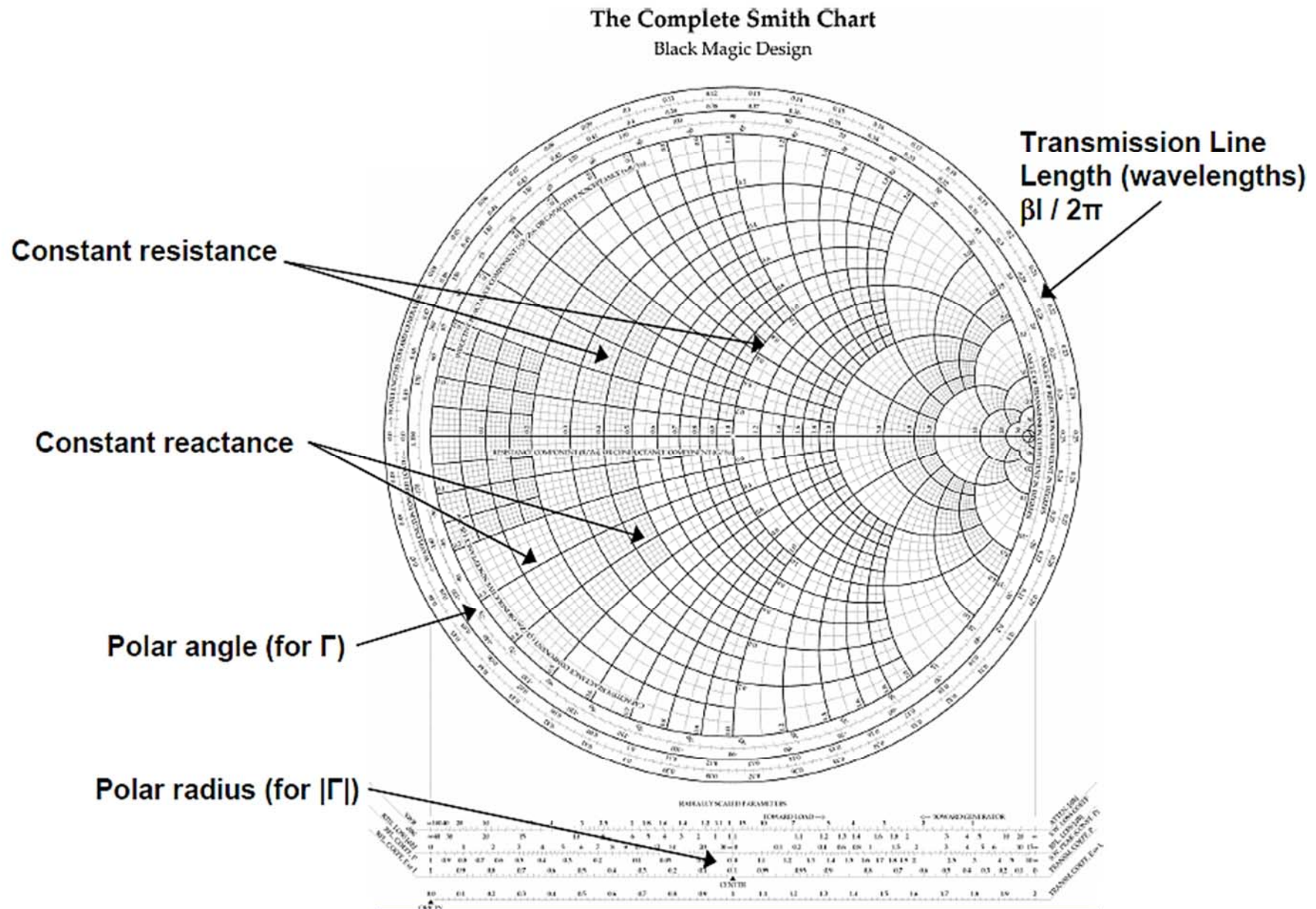

4. Getting Familiar with the Smith Chart

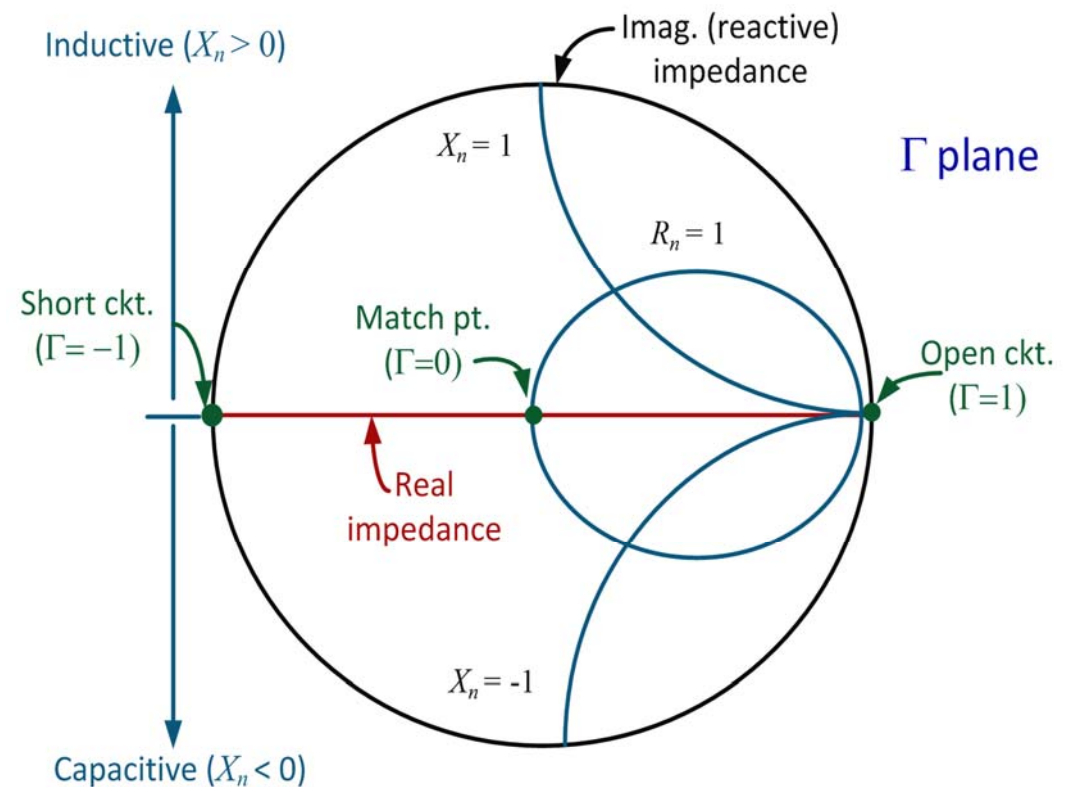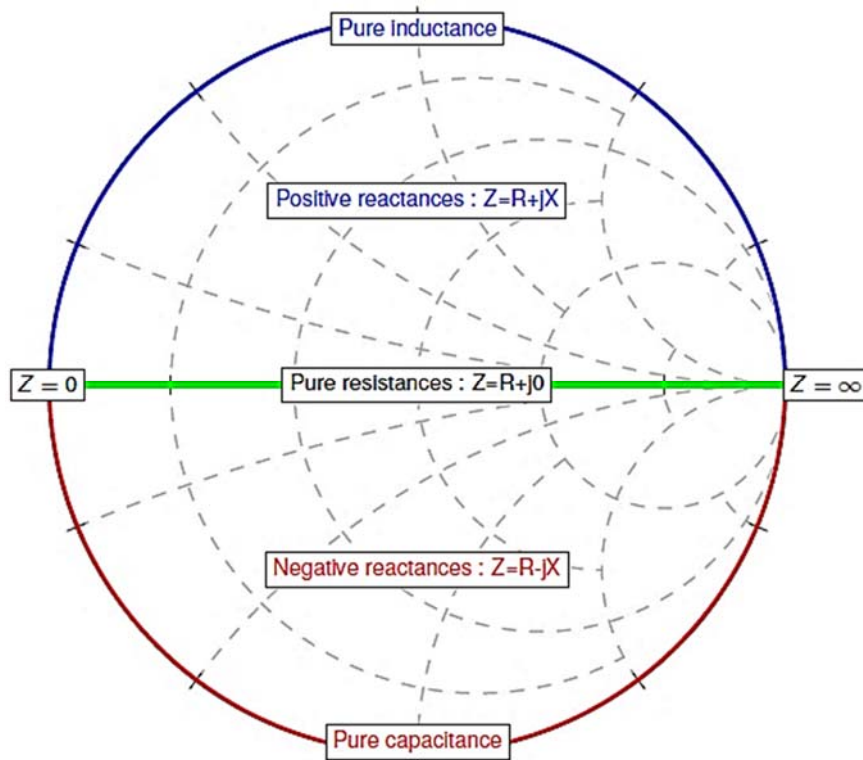



- Impedance divided by line impedance (50 Ohms)

- $Z1 = 100 + j50$
- $Z2 = 75 - j100$
- $Z3 = j200$
- $Z4 = 150$
- $Z5 = \text{infinity}$ (an open circuit)
- $Z6 = 0$ (a short circuit)
- $Z7 = 50$
- $Z8 = 184 - j900$


- Then, normalize and plot. The points are plotted as follows:


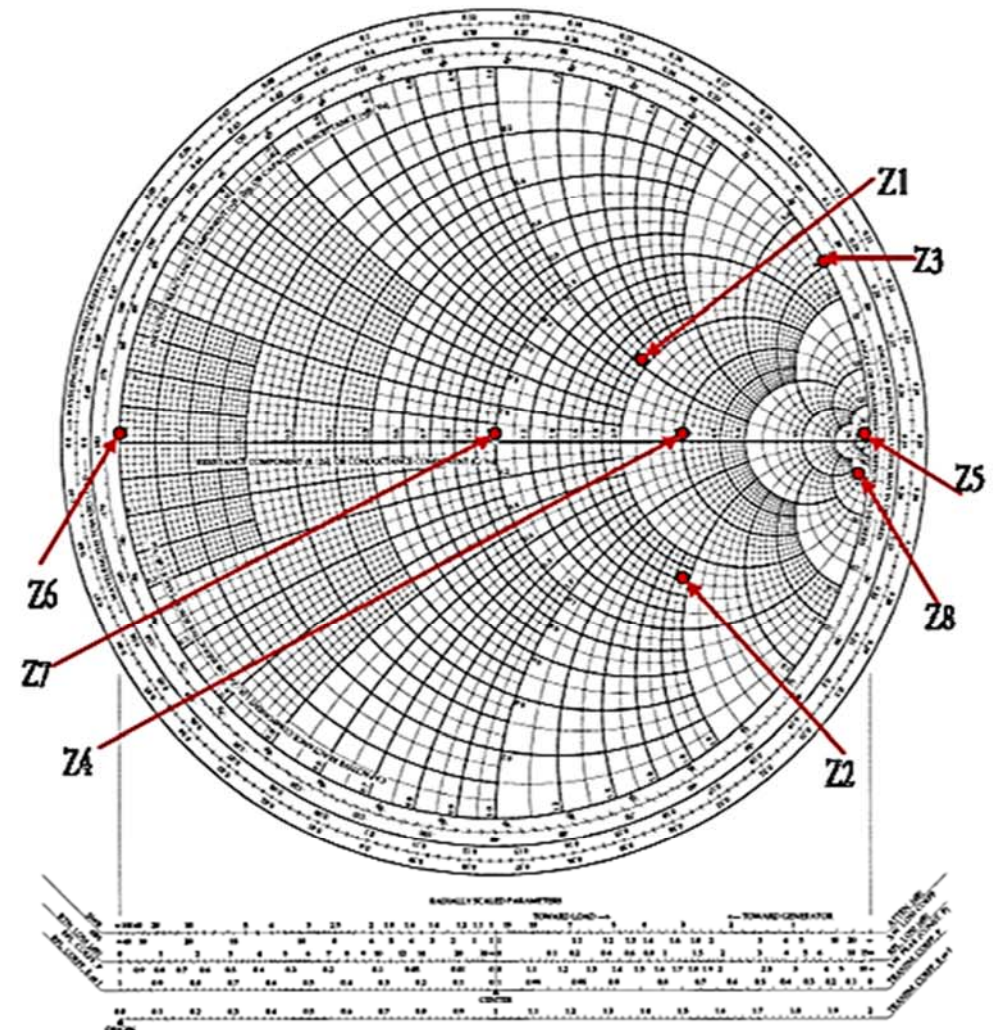
- $z1 = 2 + j$
- $z2 = 1.5 - j2$
- $z3 = j4$
- $z4 = 3$
- $z5 = \text{infinity}$
- $z6 = 0$
- $z7 = 1$
- $z8 = 3.68 - j18S$





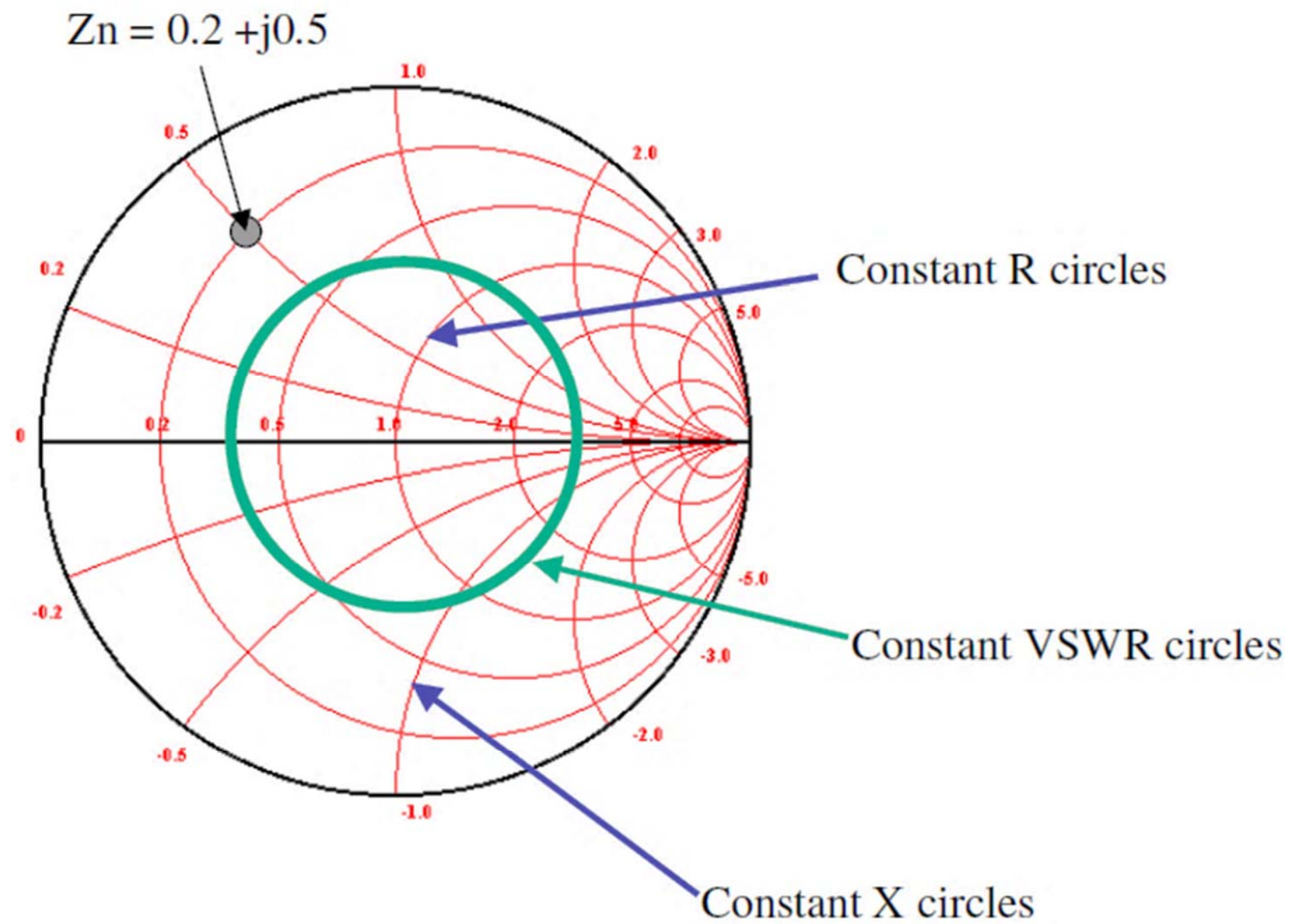

$$z_1 = 3 - j3$$

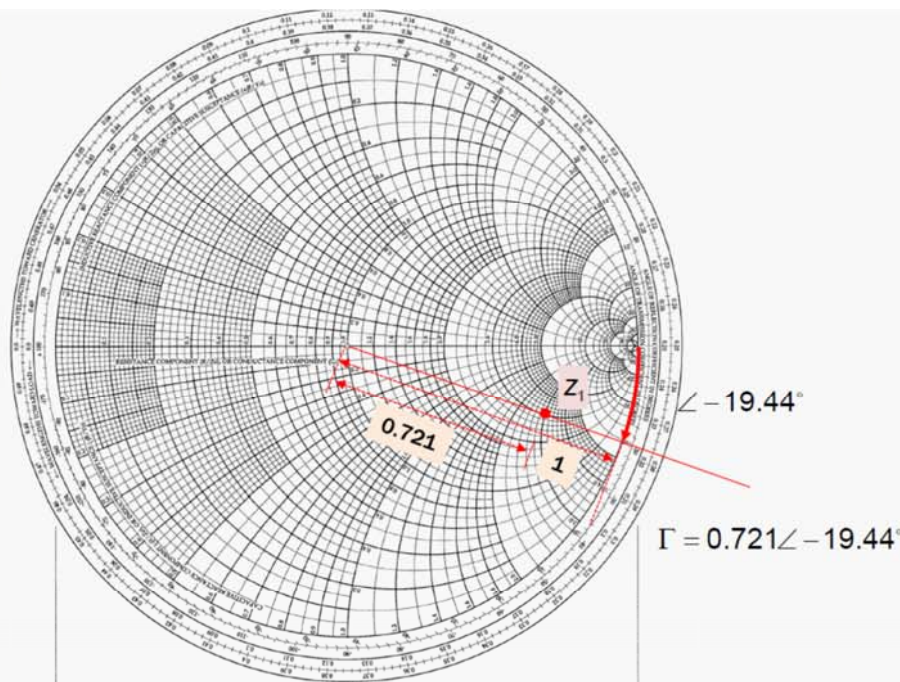

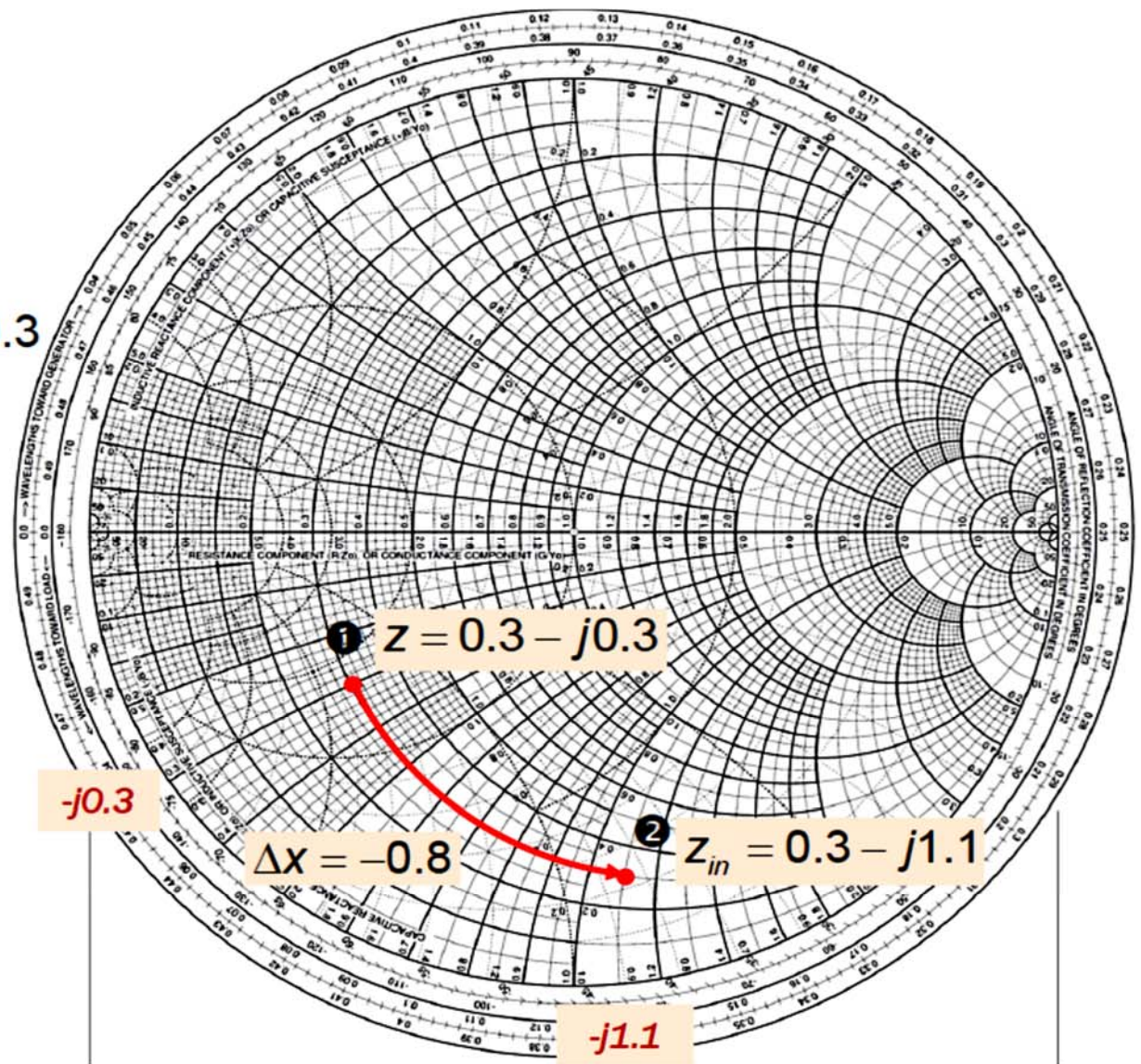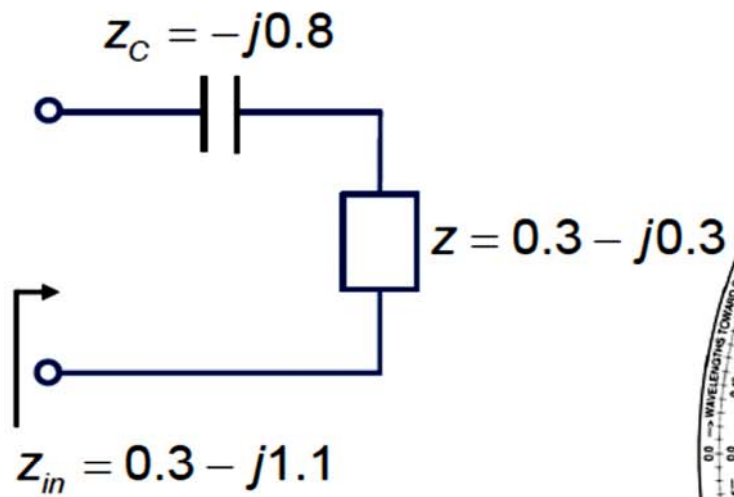

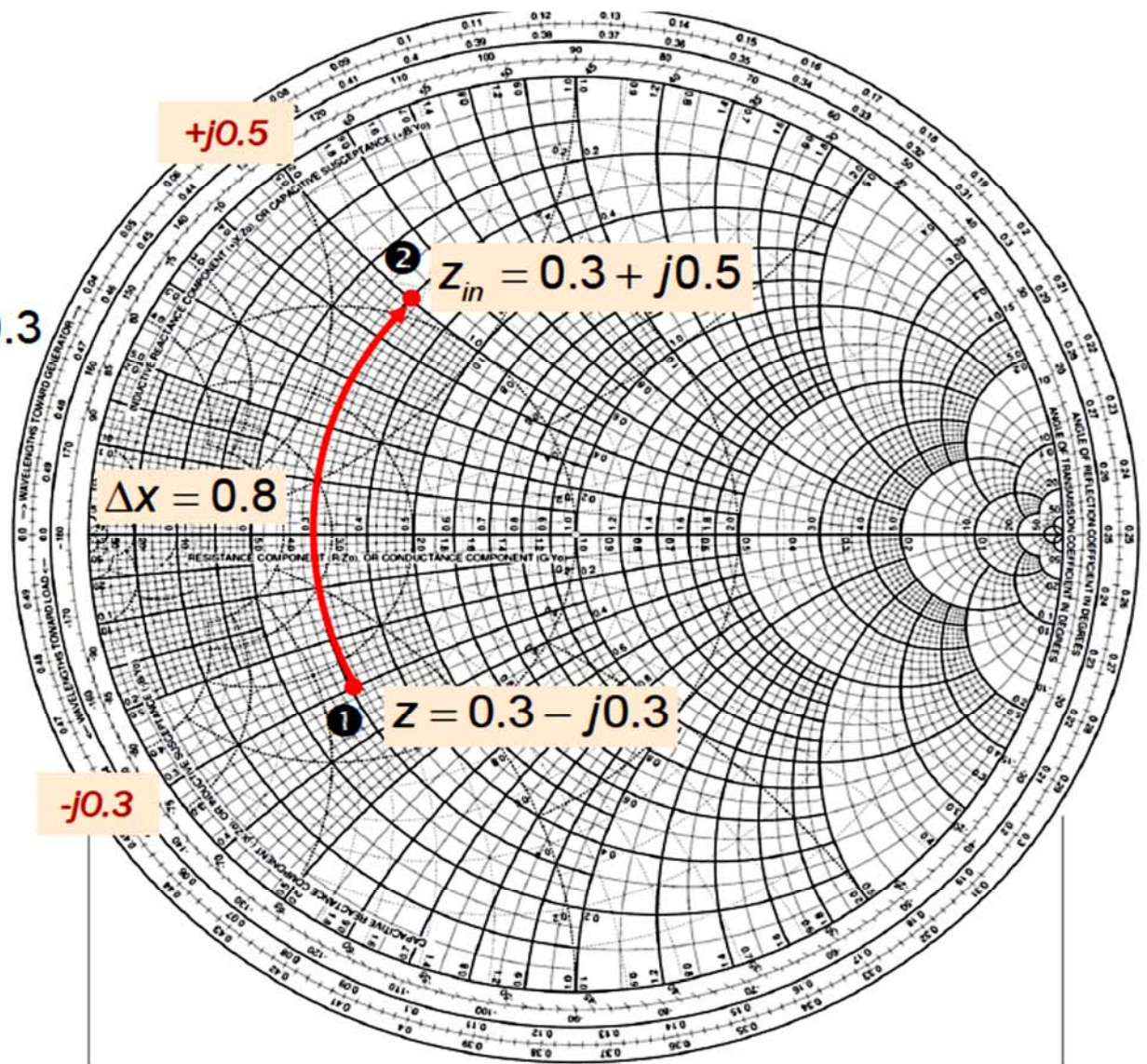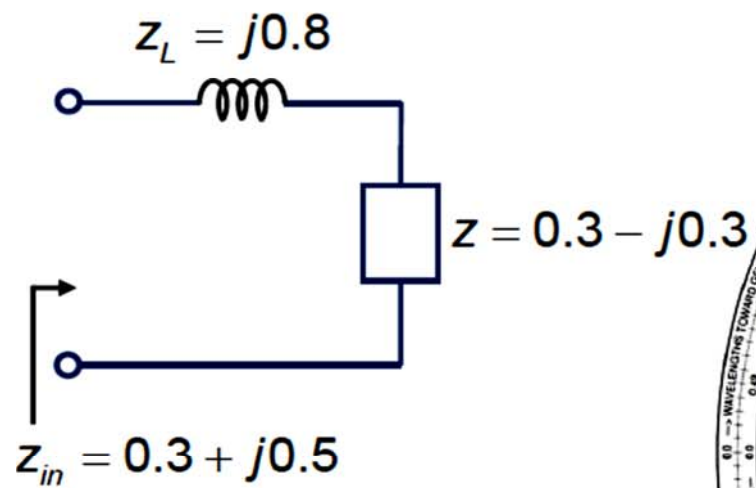


$$z_1 = 1 + j1$$

$$z_2 = 0.4 + j0.5$$

$$z_3 = 3 - j3$$

$$z_4 = 0.2 - j0.6$$

$$z_5 = \underline{0}$$

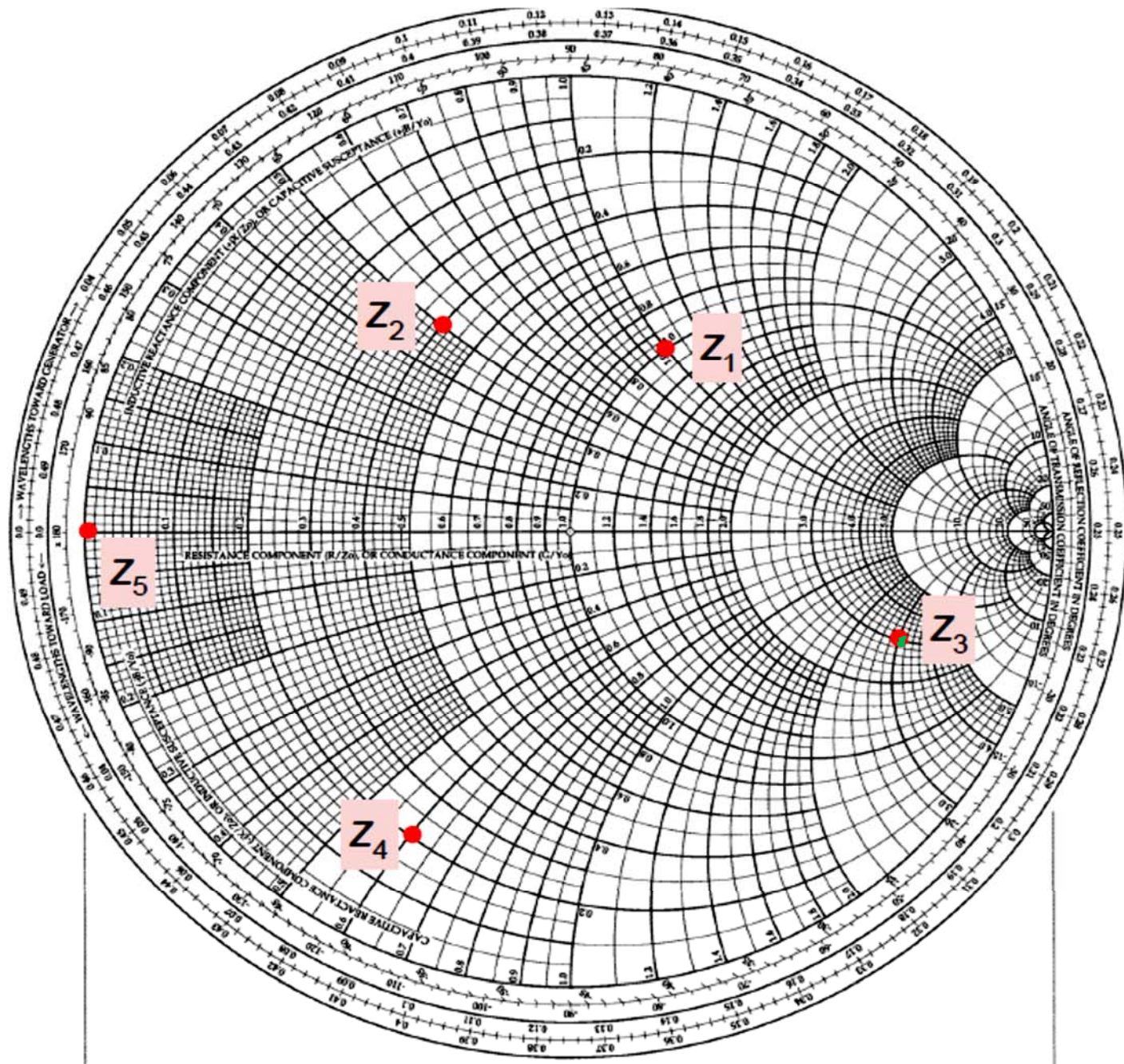

5. Admittance Smith Chart – Y Chart


- Use Z chart for admittance

$$Y = \frac{1}{Z} = \frac{1}{Z_0} \frac{1-\Gamma}{1+\Gamma} = Y_0 \frac{1+(-\Gamma)}{1-(-\Gamma)} \leftrightarrow Z = Z_0 \frac{1+\Gamma}{1-\Gamma}$$

$\Gamma \rightarrow -\Gamma$ (rotate 180°)

$Z_0 \rightarrow Y_0 = 1/Z_0$

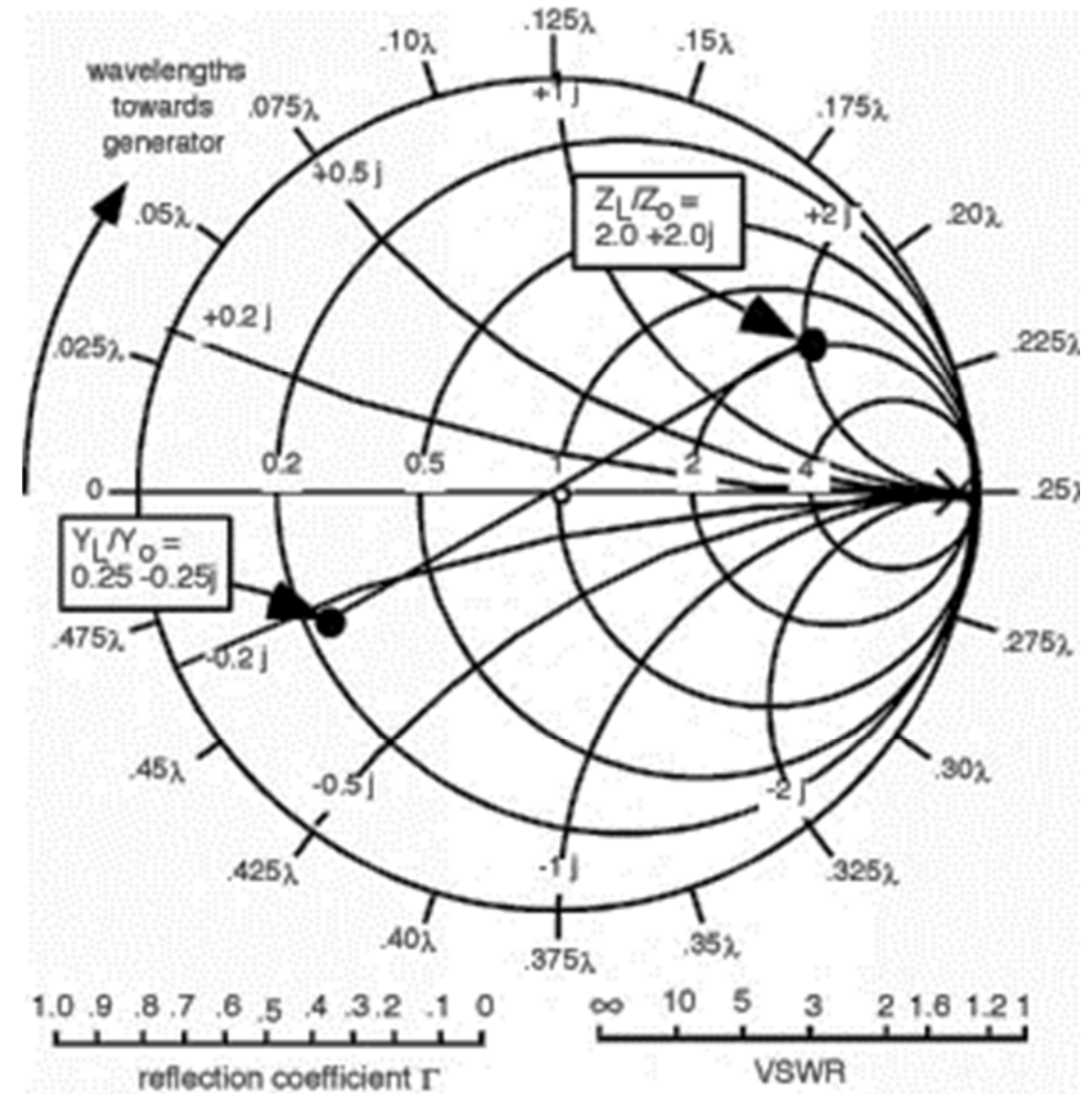- Rotate z by 180° and read a z value on the Smith chart. It is then y value.



$$y_1 = 1 + j1$$


$$y_2 = 0.4 + j0.5$$

$$y_3 = 2 - j1.4$$


$$y_4 = 0.5 - j0.2$$

$$y_5 = \infty$$



$$y = g + jb$$


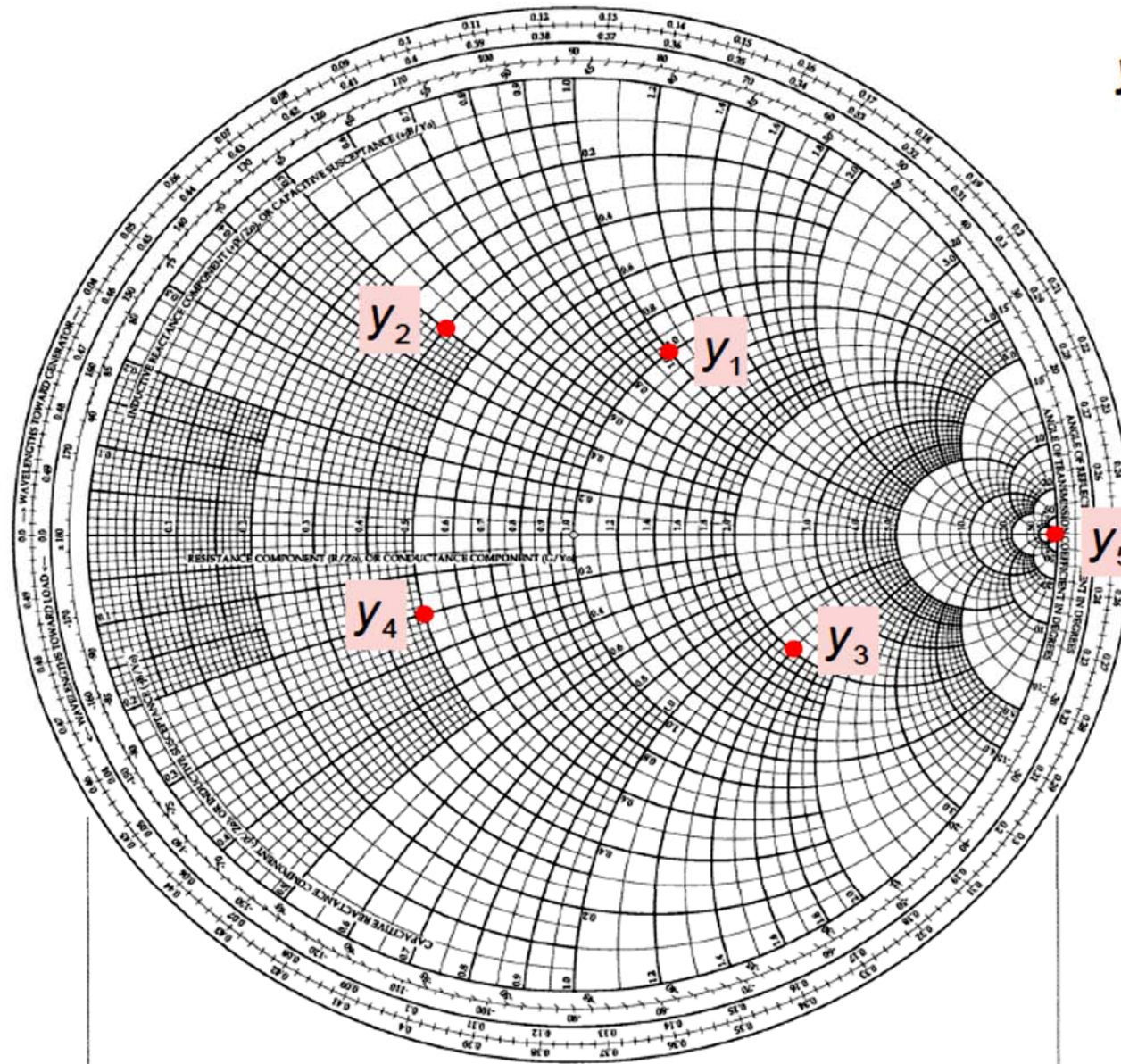



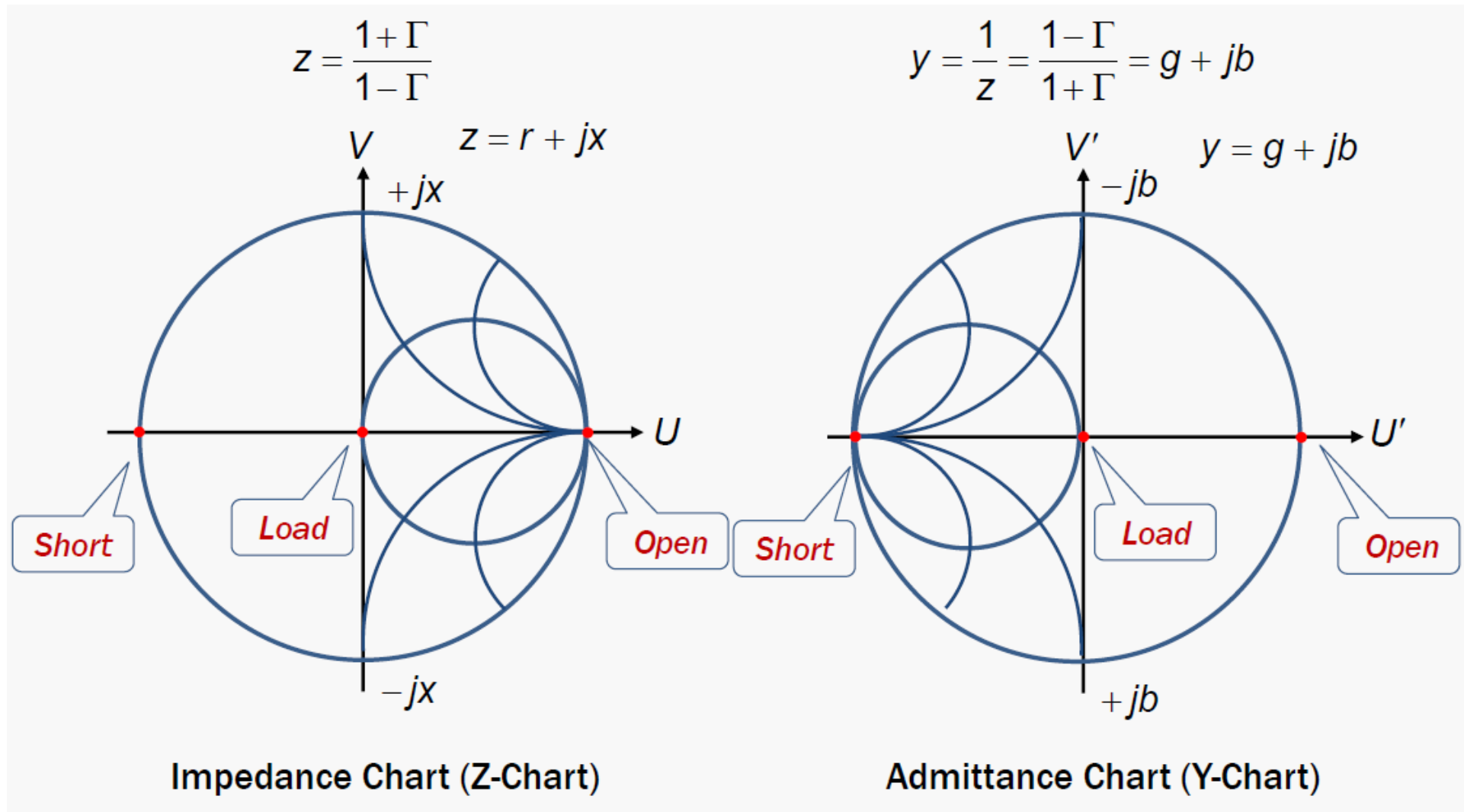
- Using the Y Smith chart
- Rotate the z Smith chart by 180°





Smith Chart
(Y-Chart)

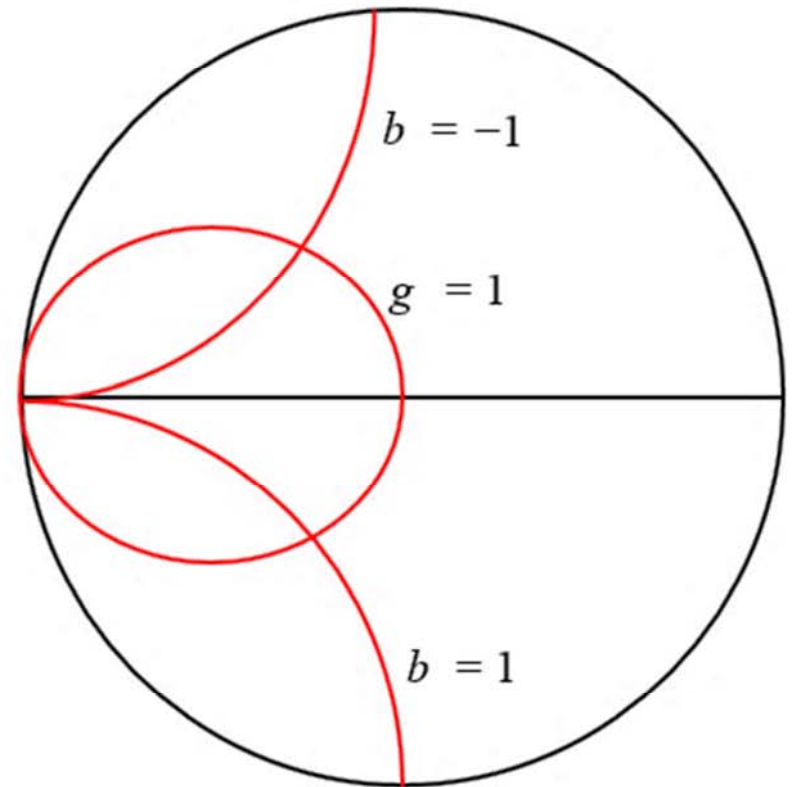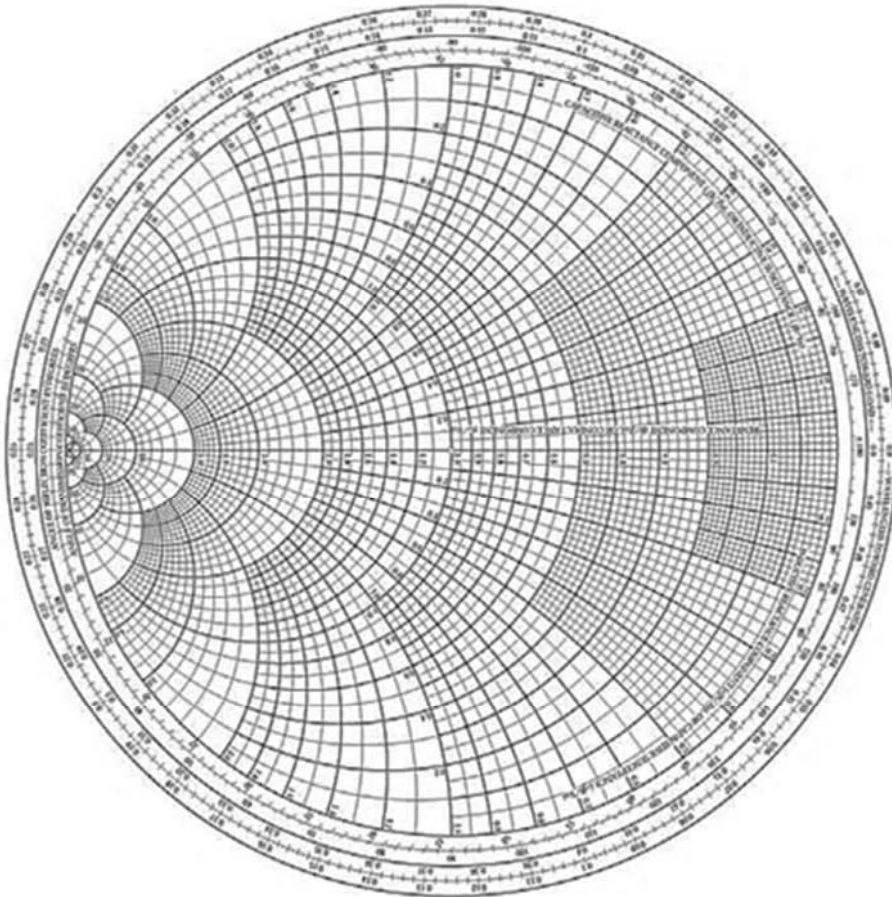


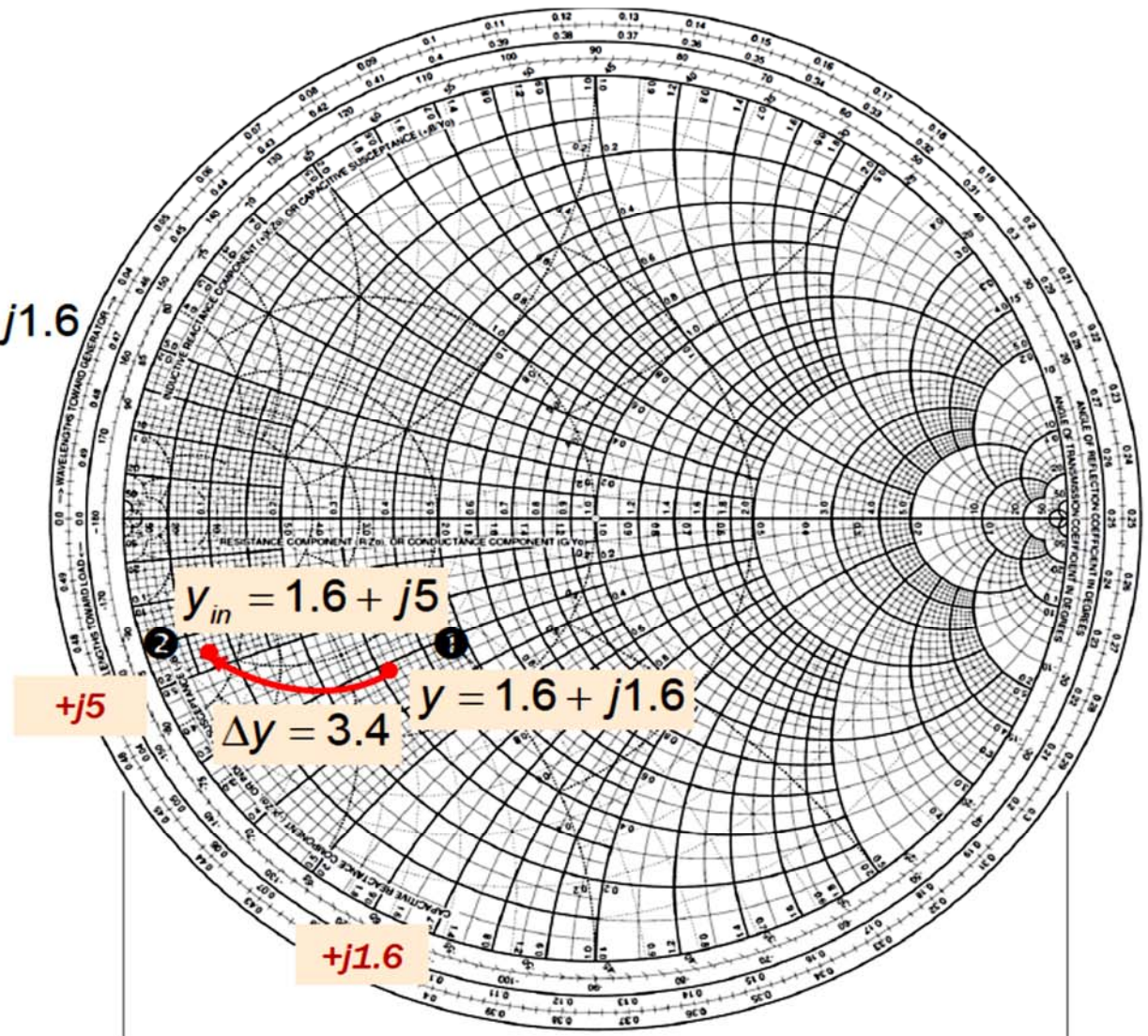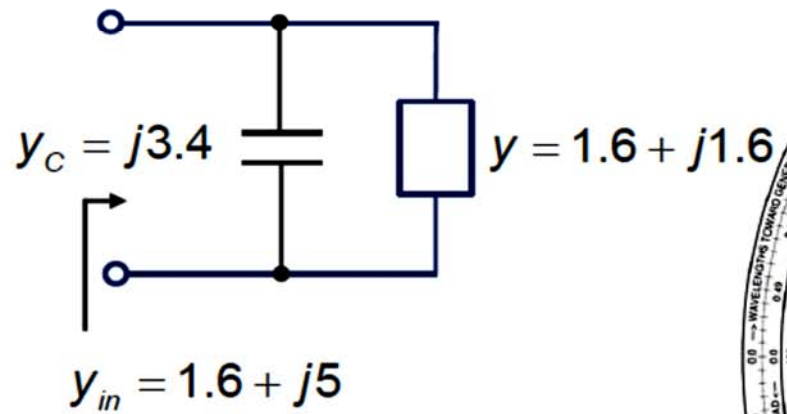

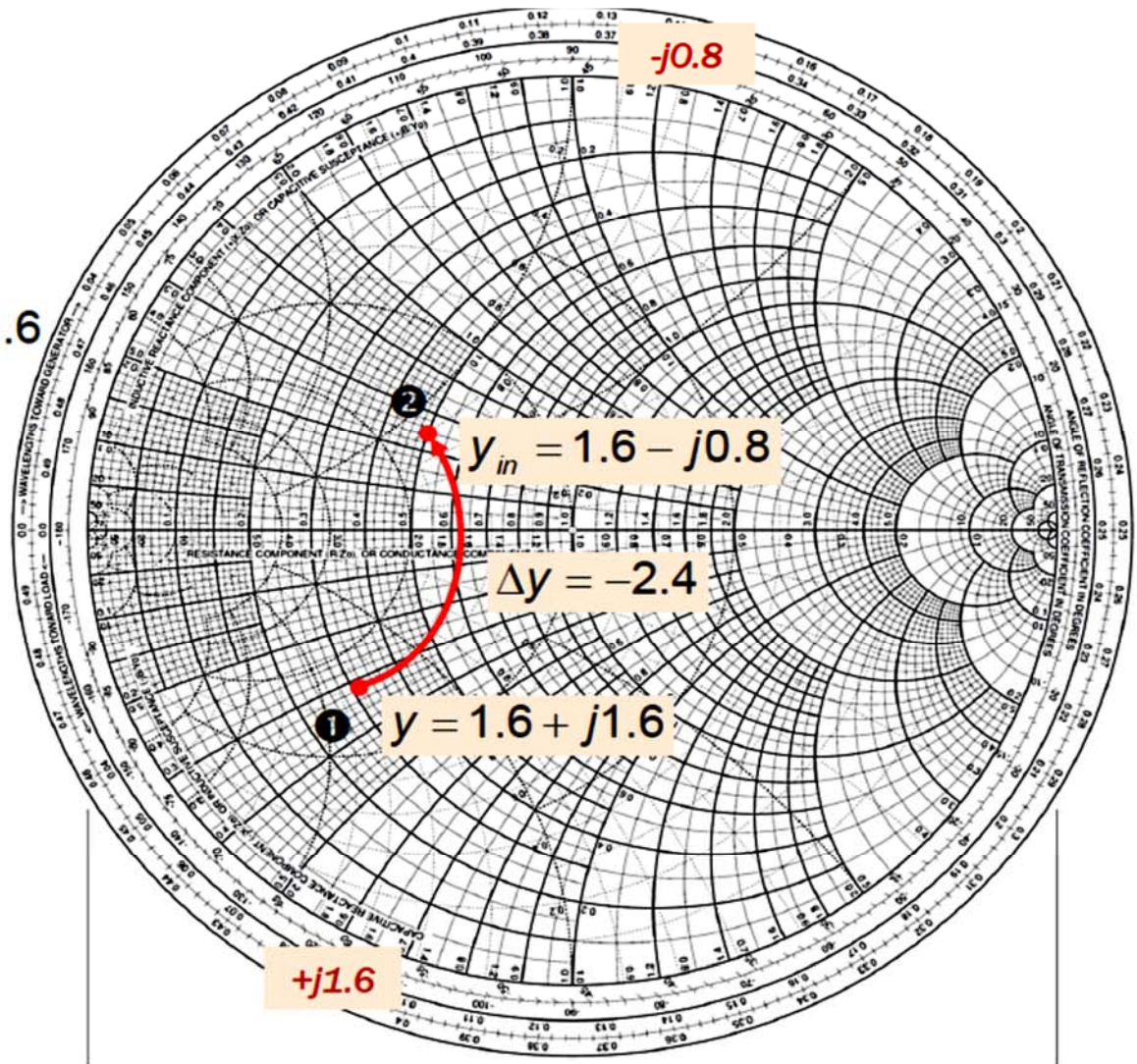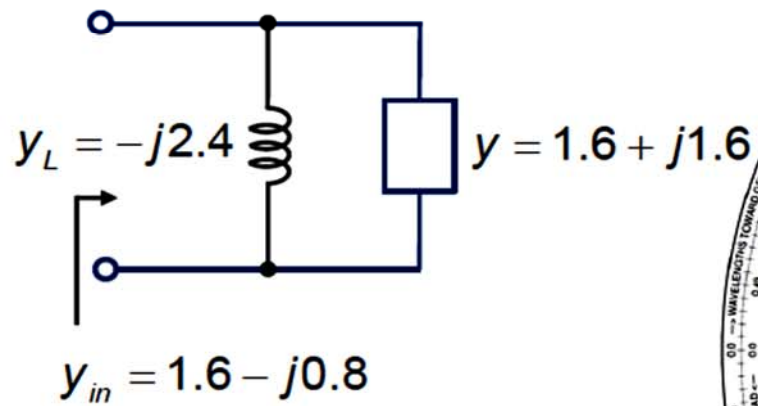


6. ZY Chart

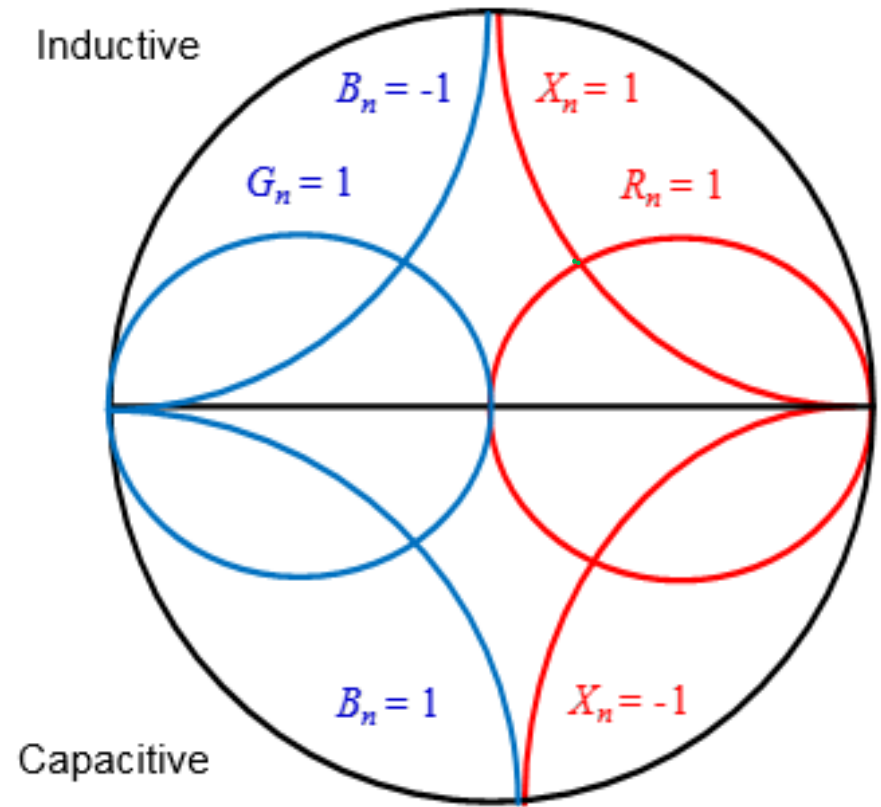
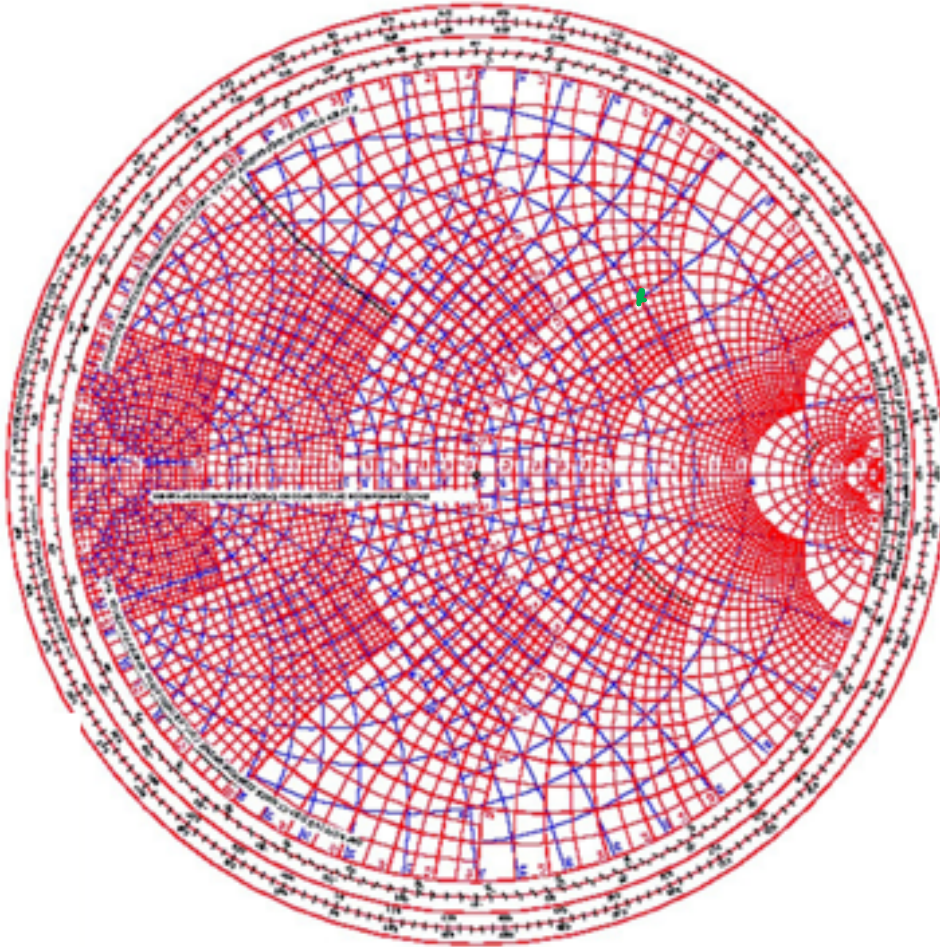


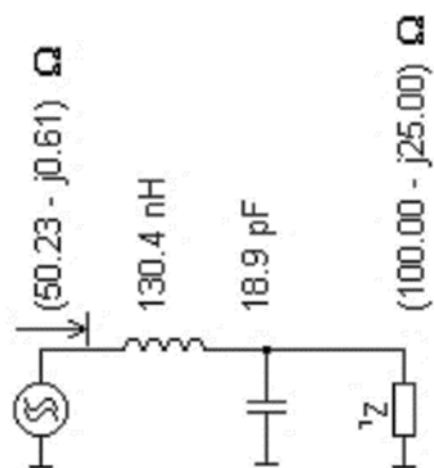

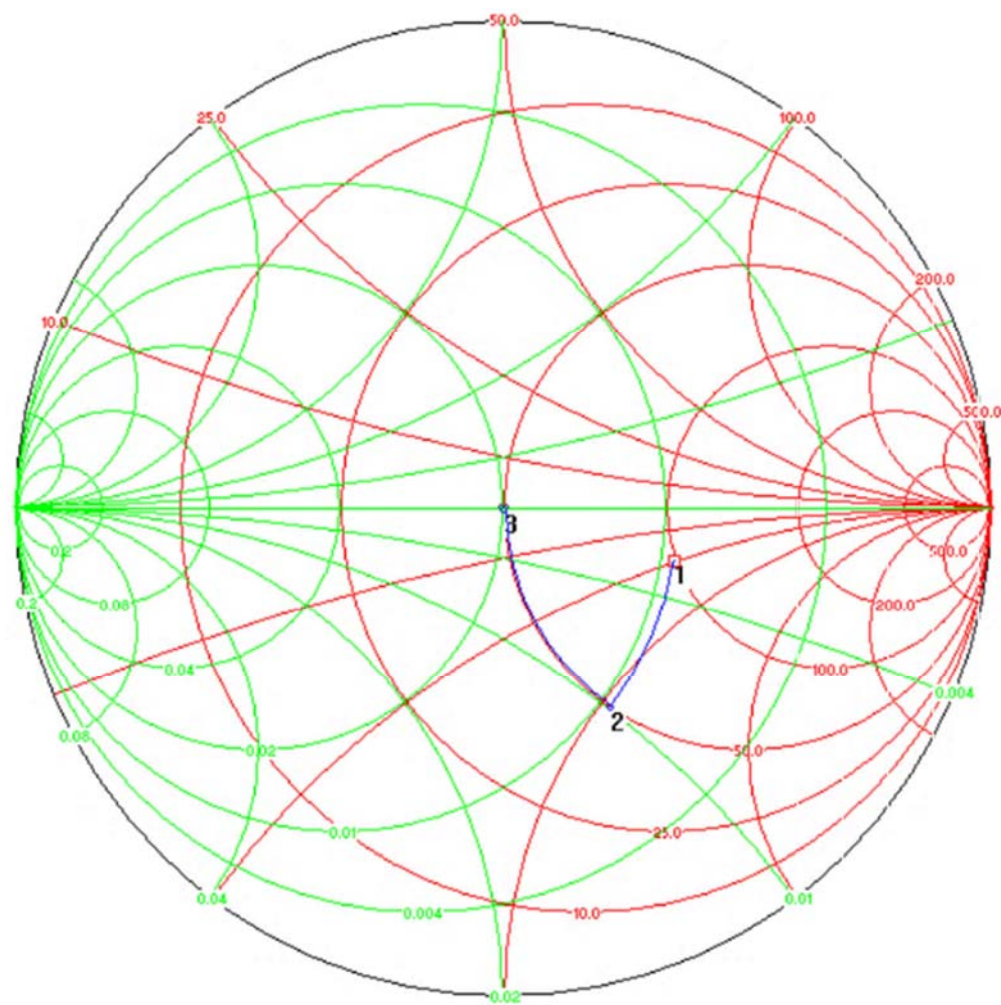
$Z_0 = 50.00 \Omega$
 $f_{\text{main}} = 64.000 \text{ MHz}$



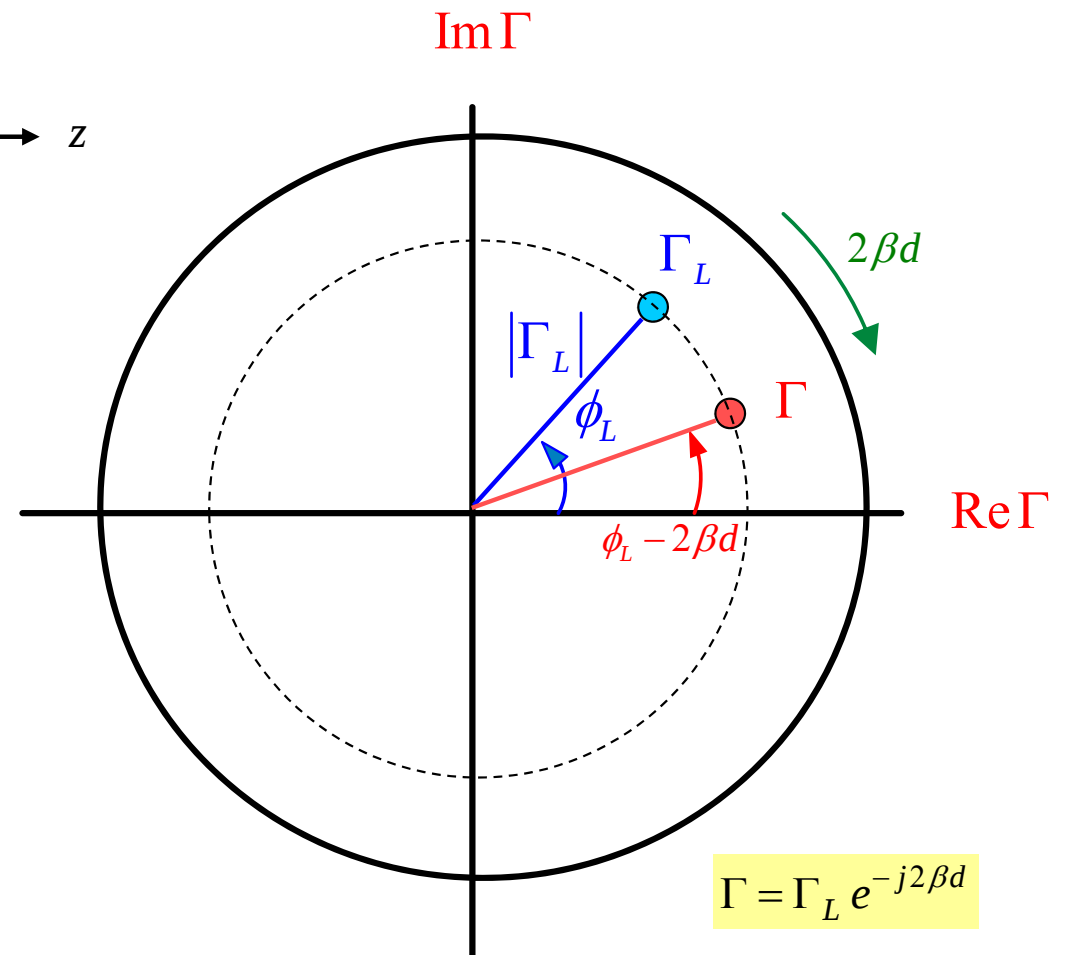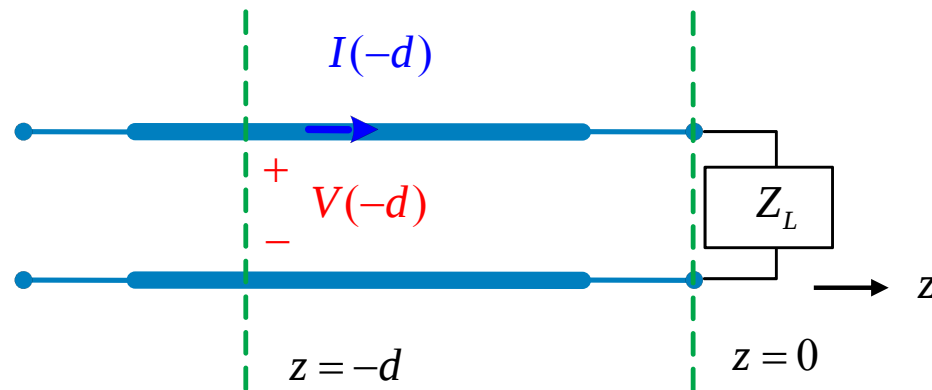- Calculating Γ on different points in a transmission line



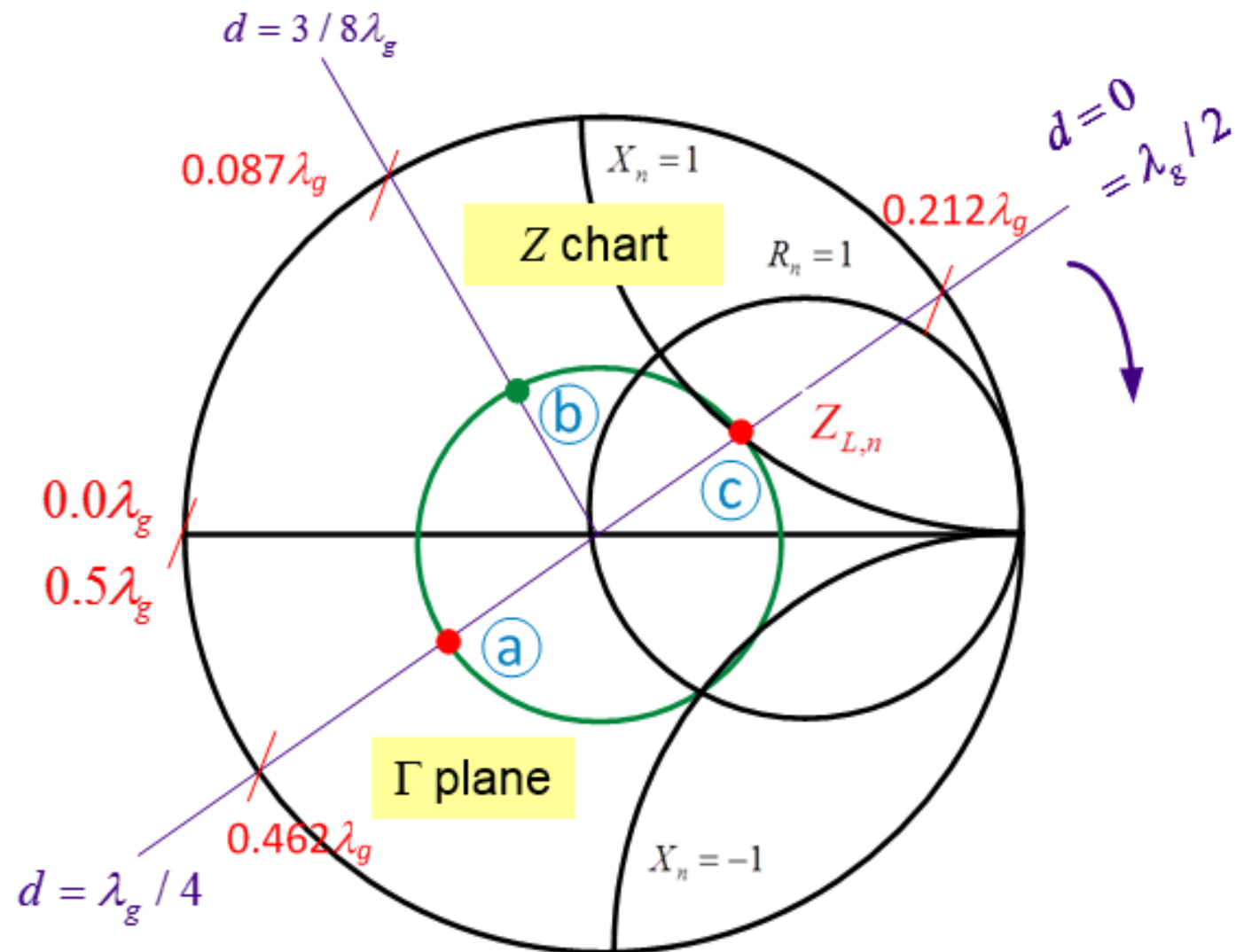- Γ with a quarter-wave TL and a half-wave TL




■ Short-circuited transmission line


Use a short-circuited section of air-filled TEM, $50\ \Omega$ transmission line ($\beta = k_0$, $\lambda_g = \lambda_d = \lambda_0$) to create an impedance of $Z_{in} = -j25\ \Omega$ at $f = 10\ \text{GHz}$.

Use the Z chart.
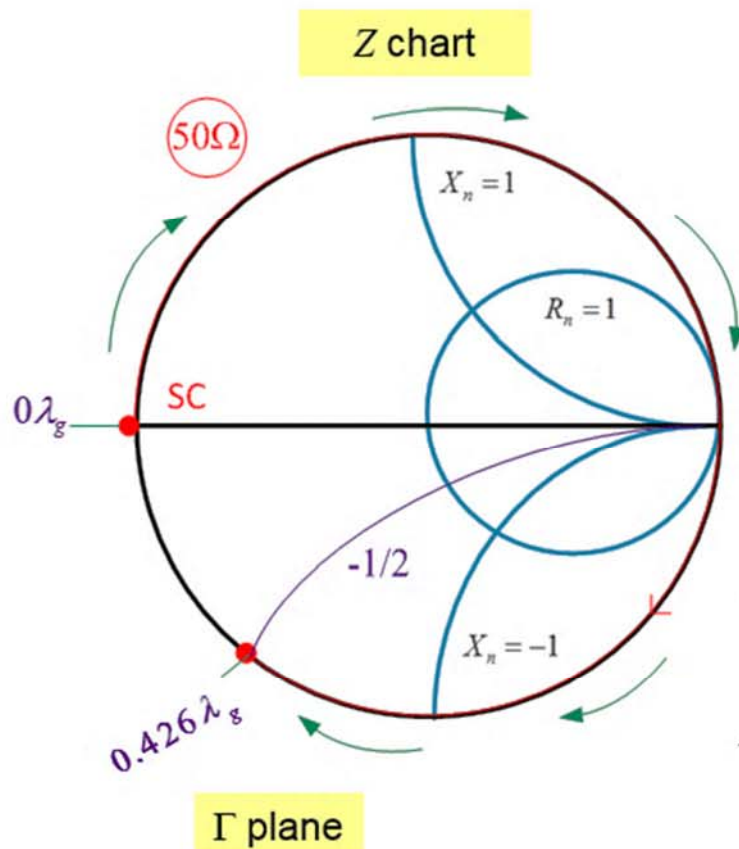
$$Z_{in,n} = -j \frac{25}{50} = -j(0.5)$$



$$Z_{in} = -j25\ \Omega$$

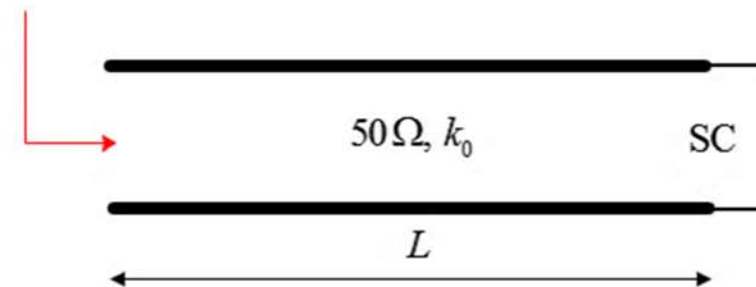

$$L = 0.426\lambda_g - 0\lambda_g = 0.426\lambda_g = 0.426\lambda_0$$


$$\lambda_0 = \frac{c}{f} = \frac{2\pi}{k_0} = \frac{2\pi}{\omega\sqrt{\mu_0\epsilon_0}} \quad \lambda_0 = 3.0\ \text{cm}$$

$$\Rightarrow L = 1.28\ \text{cm}$$

- Open-circuited transmission line

Use an open-circuited section of $75\ \Omega$ ($Y_0 = 1/75\ \text{S}$) air-filled transmission line at $f = 10\ \text{GHz}$ to create an admittance of $Y_{in} = j1/75\ \text{S}$:

Use the Y chart.

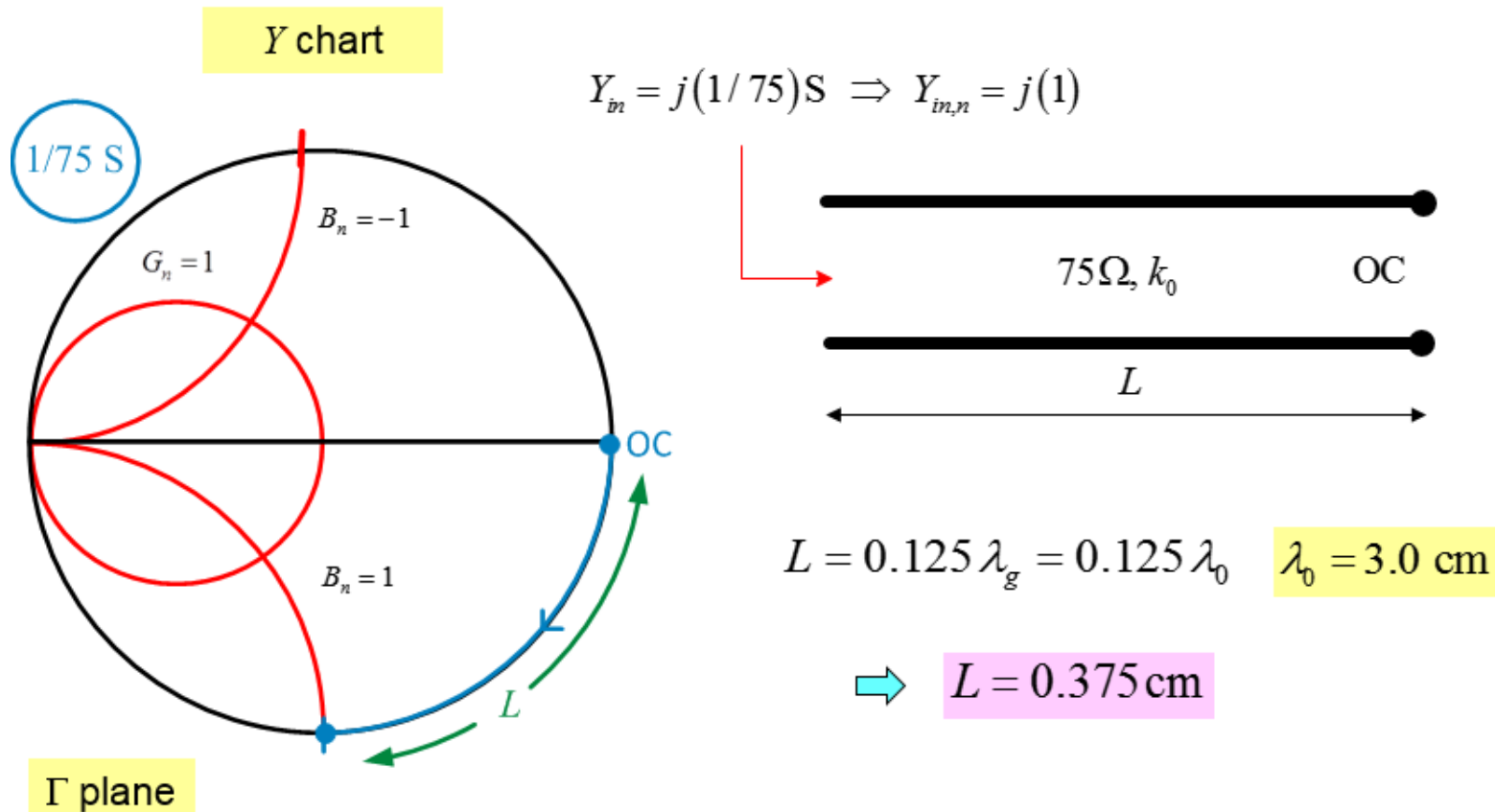

Fin
(End)